

Total number of printed pages—6

53 (CE 201) BSEL

2014

BASIC ELECTRONICS

Paper : EC 201

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

1. (a) What do you mean by a semiconductor ? Describe the covalent bond formation in germanium. 3
- (b) What do you understand by intrinsic and extrinsic semiconductor ? With the help of diagram explain how holes contribute to electric current in *P*-type semiconductor. 3

Contd.

(c) Explain the behaviour of a $P-N$ junction under forward and reverse biasing. 8

(d) Explain the following terms : $3 \times 2 = 6$

(i) Ideal Diode


(ii) Knee Voltage

(iii) Dynamic Resistance.

2. (a) What do you mean by rectification? Explain the principle of operation of a full-wave rectifier. Draw the waveforms of the diode current and load voltage for a sinusoidal input voltage applied to full wave rectifier. Derive the expression for average DC load current (I_{DC}) and average DC load voltage (E_{DC}) for F.W.R. 10

(b) Distinguish between a half-wave and a full-wave rectifier. 5

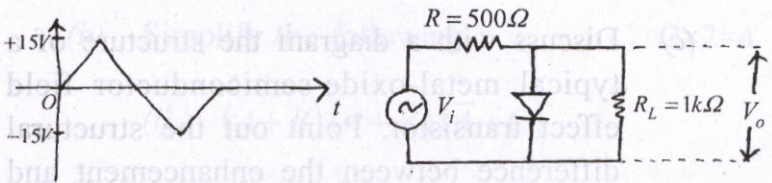- (c) The positive shunt clipper shown in figure has the input waveform as indicated. Determine the value of V_o for each of the input alternations. The silicon diode has $V_T = 0.7V$. 5



3. (a) Explain the word transistor. Clearly show the biasing arrangement of a PNP and NPN transistor for conduction. 5
- (b) Define α and β of a transistor. Give the relationship between α , β and prove it. 5
- (c) If the base current in a transistor is $20\mu A$ when the emitter current is $6.4mA$, what are the values of α and β ? Also calculate the collector current. 5
- (d) What do you understand by transistor biasing? Describe the voltage divider biasing method in detail. 5

4. (a) With a neat sketch, describe the construction of an n -channel JFET. Explain its principle of operation and also show static and transfer characteristics. 12

(b) Deduce the relationship $\mu = r_d g_m$. 3

(c) Discuss with a diagram the structure of a typical metal-oxide-semiconductor field effect transistor. Point out the structural difference between the enhancement and depletion forms of the MOSFET. 5

2.

5. (a) With a neat diagram, explain the working of a R - C phase shift oscillator. 5

(b) A Hartley oscillator circuit has $L_1 = L_2 = 100 \mu H$. The frequency of oscillations required is $50 kHz$. Calculate value of the capacitance required. 5

(c) For a non-inverting amplifier using OP -amp, derive the expression for voltage gain with feedback. 5

(d) List the important characteristics of an ideal OP -amp. What is CMRR? 5

53

6. (a) Perform the following operations : $3 \times 2 = 6$

(i) Convert $(125)_8$ to binary

(ii) $(1C00)_{16}$ to decimal

(iii) $(8000)_{10}$ to hexadecimal.

(b) Simplify the following : $2 \times 2 = 4$

(i) $(A+B)(A+\bar{B})(\bar{A}+C)$

(ii) $AB + (\overline{A+B}) + AC$

(c) The Boolean expressions of the two variables X and Y in terms of the three inputs A , B and C are given by 5

$$X = ABC + A\bar{B}\bar{C} + \bar{A}BC$$

$$Y = (\bar{A} + \bar{B} + \bar{C}) \cdot (\bar{A} + B + C) \cdot (A + \bar{B} + C)$$

What is the relationship b/w X and Y ? and

(d) Explain the importance of flip-flops in a digital system. What is S - R flip-flop? Give its logic symbol and the truth table. 5 3

7. Write short notes on : (any four) 4×5=20

- (i) Avalanche and Zener effect
- (ii) Colpitt's Oscillator
- (iii) C.R.O.
- (iv) Wein Bridge Oscillator
- (v) Filters
- (vi) LCD display.