

Total No. of printed pages = 3

EI/IT/Co-403/DE/4th Sem/2017/M

## DIGITAL ELECTRONICS

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer question No.1 and any *four* from the rest.

1. Answer the following as directed :  $1 \times 10 = 10$

(a)  $584_{10} = ( )_2$

(b)  $12 = ( )$  excess -3 code

(c)  $(01110101)_2 = ( )$  gray code

(d)  $(110010) = ( )$  one's complement

(e)  $FFFFH = ( )_2$

(f)  $(1011 \cdot 101)_2 + ( \cdot 101 )_2 = ( )_2$

(g)  $(2479)_{10} = ( )_{16}$

(h)  $(355)_8 = ( )_2$

(i)  $(1011 \cdot 011)_2 = ( )_{10}$

(j)  $(435)_{10} = ( )_8$

[Turn over

2. (a) What do you mean by universal gate ? How can you show the three operations NOT, AND, OR with the help of universal gate ? 8
- (b) State Duality theorem with example. 4
- (c) Find the dual of the following : 3
- $$\overline{AB} = \overline{A} + \overline{B}$$
3. (a) Using the truth table, show that the Boolean expression  $A + \overline{A}B = A + B$  4
- (b) Using Boolean algebra, simplify the Boolean expression : 4
- $$Z = \overline{AB + AC} + \overline{ABC}$$
- (c) Draw a Karnaugh Map for the following function of four variable and use it to reduce the function : 7
- $$F(P, Q, R, S) = \sum m (0, 1, 4, 5, 3, 2, 11, 10)$$
4. (a) What do you mean by Half Adder and Full Adder ? Explain half and full Adder giving logic gates and truth table. 10
- (b) Compare MOS circuit and TTL circuit. 5

5. (a) What is flip flop ? Draw the circuit diagram and logic symbols for J-K flip flop and give the truth table.  $2+8=10$

(b) Draw the circuit for TTL NAND gate and explain its operation briefly. 5

6. Write short notes on any *two* :  $7\frac{1}{2}\times 2=15$

(i) ASCII code

(ii) Seven segment display

(iii) Master-slave J-K flip flop

(iv) Full subtractor

(v) Digital comparator.