

Total No. of printed pages = 6

**END SEMESTER EXAMINATION - 2019**

Semester : 4th (New Syllabus)

Subject Code : CO-406

**DIGITAL ELECTRONICS**

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks  
for the questions.

**PART – A**

**Marks – 25**

1. Fill in the blanks : 1×10=10
- (a) Output of AND gate is high if and only if its all inputs are \_\_\_\_\_.
  - (b) NOT gate is also known as \_\_\_\_\_.
  - (c) Nibble is a group of \_\_\_\_\_ bits.
  - (d) BCD means \_\_\_\_\_.
  - (e) Demultiplexer has \_\_\_\_\_.

[Turn over



- (f) Flip flop is a \_\_\_\_\_ element.
  - (g) Flip flop has \_\_\_\_\_ states.
  - (h) SISO means \_\_\_\_\_.
  - (i) Minimum number of flip flop required for decade counter is \_\_\_\_\_.
  - (j) ROM means \_\_\_\_\_.
2. Write true or false : 1 × 10 = 10
- (a) In NAND gate output is high if all inputs are high.
  - (b) Flip flops are memoryless elements.
  - (c) In 2's complement representation one is added to its one's complement form.
  - (d) Zero is used to represent positive sign number.
  - (e) Encoding is the process of coding alphabets, numerals and symbols in binary format.
  - (f) Karnaugh-map (K-map) is used to minimize logic operations.



- (g) Resistors is composed of group of flipflops to store group of bits.
  - (h) In bidirectional register, data can be shifted in one direction.
  - (i) Up counter increases on every clock pulse.
  - (j) LED is liquid emission diode.
3. Choose the correct answer : 1 × 5 = 5
- (a) Output of Ex-OR gate is
 

(i) $AB+AB$	(ii) $AB+AB'$
(iii) $AB+AB'$	(iv) $AB'+AB$
  - (b) Add binary numbers 1011 and 1100
 

(i) 10111	(ii) 10011
(iii) 10001	(iv) 11100
  - (c) In SOP (sum of product) form
    - (i) AND terms ORed together
    - (ii) OR terms ANDed together
    - (iii) AND terms ANDed together
    - (iv) OR terms ORed together