

Total number of printed pages:4

2021

D/3rd/DECE302

ELECTRONIC DEVICES AND CIRCUITS

Full Marks: 100


Time: Three hours

The figures in the margin indicate full marks for the questions.


Answer any five questions.

 1. a) The number of electrons in the valence shell of Si is _____ . 1
- b) The unit of resistivity is _____ . 1
- c) At zero degree Kelvin, the acceptor energy level is completely _____ . 1
- d) In a semiconductor, the product of electron and hole concentrations is a constant of _____ . 1
- e) Under reverse bias, the current in a p-n junction diode is due to _____ carriers. 1
- f) The expression for forward bias current can be approximated as _____ function. 1
- g) The dynamic resistance of a diode varies with the _____ of the diode. 1
- h) The voltage across a Zener diode is _____ when it is operating in the breakdown region. 1
- i) An LED emits light when it is _____ biased. 1
- j) If we connect a Si and Ge diodes in parallel (with same type of bias) and them in series with a 100-ohm resistance and a battery of 1 Volts, the current will flow through _____ diode. 1
- k) The peak inverse voltage (PIV) rating required for the diode used in half wave rectifier (HWR) circuit is _____ . 1
- l) The conduction angle for a full wave rectifier (FWR) with ideal diodes is _____ degrees. 1
- m) The average dc voltage at the output of a FWR with ideal diodes is _____ times that of a HWR. 1


- n) In a clamper circuit which can shift the input waveform upwards, the capacitor voltage will have a polarity in the _____ direction of the input waveform. 1
- o) The regulation of output voltage against the variation of input fluctuation is called _____. 1
- p) The _____ region has the smallest width in the structure of BJT. 1
- q) The dc current gain in CB configuration is approximately equal to _____. 1
- r) For obtaining the ac equivalent circuit, the dc voltage sources are replaced by _____. 1
- s) For common collector (CC) configuration, the load resistance is connected to _____ terminal of the transistor. 1
- t) The gate material in a p-channel JFET is made of _____. 1
2. a) Why the number free electrons and holes are equal for intrinsic semiconductor? 4
- b) What do you understand by the term 'doping'? 4
- c) Draw the energy band diagram of n-type and p-type semiconductors and discuss why they have greater conductivity than the intrinsic semiconductor. 8
- d) What do you mean by depletion region and how it is created in a p-n junction diode? 4
3. a) Draw and explain the I-V characteristics of a p-n junction diode. 4
- b) Discuss the mechanism of avalanche breakdown in a reverse biased p-n junction diode. 4
- c) In the following circuit, find the value of current through $5.6\text{K}\Omega$ resistance. 4



 - d) Draw the diode-resistor circuit implementation of a two input OR gate and explain how it satisfies the truth table. 4
- e) Draw the circuit diagram of a center tapped transformer FWR and explain its working. 4
4. a) Derive the value of minimum input voltage required for regulation action in a Zener voltage regulator. 5
- b) Why Bipolar Junction Transistor (BJT) is called so? Explain the working of a BJT biased in an active mode. 5
- c) Find the output voltage waveform of the following circuit. 5



 - d) Identify the following circuit and plot its output waveform. 5




5. a) Draw the circuit diagram of a pnp transistor biased under CB configuration and mark the direction of current flow at each terminal. Identify the input and output current and voltages for this configuration. 5
- b) Draw the input and output characteristics of a BJT in CE configuration and explain how it is able to amplify a weak input signal. 5
- c) Explain the purpose of biasing circuits in small signal amplifiers. 4





- d) Determine the dc bias voltage V_{CE} and the current I_C for the voltage-divider bias network shown below.

6

 

Given

$\beta = 100$, $V_{CC} = +22.0V$,
 $R_1 = 39K\Omega$, $R_2 = 3.9K\Omega$,
 $R_E = 1.5K\Omega$, $R_C = 10K\Omega$,
 $C_E = 50\mu F$ and
 $C_1 = C_2 = 10\mu F$

6. a) What do you understand by pinch-off in JFET operation? Explain how it differs when $V_{GS}=0$ in comparison to when $V_{DS}=0$. 5
- b) Write the expression for saturation current for a p-channel JFET as a function of gate to source voltage and explain its significance. 5
- c) Draw the schematic diagram of a p-channel depletion type MOSFET and explain its working. 5
- d) Write the expression for transfer characteristics of an enhancement type MOSFET. Explain how it could be used to explain the operation of both n-channel and p-channel devices. 5
7. a) Draw the r_e model of a BJT in CE configuration and explain how it is able to duplicate its small signal operation. 6
- b) Write the hybrid parameter equations for a two-port network. Discuss what each parameter stands for when it models a BJT in CB configuration. 6
- c) Derive the expressions for (i) input impedance Z_i (ii) output impedance Z_o and (iii) voltage gain A_V in the case of a voltage-divider bias network using its small-signal equivalent. 8