

Total No. of printed pages = 4

19/3rd Sem/DECE302

2021

ELECTRONIC DEVICES AND CIRCUITS

Full Marks – 100

Time – Three hours


The figures in the margin indicate full marks for the questions.

Question No. 1 is compulsory and answer any *four* questions from the rest.

1. (a) Write a short note on n-type semiconductor. 5
- (b) Why semiconductors are popular choice for making electronic components? 2
- (c) What do you mean by doping in semiconductors? Mention the different types of doping materials. 1+2=3
- (d) Name the part number of a general purpose pt.-diode; mention few applications of diodes. 1+2=3

[Turn over

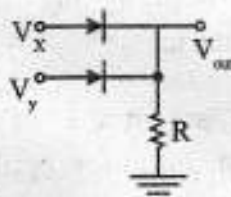
- (e) Mention the various operation modes of BJT. Which mode is suitable for signal amplification purpose? $1+1=2$
- (f) What do you mean by Pinch-off voltage and write the expression for MOSFETs. $1+1=2$
- (g) How depletion layer is formed in pn-junctions? explain in brief. 3
2. (a) Write a comparison between the Zener Breakdown and Avalanche Breakdown. 6
- (b) Draw the input and output characteristics of NPN transistor in Common Emitter Configuration. $2+2=4$
- (c) Derive the expression for I_{CBO} in relation to I_{CEO} . Hence find the relation between α and β . $4+6=10$
3. (a) Describe the operation of the circuit if V_x and V_y can be $0V/5V$ and find the output voltage for different condition of input voltages. Assume ideal diodes. 10



10/19/3rd Sem/DECE302

(2)

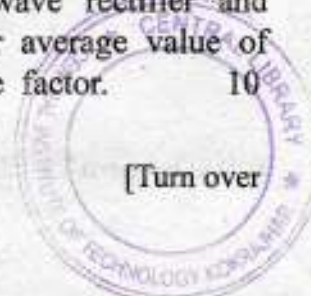- (b) The current gain of a transistor in CE mode is 49. Calculate its CB current gain. Also find the collector current when the emitter current is 3mA. 5
- (c) For a certain transistor, base current is $20\mu\text{A}$; Collector current is 2mA and $\beta = 80$. Calculate value of I_{CBO} . 5
4. (a) Describe the operation of n-Channel MOSFET (Enhancement) and draw the $I_{DS} \sim V_{DS}$ characteristics. 10
- (b) (i) Draw the model of NPN transistor in active mode. 4
- (ii) Explain the operation of RC filter with proper circuit diagram. 6
5. (a) Describe the construction and working principle of JFET and write the expression for I_{Ds} . 6
- (b) Compare the Depletion and Enhancement mode of MOSFET. 4
- (c) Draw the circuit diagram of Center-tapped transformer based full wave rectifier and derive the expression for average value of output voltage and ripple factor. 10



6. (a) Describe the operation of NPN transistor in Common-Base Configuration, draw the input and output characteristics. 6+4=10
- (b) Describe the operation of p-channel MOSFET (Enhancement) and draw the $I_{DS} \sim V_{DS}$ characteristics. 10

