

Total No. of printed pages = 4

19/3rd Sem/DECE303

2021

DIGITAL ELECTRONICS

Full Marks -100

Time – Three hours

The figures in the margin indicate full marks
for the questions.

Answer any five questions.

1. (a) Convert the following : $1 \times 4 = 4$

- (i) Binary 1001 into decimal
- (ii) Decimal 31 into binary
- (iii) F01 into binary
- (iv) Binary 110001 into Hexadecimal.

(b) Simplify the following using Boolean algebraic techniques : $1 \times 5 + 2 \times 3 = 11$

- (i) $a+ab$
- (ii) $a+a'b$
- (iii) $a+abc$

[Turn over

(iv) $(a+b)(a+b')$

(v) $a'+a'' + a' + a'$

(vi) $(x'+y')' + (x \cdot y)'$

(vii) $(x \cdot x' + x + x' + x'')'$

(viii) $xyz + xyz' + x'y'z' + xy'z'$.

(c) Prove that $x+yz = (x+y)(x+z)$. 5

2. (a) Use kmap method to simplify below Boolean equations. $2+3+5 \times 2=15$

(i) $f(x,y) = \sum m(0,1,2)$

(ii) $f(x,y,z) = \sum m(0,1,4,5)$

(iii) $f(w,x,y,z) = \sum m(0,1,4,5,8,9)$

(iv) $f(w,x,y,z) = \sum m(0,2,4,6,8,10,11,15)$

(b) Use basic gates to realize
 $Y = xy + (xy)'z + x'y'z (x+y)'$ 5

3. (a) Design the following : $4+6=10$

(i) Half Adder

(ii) Full Adder

(b) Use NAND gate only to realize 3+3=6

(i) $Y = A + B$

(ii) $Y = AB$

4. (a) Find out minterm for following : 1×3=3

(i) $x = 0 \ y = 1 \ z = 0$

(ii) $w = 0 \ x = 0 \ y = 1 \ z = 1$

(iii) $x = 0 \ y = 1$

(b) Find out maxterm for following : 1×3=3

(i) $x = 1 \ y = 1 \ z = 0$

(ii) $w = 1 \ x = 0 \ y = 1 \ z = 1$

(iii) $x = 1 \ y = 1$

(c) Convert the following : 2×2=4

(i) $xyz + xy'z + xy$ into canonical SOP form.

(ii) $(x+y)(x+y+z)$ into canonical POS form.

(d) Design a Full Subtractor.

5. (a) Draw the logic diagram and explain it's truth table of the following latches. $2 \times (2+3)=10$
- (i) S-R latch
(ii) J-K latch.
- (b) Use two input basic gates to realize the following boolean functions : $2 \times 2 + 3 \times 2 = 10$
- (i) $Y=abcd$ (ii) $Y= a+b'+c+d$
(iii) $Y=a+bcd'$ (iv) $ab+b'(a+cd)$
6. (a) Design a 2 to 4 Decoder. 5
- (b) Draw the symbol and truth table of a XNOR gate. 2
- (c) Design 4:1 Multiplexer and 1:4 De-multiplexer. $5 \times 2 = 10$
- (d) Prove that $(a+b+c)'=a'.b'.c'.$ 3

