

Total No. of printed pages = 6

19/3rd Sem/DECE305



2021

ELECTRIC CIRCUITS AND NETWORK


Full Mark – 100

Time – Three hours

The figures in the margin indicate full marks for the questions.


Answer any *five* questions.

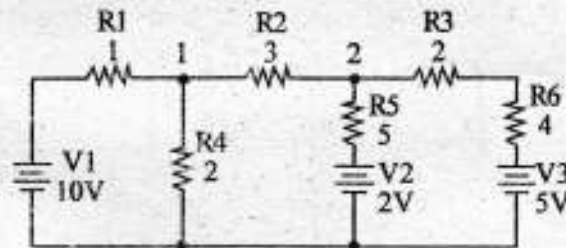1. (a) Point out the main differences between Nodal and Mesh analysis. 5
- (b) Find the voltage (V) at node 1 in the circuit shown by using Nodal analysis. 8




[Turn over

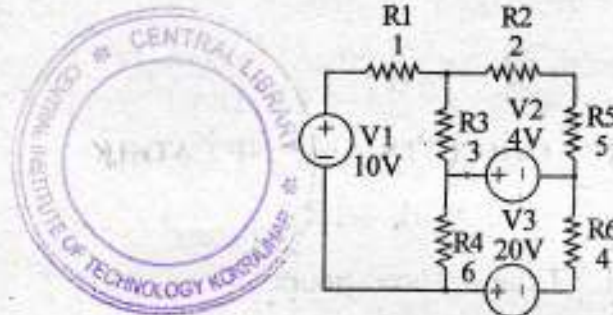
- (c) Find the current I_3 (A) from the figure given below by using Mesh analysis. 7



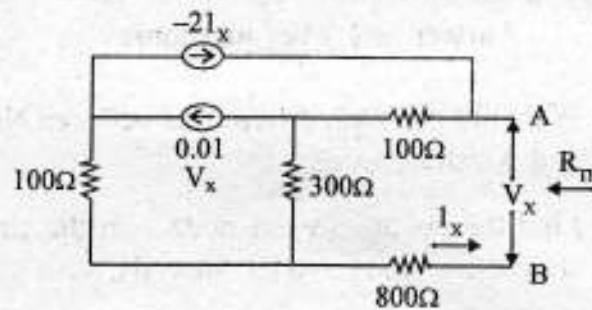2. (a) For the circuit shown in figure below, find the value of Norton's resistance: 5



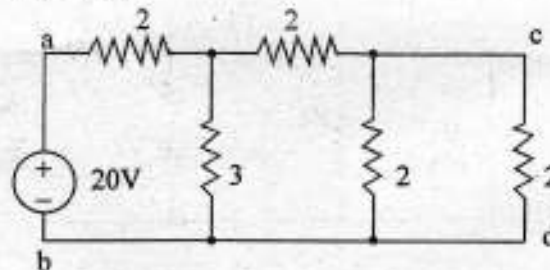- (b) The following circuit satisfies Reciprocity Theorem. 1



True or False ?

(c) While considering Reciprocity theorem, we consider ratio of response to excitation as ratio of? 1


- (a) voltage to voltage
- (b) current to current
- (c) voltage to current
- (d) None of the mentioned above

(d) Define maximum power transfer theorem. Also find the condition of maximum power transfer in an electrical circuit. 1+6=7

(e) For the incidence matrix shown below, draw the graph. 6

	1	2	3	4	5	6	7	8		
a	[1	0	0	0	1	0	0	1]
b	[0	1	0	0	-1	1	0	0]
c	[0	0	1	0	0	-1	1	-1]
d	[0	0	0	1	0	0	-1	0]

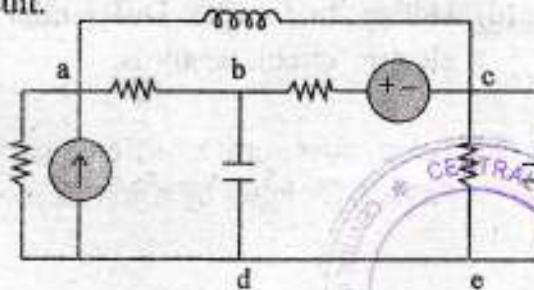3. (a) Refer the circuit shown below. Draw the graph, one tree and its co-tree from the circuit. 6




(b) For the network shown below, determine the number of all possible trees. For a tree consisting of (1, 2, 3)

(i) draw tie set matrix

(ii) draw cut-set matrix.

6

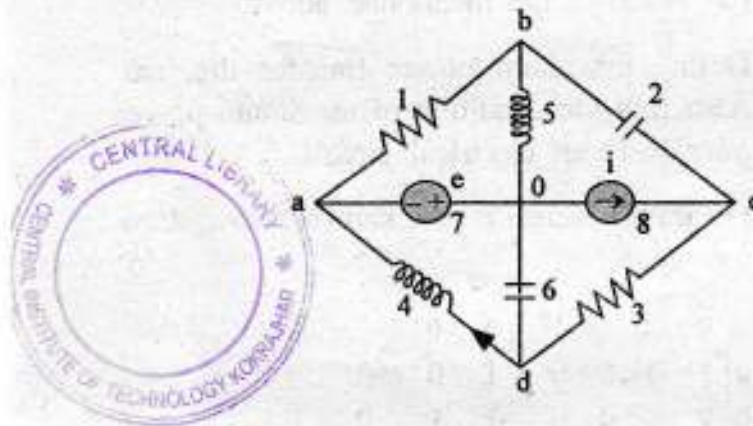

(c) What do you mean by Time domain and frequency domain analysis? Also differentiate between them. 2+3=5

(d) Define first order Differential equation of electric circuit analysis. 3

4. (a) Solve first order differential equation of series RC circuit by using its proper diagram. 7

(b) A series RL circuit with $R = 35\Omega$ and $L = 20$ H has a constant voltage $V = 100$ V applied at $t = 0$ by the closing of a switch. Find,


7

- (i) The equation for i .
 - (ii) The current at $t = 1.65$ s
 - (iii) The expressions for V_R and V_L
 - (iv) The time at which $V_R = V_L$
- (c) Find the transient response of series RL circuit in details. 6

5 (a) What do you mean by Fourier series? Also explain Dirichlet's condition of Fourier series. 2+4=6

(b) Explain about the three different coefficients (with equations) of Trigonometric Fourier series representation. 7

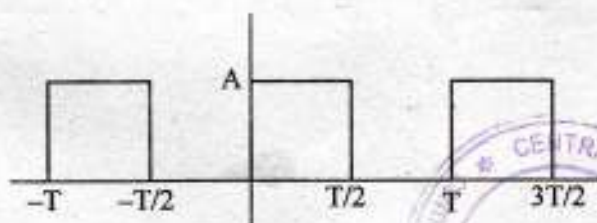(c) Determine the Fourier series of the wave shown in figure below. 7



6. (a) Differentiate between the Average value and RMS value of periodic wave in Fourier series representation by using proper equations. 7
- (b) Define Fourier Transform. Also explain the Dirichlet's condition of the same. 2+4=6
- (c) Obtain the Fourier transform of a two sided exponential function e^{-at} . 7
7. (a) What is known as Z-parameter of two port network? Explain. 7
- (b) What is known as Y-parameter of two port network? Explain. 6
- (c) What is known as H-parameter of two port network? Explain. 7

