

2022



**ELECTRIC CIRCUITS AND NETWORK**





Full Marks : 100





Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

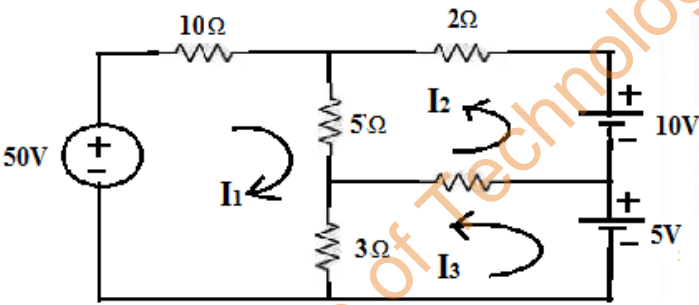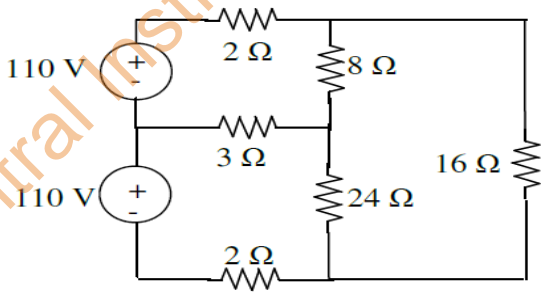1.	a) Define node and mesh of a network. Write statement of Norton's and Thevenin's theorem.	3+5=8
	b) Determine the mesh currents for the following network. 	6
	c) Using nodal analysis find all branch currents for the following circuit 	6
2.	a) Define the following terms (i) Branch (ii) Sub graph (iii) Tree	3
	b) For the graph below, find incidence and cut set matrices.	8

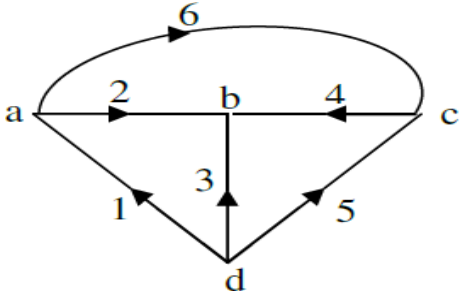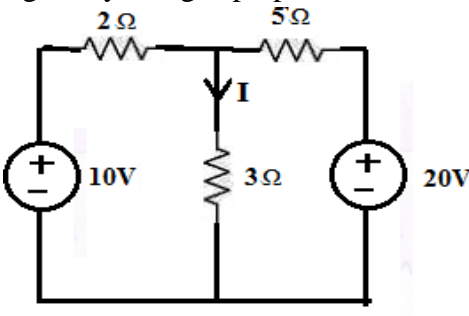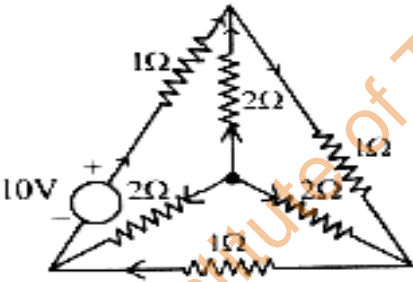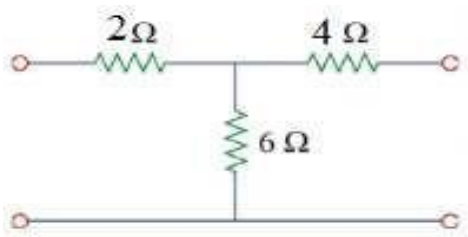			
	c)	<p>State Reciprocity theorem. Calculate the current “I” shown in below figure by using superposition theorem.</p> 	3+6=9
3	a)	<p>Define and state the properties of incidence matrix. For the network shown below, draw the graph and find incidence and tie – set matrix.</p> 	5+8=13
	b)	<p>State and prove Maximum power transfer theorem.</p>	7
4	a)	<p>What is transient and steady state of a circuit. Derive the Transient Response of series RL-circuit with D.C excitation.</p>	3+7=10
	b)	<p>Find the Z and Y parameters for the following circuit.</p> 	10

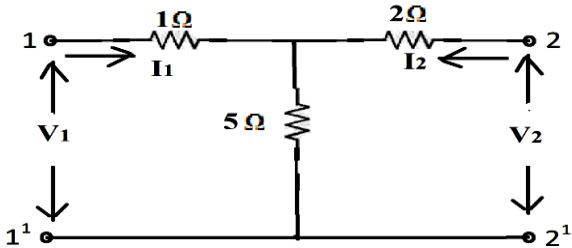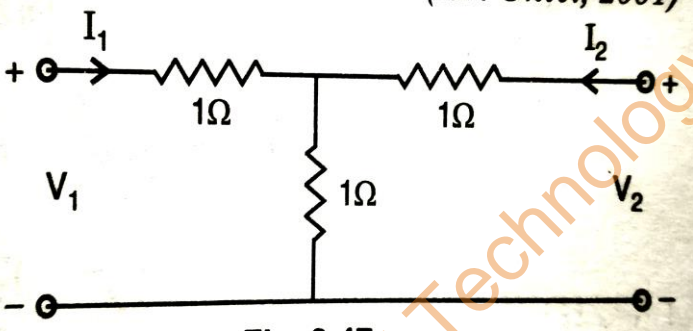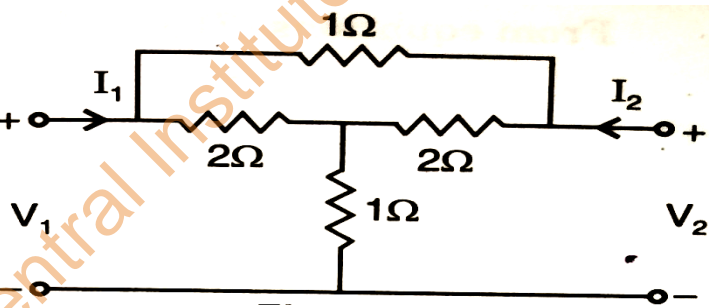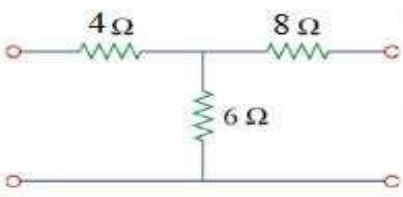5	<p>a) Define Two-port network. The given Y-parameters are, <math>Y_{11}= 0.5</math>, <math>Y_{12}= Y_{21}= 0.6</math>, <math>Y_{22}= 0.9</math>. Find the impedance parameters.</p>	2+3=5
	<p>b) Find the transmission parameters for the circuit shown in figure.</p> 	5
	<p>c) Define input and output impedances. Derive the condition (or result) for parallel interconnection of two 2-port networks.</p>	3+7=10
6	<p>a) Two identical sections of the network shown in figure are cascaded. Calculate the transmission parameters of the resulting network</p> 	7
	<p>b) Find the short circuit and open circuit impedances of the network shown in figure.</p> 	7
	<p>c) Find the h- parameters for the following circuit.</p> 	6