

2023

ELECTRIC CIRCUITS AND NETWORK

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

1. a) What is the difference between loop and mesh? Find i_1 and i_2 of the following circuit (Figure-1). 3+5=8

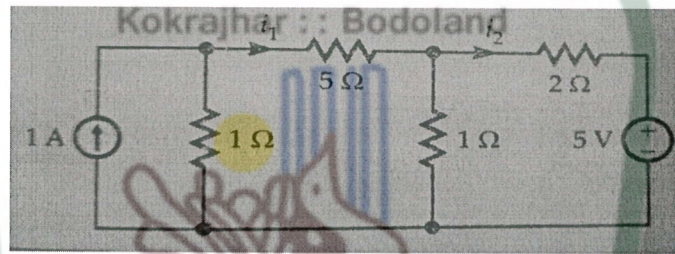


Figure-1

- b) State and prove the maximum power transfer theorem. Find the current in the 5Ω resistor for the circuit shown in Figure-2 6+6=12

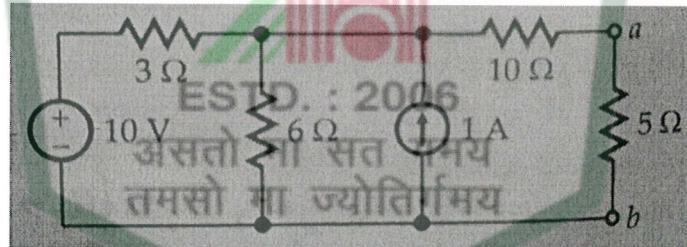


Figure-2

- 2 a) Explain the procedure to obtain Thevenin's and Norton's equivalent circuits. 5
- b) Define the terms: (i) Graph (ii) Tree (iii) Incidence matrix (iv) Cut-set matrix (v) Tie-set matrix 3×5=15
- 3) a) Write properties of the tree of a graph. Draw a graph of resistive network shown in Figure-3. Select a suitable tree and obtain the tie-set matrix. 4+6=10

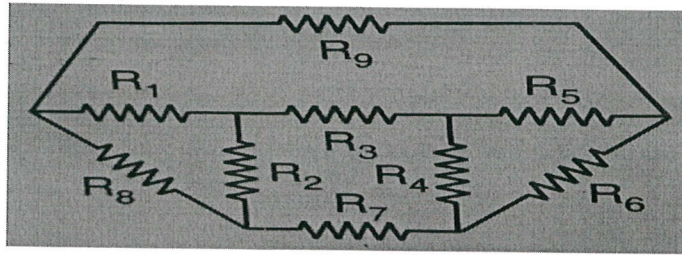


Figure-3

b) The incidence matrix of a network is given by

3+7=10

Nodes	Branches					
	1	2	3	4	5	6
A	-1	+1	+1	0	0	0
B	0	-1	0	-1	+1	0
C	0	0	-1	+1	0	+1
D	+1	0	0	0	-1	-1

Draw the oriented graph. Select a tree and find f-cut set matrix.

4 a) Find the transient responses of (i) series R-L and (ii) series R-C circuit having DC excitation.

5+5=10

b) What is steady state response and transient response? Define (i) Laplace transform and (ii) Fourier transform of a continuous-time function.

4+2+4=10

5 a) What is two-port network? Derive the condition (or result) for parallel interconnection of two 2-port networks.

3+7=10

b) Find the Z and ABCD parameters of the following circuit (Figure-4).

5+5=10

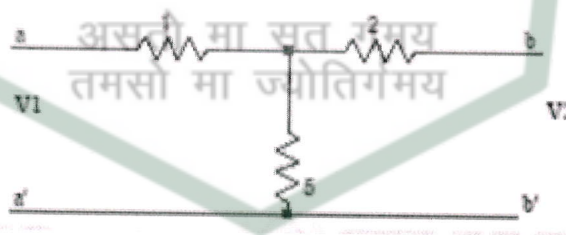


Figure-4

6 a) Draw the equivalent circuit of a 2-port network in terms of (i) Z-parameters and (ii) h-parameters.

5+5=10

b) Write the condition for reciprocity in terms of Z-parameters and T-parameters. Show that the overall transmission parameters matrix for cascaded Two 2-port networks is simply the matrix products of transmission parameters for each individual 2-port network in cascade.

4+6=10
