

2024



ELECTRIC CIRCUITS AND NETWORK

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer **any five** questions.

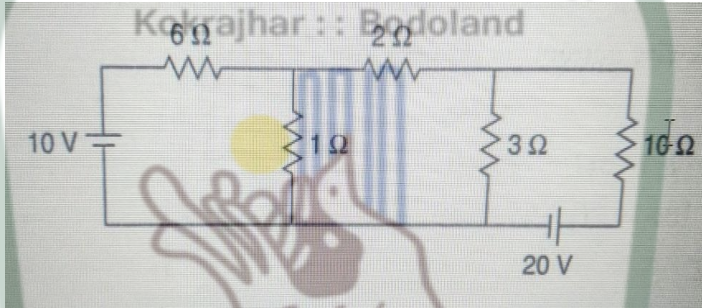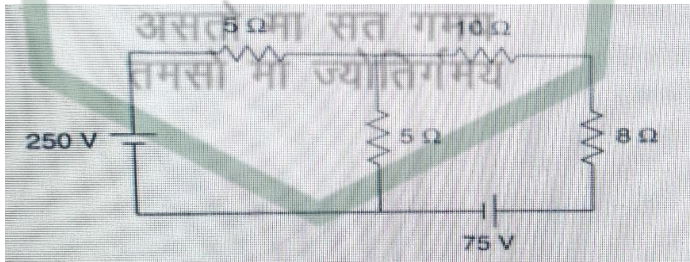1.	a)	Which Kirchhoff's law is used in mesh analysis? In the given circuit diagram, determine the number of junction points and meshes.	1+3=4
		 <p>Figure-1</p>	
	b)	Find the current through 2 Ω resistor as shown in Figure-1 using Mesh analysis.	10
	c)	Find the current through 8 Ω resistor in the network using Thevenin's theorem.	6
		 <p>Figure-2</p>	
2	a)	Explain fundamental cut set matrix with an example.	5
	b)	Find the tie set matrix for the graph shown in Figure-3	7

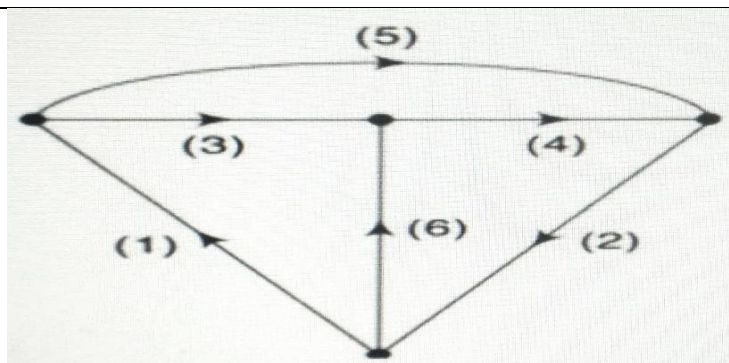


Figure-3

- c) For the network shown in the Figure (4), draw network graph. Selecting elements 1,2 and 3 as the tree elements, obtain basic cut-sets and write cut-set matrix.

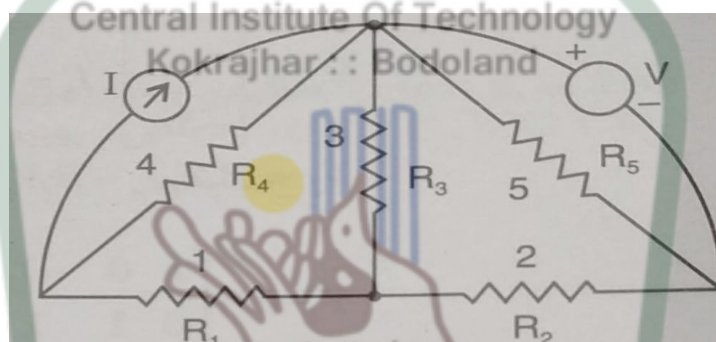


Figure-4

- 3) a) Find the transient responses of series R-L circuit having DC excitation.
b) Define the various transfer functions of a two-port network. Derive the condition (or result) for series-parallel interconnection of two 2-port networks.
- 4) a) Express the Fourier-series coefficients for complex exponential function. Determine the Fourier series coefficients for $x(t)$ as shown in Figure-5.

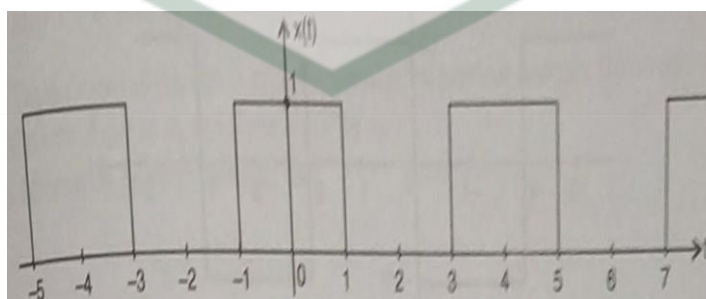


Figure-5

- b) Express Z-parameters in terms of ABCD parameters.
5. a) Find the Z and hybrid (h) parameters of the following circuit (Figure-6).

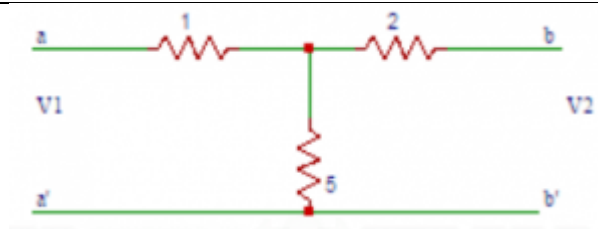


Figure-6

b) Define open circuit and short circuit impedances parameters.

6

6. a) The incidence matrix of a network is given by

6

Nodes	Branches					
	1	2	3	4	5	6
A	-1	+1	+1	0	0	0
B	0	-1	0	-1	+1	0
C	0	0	-1	+1	0	+1
D	+1	0	0	0	-1	-1

Draw the oriented graph.

b) In the circuit given below, find the value of ABCD parameters.

8

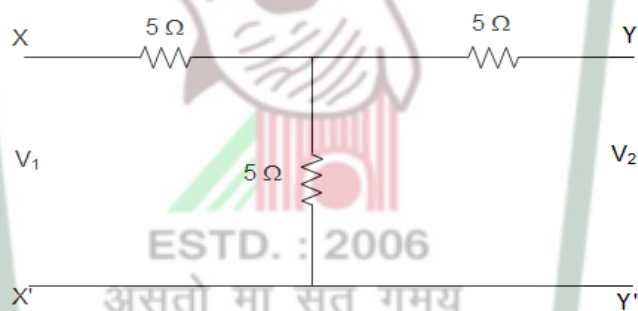


Figure-7

c) Define the following any three terms:

2×3=6

(i) Circuit elements (ii) Branch (iii) Graph (iv) Tree