

Total No. of printed pages = 4

19/6th Sem/DECE 612A

2022

POWER ELECTRONICS

Full Marks – 100


Time – Three hours

The figures in the margin indicate full marks
for the questions.

Answer any *five* questions.

1. (a) Draw the static I-V characteristic of a thyristor. What are the three modes of operation of a thyristor? Discuss each of them briefly. 2+3+5=10
- (b) Explain the two-transistor model of a thyristor. Hence, find an expression for the anode current (I_a) in the thyristor. 3+7=10
2. (a) The given circuit shows a controlled AC-DC converter with R-L load.

[Turn over

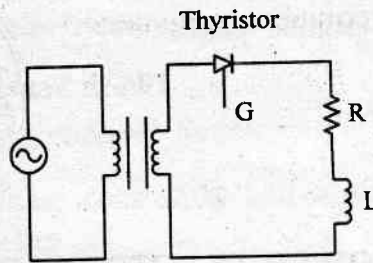


Discuss the operation of the circuit. Why the output current or the output voltage exists when the input voltage becomes negative? Draw the output voltage, output current, and the thyristor voltage. $4+2+4=10$

- (b) Discuss the effect of a free-wheeling diode on the controlled AC-DC converter with R-L load. Explain how the output power factor (pf) can be increased. $5+5=10$
3. (a) Discuss the operation of a single phase full-wave midpoint controlled rectifier with R-L load. Hence draw the output voltage and current. $7+3=10$
- (b) Discuss the evolution of a 3-phase 6-pulse controlled AC-DC converter. Draw the output voltage for such a converter with resistive load. $4+6=10$
4. (a) Discuss the working principle of a shunt regulator. Hence discuss the line regulation for such a regulator. $10+2=12$

- (b) Determine the regulated voltage (V_L), current (I_L), source current (I_s) and the collector current (I_c) from the figure given below :

$$2+2+2+2=8$$

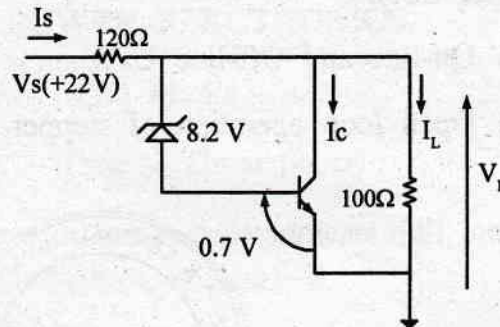

5. (a) Discuss the operation of a full-bridge voltage source inverter and draw the output voltage. Explain the purpose of connecting feedback diodes across the thyristors. $6+2=8$
- (b) With reference to a three phase voltage source inverter with (180°) conduction and resistive load, draw the phase-to-neutral voltage for any two phases with necessary calculations. 12

6. Write short notes on any *two* from the following :
10+10=20

- (a) Step-up chopper circuit
- (b) AC phase control by half-wave AC voltage controller
- (c) On-line and Off-line UPS
- (d) Open loop operation of stepper motor.

