

2021

**FUNDAMENTALS OF ELECTRICAL AND ELECTRONICS
ENGINEERING**

Full Marks: 60

Time: 2 hours

The figures in the margin indicate full marks for the questions.

A. Multiple Choice Questions

1 x 20=20

1. Which of the following is a semiconductor?
 - a. Copper
 - b. Platinum
 - c. Germanium
 - d. Iron
2. The number of valance electrons in silicon are
 - a. 1
 - b. 2
 - c. 3
 - d. 4
3. Which of the following is a pentavalent impurity?
 - a. Aluminum
 - b. Arsenic
 - c. Boron
 - d. Cadmium
4. Bipolar Junction Transistor has how many terminals?
 - a. 1
 - b. 2
 - c. 3
 - d. 4

5. Which layer of BJT is heavily doped?
 - a. Emitter
 - b. Base
 - c. Collector
 - d. Both a and c.
6. In the output characteristics of a Bipolar Junction Transistor, the output current I_c is zero in _____
 - a. active region
 - b. saturation region
 - c. cutoff region
 - d. both b and c.
7. The purpose of using a capacitor in a voltage regulator circuit is to
 - a. rectify the ac voltage.
 - b. filter the ripples.
 - c. regulate the output voltage.
 - d. step down the input voltage.
8. The SI units of potential difference, electric current, electric power and energy are
 - a. Volt, ampere, joule and watt respectively
 - b. Volt, ampere, watt-hr and joule/sec respectively
 - c. Volt, ampere, joule/sec and joule respectively
 - d. None of the above
9. A junction where two or more than two network elements meet is known as a
 - a. node
 - b. branch
 - c. loop
 - d. mesh
10. The period of a wave is
 - a. the same as frequency
 - b. time required to complete one cycle
 - c. expressed in ampere

- d. none of the above
11. The peak value of a sine wave is 200V. It's average value is
- a. 127.4 V
 - b. 141.4 V
 - c. 282.8 V
 - d. 200 V
12. In the complex number $(4+j7)$, 4 is called the _____ component.
- a. real
 - b. imaginary
 - c. in-phase
 - d. quadrature
13. For a frequency of 200Hz, the time-period will be
- a. 0.055 s
 - b. 0.005 s
 - c. 0.0005 s
 - d. 0.5 s
14. V_{th} is found across the _____ terminals of the network
- a. Input
 - b. Output
 - c. Neither input nor output
 - d. either input nor output
15. Least current will flow through
- a. 18 ohm resistor
 - b. 5 ohm resistor
 - c. 10 ohm resistor
 - d. 25 ohm resistor
16. The algebraic sum of voltages around any closed path in a network is equal to
- a. Infinity
 - b. 1
 - c. 0
 - d. Negative polarity

17. All _____ are loops but all _____ are not meshes
- loops, meshes
 - meshes, loops
 - branches, loops
 - nodes, branches
18. An ideal voltage source has
- Infinite internal resistance
 - 2 ohm internal resistance
 - Zero internal resistance
 - Very small internal resistance
19. Kirchhoff's voltage law is applied
- At a junction only
 - Across a branch only
 - In Thevenin's loop
 - In a closed electric path
20. SI unit of resistance is
- $\Omega\text{-m}$
 - $\Omega\text{-cm}$
 - Ω^{-1}
 - Ω

B. Very Short Question


2*6=12

- What do you mean by extrinsic and intrinsic semiconductor?
- What will happen to PN junction diode when it is forward bias?
- Two resistors 3Ω and 6Ω are connected in parallel and this combination is connected with 22V DC supply. Estimate the total power loss in this circuit.
- An ideal voltage source of 18V is in series with a 10Ω resistor. Obtain it's current source equivalent.
- An AC voltage wave is represented by ' $v = 120 \text{ Sin } (314.t)$ '. Find the maximum value and frequency.
- A sinusoidal AC current wave makes 120 cycles per minute. What is its frequency?


C Short Question

4*7=28

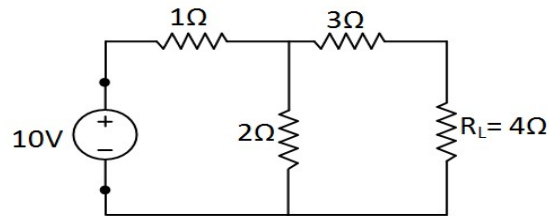1. How a Bipolar Junction Transistor is operated in CB or CE configuration? Explain with a diagram. Also, draw the output characteristics for the particular configuration.
2. Describe the working of a half wave rectifier using suitable diagrams? What do you mean by ripple factor of a rectifier?
3. What is the function of filter circuit in a voltage regulator? Explain with a diagram.
4. Calculate V_{th} for the given circuit. $R_L = 4\Omega$ is given as the load resistance.



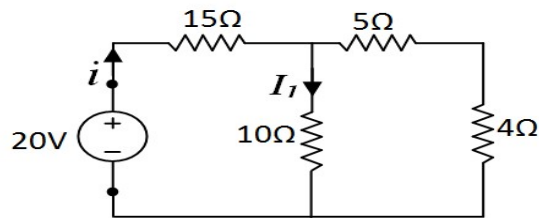5. In the circuit shown below, calculate circuit current ' i ' and branch current ' I_1 '.



6. Given, $A = (4-j2)$ and $B = (1-j5)$. Perform the operation $A.B$ and represent the result in polar form.
7. Define the following terms associated with sinusoidal AC quantities –
Amplitude, frequency, time period and average value