

Total number of printed pages = 4

19/2nd Sem/DEE 203



2022

**FUNDAMENTALS OF ELECTRICAL AND
ELECTRONICS ENGINEERING**

Full Marks : 100

Time : Three hours


The figures in the margin indicate full marks
for the questions.

Answer any *five* questions.


1. (a) Write notes on intrinsic semiconductor and extrinsic semiconductor. 5
- (b) Write down the distinction between p-type and n-type semiconductor. 5
- (c) What is a P-N junction? Write a note on formation of P-N junction. 7
- (d) Write down the applications of P-N junction diode. 3
2. (a) How does current flows in P-N junction diode in forward and reverse bias? Draw a I-V characteristic for it. 10

[Turn over

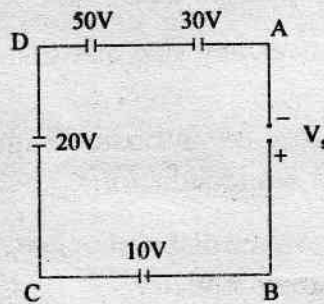
- (b) What is Bipolar Junction Transistor (BJT).
Make symbols of PNP and NPN BJT. 5
- (c) Write a note on construction of PNP and NPN
bipolar junction transistor. 5
3. (a) Write a note on different types of biasing
system of bipolar transistor. 5
- (b) Write down the Kirchoff's voltage law. 5
- (c) Calculate the voltage V_s across the open
switch in the given circuit? 10



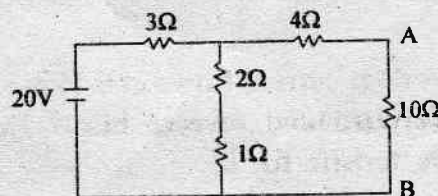4. (a) Find the Thevenin equivalent circuit between
the terminal A and B in the Figure shown
below also find the load current. 5



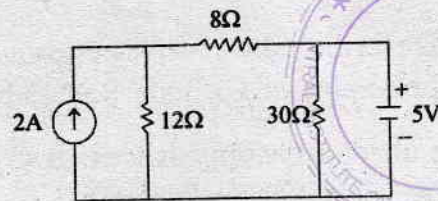- (b) Find the current across 8Ω resistor using superposition theorem in the circuit shown below : 5



- (c) Explain the different types of energy sources and differentiate between conventional as well as non-conventional source of energy. 10
5. (a) A series AC circuit contains a resistor, an inductor of 220 mH , a capacitor of $4.70\ \mu\text{F}$, and a generator with $\Delta V_{\text{max}} = 240\text{ V}$ operating at 50.0 Hz . The maximum current in the circuit is 200 mA .
- Calculate the inductive reactance.
 - Calculate the capacitive reactance.
 - Calculate the impedance.
 - Calculate the phase angle between the current and the generator voltage. 10

- (b) What is Full wave rectifier ? Draw and explain the working principle of Full wave rectifier. 5
- (c) Write note on Peak Inversion Voltage. 5
6. (a) Describe the construction and working principles of Cathode Ray Tube (CRT). 10
- (b) Calculate the impedance in R-C parallel circuit by using Phasor Diagram. 5
- (c) Explain the advantages of full-wave rectifier over Half-wave rectifier as well as compare their efficiencies. 5

