

Total number of printed pages: 02

Programme(D)/2nd Semester/ DEE203

2023



Fundamental of Electrical & Electronics Engineering

Full Mark: 100

Time: Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

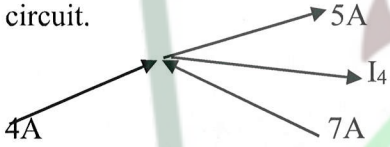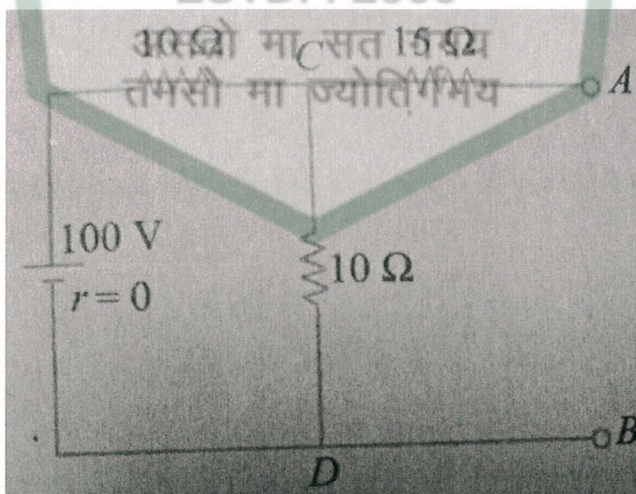1.	a)	Differentiate between conventional and non-conventional sources of energy.	10
	b)	(i) What is the main source of energy in India? (ii) Can any source of energy be pollution free? (iii) What are advantages and disadvantages of the wind power?	3+3+4
2.	a)	Using Kirchoff's current law, find the value of I_4 in the following given circuit. 	5
	b)	Using Norton's theorem, find the constant current equivalent of the circuit. 	15
3.	a)	A series RLC circuit contains the following components: $R=150\ \Omega$, $L=0.25\ \text{H}$, $C=2\ \mu\text{F}$, and a source with 210 V operating at 50 Hz. Find the (i) Inductive reactance in the circuit	$4 \times 5 = 20$

		(ii) Capacitive Reactance in the circuit (iii) Impedance in the circuit (iv) Maximum current in the circuit (v) Phase angle between the current and source voltage	
4.	a)	Write the difference between intrinsic and extrinsic semiconductor.	5
	b)	Write a short note on p-type and n-type semiconductor	5
	c)	Discuss the forward and reverse bias of the P-N junction diode and its V-I characteristics.	10
5.	a)	Make the symbol of: (i) p-n junction diode in forward and reverse bias (ii) Zener diode (iii) Varactor diode (iv) Tunnel diode (v) PIN diode	2×5=10
	b)	Write a short note on Tunnel diode and Zener diode	5+5=10
6.	a)	What is a Bipolar junction transistor (BJT)? Discuss about the PNP and NPN BJT.	10
	b)	Write down the operation of PNP and NPN bipolar junction transistor.	10
7.	a)	What is rectifier? Write down a short note on full wave rectifier and its working principle.	10
	b)	Discuss the construction and features of the cathode ray oscilloscope	10