

Total number of printed pages: 02
Diploma/2nd /DEE203

2022

**FUNDAMENTALS OF ELECTRICAL & ELECTRONICS
ENGINEERING**

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

1.	a)	Draw the schematic diagram of general power system.	5
	b)	Write a short note on overhead power transmission sub-station.	5
	c)	What is a P-N junction? Write a note on formation of P-N junction.	10
2.	a)	What is bipolar junction transistor (BJT). Make symbol of PNP and NPN BJT.	8
	b)	How does current flows in P-N junction diode in forward and reverse bias? Draw a I-V characteristic for it.	7
	c)	Write a note on construction of PNP and NPN bipolar junction transistor.	5
3.	a)	Write down a note on linear and non-linear circuits	5
	b)	Write a note on different types of biasing system of bipolar transistor.	5
	c)	Find the unknown voltage V_1 in the circuit in the following figure (B)	10

4.	a)	<p>Find the Thevenin equivalent circuit between the terminal A and B in the Figure shown below also find the load current.</p>	5
	b)	<p>Find the current across 8Ω register using superposition theorem in the circuit shown below</p>	5
	c)	<p>Explain different types of energy sources and Differentiate between conventional as well as non-conventional source of energy.</p>	10
5.	a)	<p>A series AC circuit contains a resistor, an inductor of 220 mH, a capacitor of $4.70\text{ }\mu\text{F}$, and a generator with $\Delta V_{\text{max}}=240\text{ V}$ operating at 50.0 Hz. The maximum current in the circuit is 200 mA.</p> <p>(i) Calculate the inductive reactance. (ii) Calculate the capacitive reactance. (iii) Calculate the impedance. (iv) Calculate the phase angle between the current and the generator voltage.</p>	10
	b)	<p>What is Full wave rectifier? Draw and explain the working principle of Full wave rectifier.</p>	5
	c)	<p>Write notes on Peak Inversion Voltage</p>	5
6.	a)	<p>Can any source of energy be pollution free? Biomass energy is..... (renewable/non-renewable sources of energy).</p>	7
	b)	<p>Write short note on active and passive devices</p>	5
	c)	<p>Explain the advantages of full wave rectifier over Half wave rectifier as well as compare their efficiencies.</p>	8