

Total No. of printed pages = 3

19/5th Sem/DEE504

2021

**POWER ELECTRONICS**

Full Marks – 100

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer all *five* questions.

1. (a) What do you mean by the term “junction” in semiconductor devices? 2
- (b) What is the function of the drift region found in a power diode? Briefly explain how it affects the characteristic of a diode. 4
- (c) Draw the I-V characteristics of a power BJT and define the important points in the curve. 5
- (d) Draw the structure of a power MOSFET clearly showing the parasitic BJT and parasitic diode in it. 5

[Turn over

- (e) State four differences between BJT and MOSFET. 4
2. (a) Differentiate between controllable and semi-controllable switches with two examples of each type. 3
- (b) Explain the different modes of operation of an SCR with the help of its static I-V characteristics. 5
- (c) Describe the method of line commutation to turn-off a thyristor. 5
- (d) With the help of voltage and current waveforms, explain the working of a single phase half-wave circuit with R-L load. 7
3. (a) Describe the various methods that can be applied to turn-on a thyristor. 8
- (b) What is a firing circuit? Draw the circuit diagram of Resistance firing circuit of a thyristor and briefly explain its working. 6
- (c) Describe the structure and working of a triac. 6



4. (a) What is the main function of a DC chopper ?  
Deduce the output voltage expression for an elementary chopper circuit. 5
- (b) Describe the various control strategies for varying the duty cycle of chopper. 6
- (c) What is an inverter ? Draw the circuit diagram of a single phase full-bridge inverter and explain its working. 7
- (d) What is a cycloconverter ? 2
5. Write short notes on any *four* : 5×4=20
- (i) GTO
  - (ii) UJT
  - (iii) IGBT
  - (iv) Load commutation technique
  - (v) BJT as a switch
  - (vi) Two transistor model of thyristor.

