

Total No. of printed pages = 7

19/3rd Sem/DIE301



2021

ELECTRICAL CIRCUITS AND NETWORKS

Full Marks-100

Time-Three hours

The figures in the margin indicate full marks for the questions.

Answer any *five* questions.

1. (a) Determine the equivalent resistance between A and B (Figure 1). 6

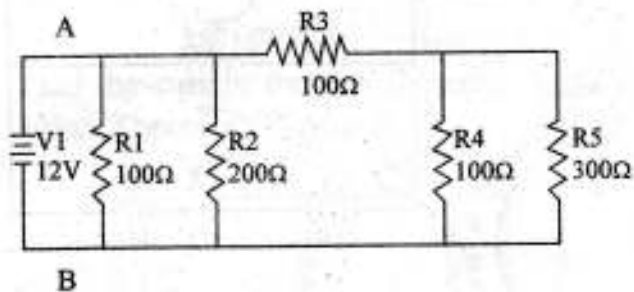


Figure 1

[Turn over

- (b) Determine the current through resistor R_1 using current divide rule (Figure 2). 6

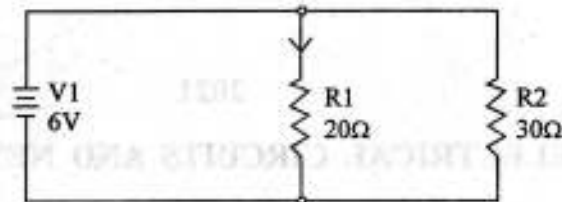


Figure 2

- (c) State and explain Kirchhoff's voltage law and Kirchhoff's current law using suitable circuit diagrams. 8
2. (a) Using mesh analysis, determine the current through resistor R_1 (Figure 3) 8

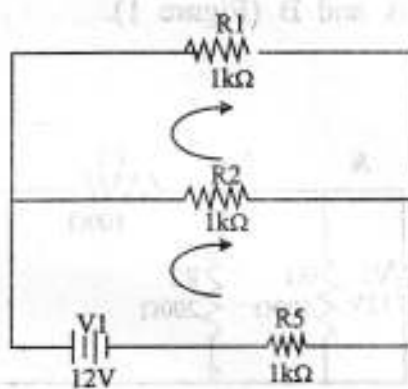


Figure 3



- (b) Determine voltage V_a using nodal analysis (Figure 4). 6

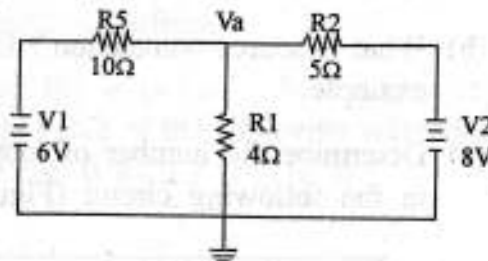


Figure 4

- (c) Explain Maximum Power Transfer Theorem with a suitable example. 6
3. (a) Find the current through resistance R_3 using Thevenin's Theorem (Figure 5). 10

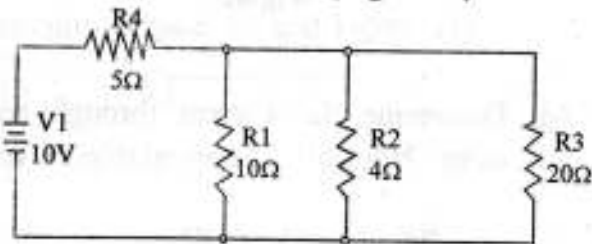


Figure 5

- (b) Find the current through R_1 using Superposition Theorem (Figure 6). 10

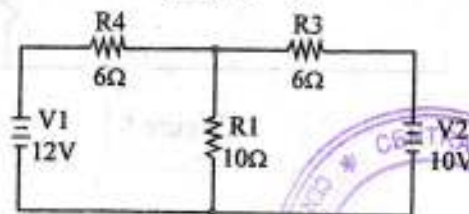


Figure 6



4. (a) What are independent and dependent sources ?
Draw their symbols. 4
- (b) What is source conversion ? Explain with an example. 4
- (c) Determine the number of loops and meshes in the following circuit (Figure 7). 2

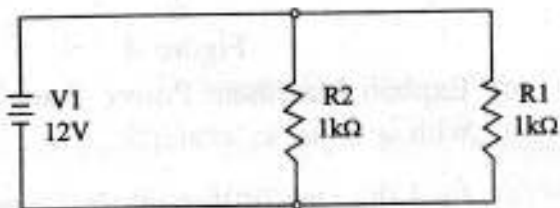


Figure 7

- (d) Determine the current through resistor R_5 using Norton's Theorem (Figure 8). 10

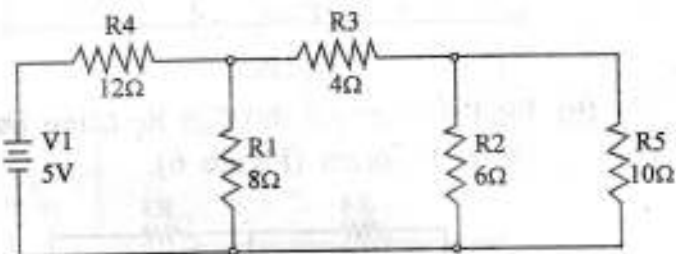



Figure 8



18/19/3rd Sem/DIE301

(4)

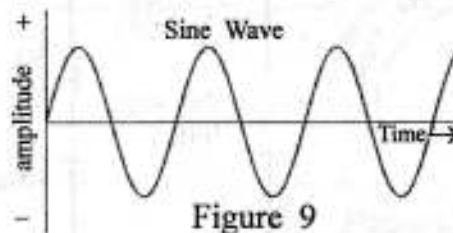5. (a) What are instantaneous value, maximum value, frequency and time period of a sinusoidal waveform? 6
- (b) Deduce the expression for rms value and average value of the following waveform for the period 0 to 2? (Figure 9) 10



- (c) Draw the phasor diagram of the following circuits (Figure 10 and Figure 11). 4

(i)



Figure 10

(ii)

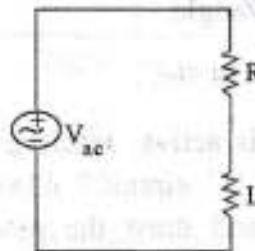


Figure 11

6. (a) Two impedances $Z_1 = 2 + j6$ ohm and $Z_2 = 4 - j10$ ohm are connected in series in a circuit. Determine the resultant impedance in the polar form. 5
- (b) A series RC circuit is shown below: 10



Figure 12

Determine the following from the circuit (Figure 12):

- (i) Capacitive reactance X_c .
 - (ii) Impedance Z_t .
 - (iii) RMS Value of current.
 - (iv) Phase angle
 - (v) Power factor.
- (c) What is active, reactive and apparent power in an AC circuit? Also write their expressions and draw the power triangle. 5

7. (a) How an AC waveform is generated and represented in phasor diagram? Explain. 5
- (b) Determine the impedance and current of the circuit shown in figure 13. The supply frequency is 50 Hz. 5

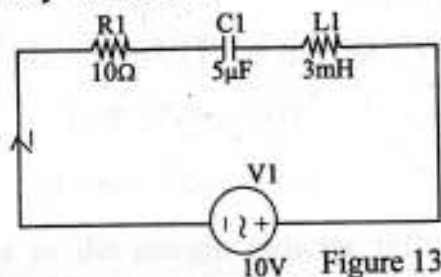


Figure 13

- (c) Two impedances $Z_1 = 10 + j6$ and $Z_2 = 6 + j8$ are connected in parallel as shown in figure below (Figure 14) : 10

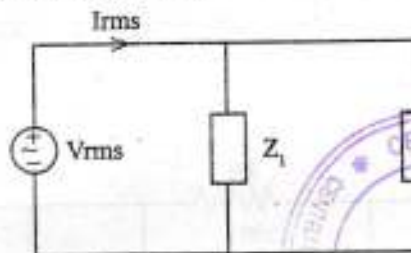


Figure 14

Given $I_{rms} = 10$ A. Find :

- (i) V_{rms} ,
- (ii) Phase angle and power factor of the circuit,
- (iii) Power consumed by Z_1 and Z_2 .