

2022



**ELECTRICAL CIRCUITS AND NETWORKS**



Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.
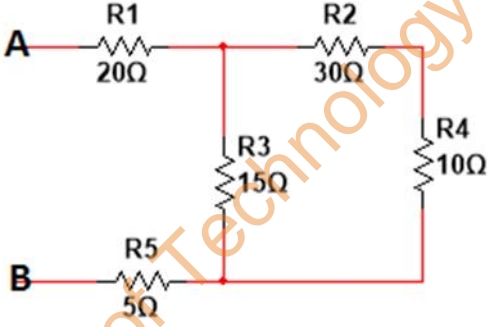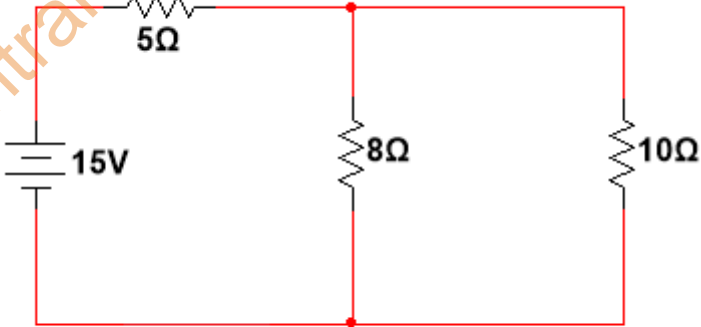
<p>1. a)</p>	<p>Determine the equivalent resistance between terminals A and B in figure 1.</p>  <p style="text-align: center;">Figure 1</p>	<p>7</p>
<p>b)</p>	<p>Using current divide rule , determine the current through 8Ω and 10Ω resistors in figure 2.</p>  <p style="text-align: center;">Figure 2</p>	<p>7</p>

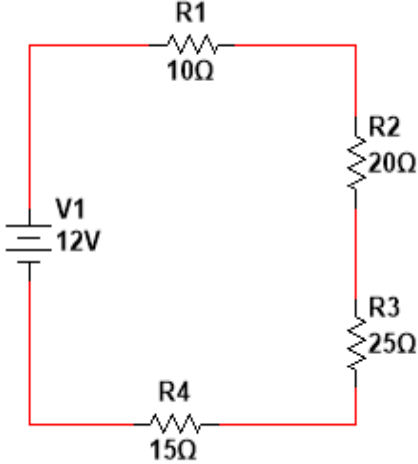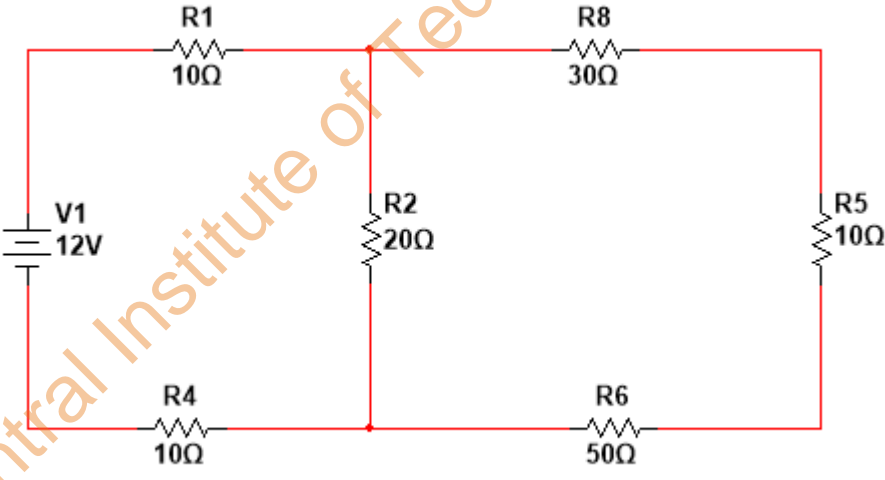	<p>c) Determine the voltage across R3 and R4 in figure 3 using voltage divide rule.</p> <div style="text-align: center;">  </div> <p style="text-align: center;">Figure 3</p>	6
2.	<p>a) State Kirchoff's voltage law and Kirchoff's current law.</p>	4
	<p>b) Determine the current through 20 Ω resistor in figure 4 using KVL method or mesh analysis.</p> <div style="text-align: center;">  </div> <p style="text-align: center;">Figure 4</p>	10
	<p>c) Explain Thevenin's Theorem using a suitable circuit diagram.</p>	6
3.	<p>a) Determine the currents through 50Ω, 30Ω and 20Ω resistances in figure 5 using nodal analysis.</p>	7

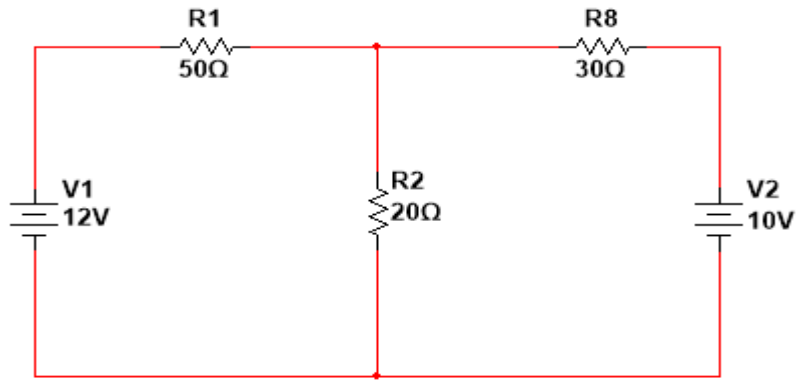


Figure 5

- b) What do you mean by node, branch, loop and mesh in a circuit? Determine the number of branches and meshes in the following circuit (figure 6)

7

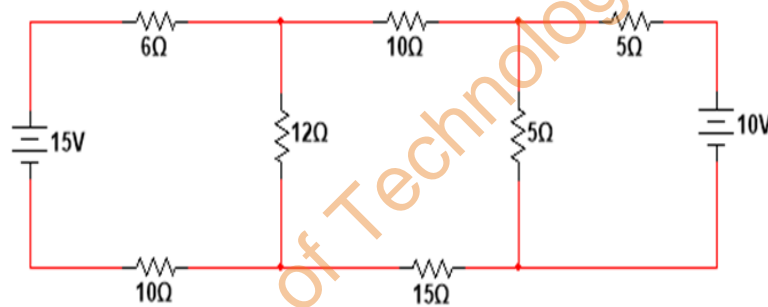


Figure 6

- c) What is independent and dependent sources? Show the symbols of independent and dependent voltage and current sources.

6

4. a) Determine the current through  $10\Omega$  resistor in figure 7 using Norton's Theorem.

10

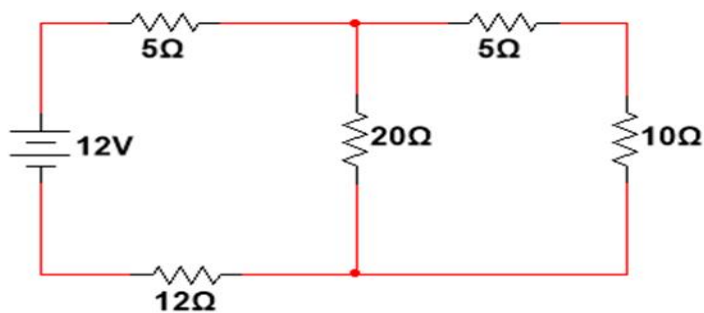
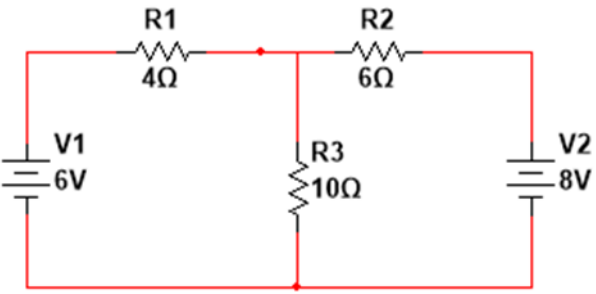
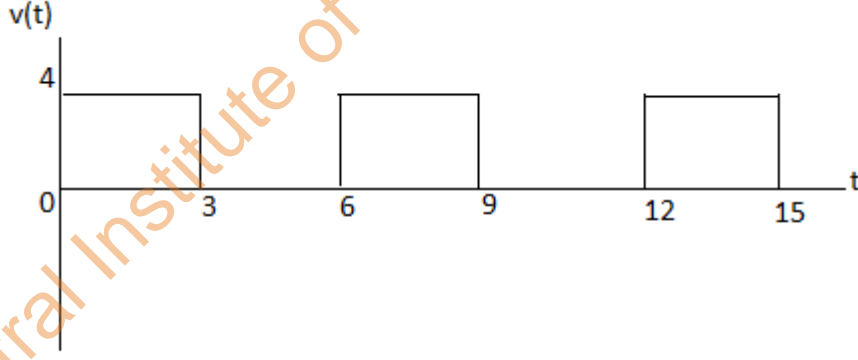
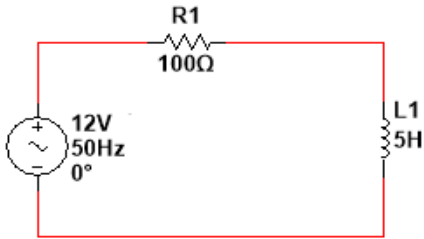
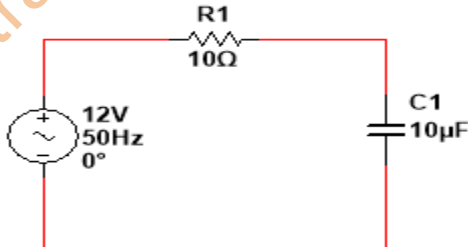


Figure 7

	b)	<p>Determine current through <math>10\Omega</math> resistor in figure 8 using Superposition Theorem.</p>  <p style="text-align: center;">Figure 8</p>	10
5.	a)	<p>The instantaneous value of a sinusoidal waveform is given as <math>v(t)=100\sin 100\pi t</math>.</p> <p>Determine</p> <ol style="list-style-type: none"> <li>(i) RMS value of the waveform</li> <li>(ii) Average value of the waveform.</li> <li>(iii) Frequency of the waveform</li> </ol>	6
	b)	<p>Determine the average value and RMS value of the following waveform (figure 9):</p>  <p style="text-align: center;">Figure 9</p>	10
	c)	<p>A voltage waveform is represented in polar form as <math>15\angle 30^\circ</math>. Represent it in</p> <ol style="list-style-type: none"> <li>(i) Trigonometric form</li> <li>(ii) Rectangular form</li> </ol>	4
6	a)	<p>A RL circuit with source voltage <math>12\text{V(RMS)}</math> at <math>50\text{Hz}</math> is given below (figure 10):</p>	10

	<div style="text-align: center;">  </div> <p style="text-align: center;">Figure 10</p> <p>Determine:</p> <ol style="list-style-type: none"> <li>(i) Impedance of the circuit.</li> <li>(ii) RMS value of current.</li> <li>(iii) Phase angle.</li> <li>(iv) Power factor.</li> <li>(v) Active and reactive power of the circuit.</li> </ol>	
	<p>b) Discuss the behaviour of a circuit, when an AC voltage is connected to the following:</p> <ol style="list-style-type: none"> <li>(i) Resistance.</li> <li>(ii) Inductance.</li> <li>(iii) Series RL circuit.</li> <li>(iv) Parallel circuits.</li> </ol>	10
7	<p>a) Discuss any two of the following with suitable examples</p> <ol style="list-style-type: none"> <li>(i) Source conversion</li> <li>(ii) Norton's Theorem</li> <li>(iii) Current divide rule</li> </ol>	5x2=10
	<p>b) A RC circuit with source voltage 12 V (maximum) at 50Hz is given below (Figure 11):</p> <div style="text-align: center;">  </div> <p style="text-align: center;">Figure 11</p> <p>Draw the phasor diagram of the circuit. Also determine the active and reactive power of the circuit.</p>	10

Central Institute of Technology KOkrajhar