

2023

ELECTRICAL CIRCUITS AND NETWORKS


Full Marks : 100

Time : Three hours


The figures in the margin indicate full marks for the questions.


Answer any five questions.

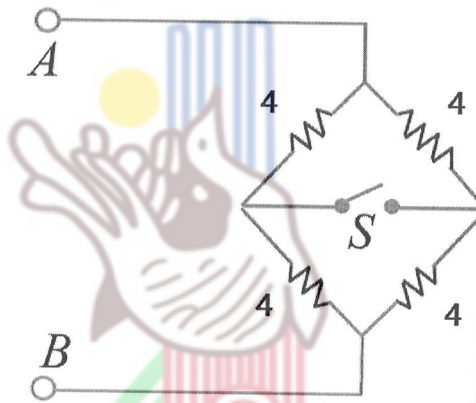1. a) In the circuit below, find the resistance between terminals A and B when switch is: (a) open and (b) closed. 2+2



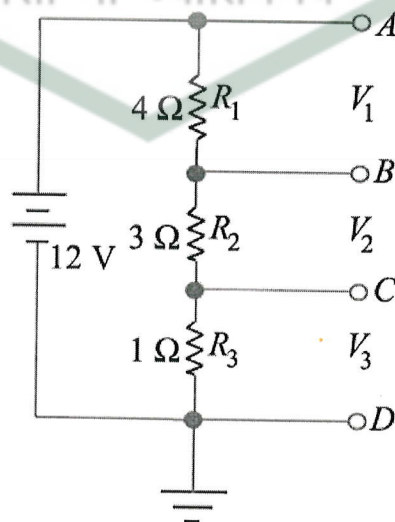
- b) Find the values of different voltages (V_1 , V_2 and V_3) with the help of voltage divider rule. 4



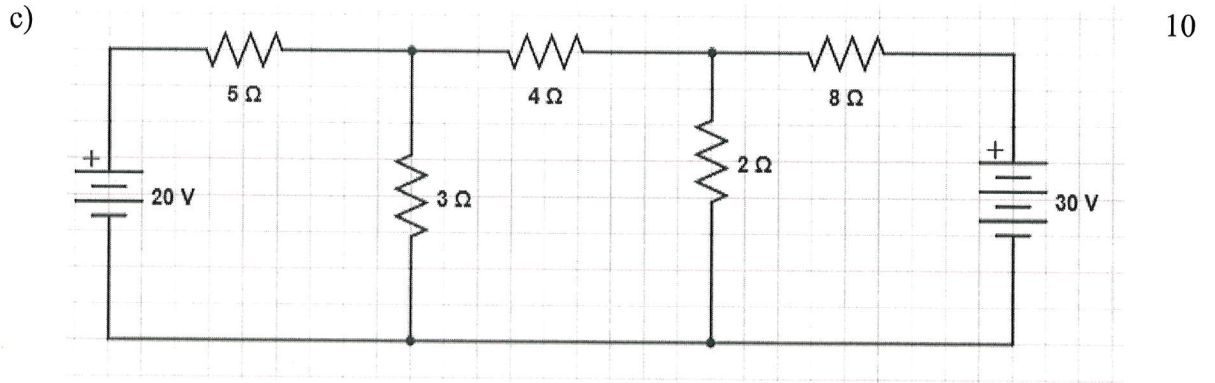


Find the current flowing through the 4Ω resistance using Maxwell's Loop Current Method.

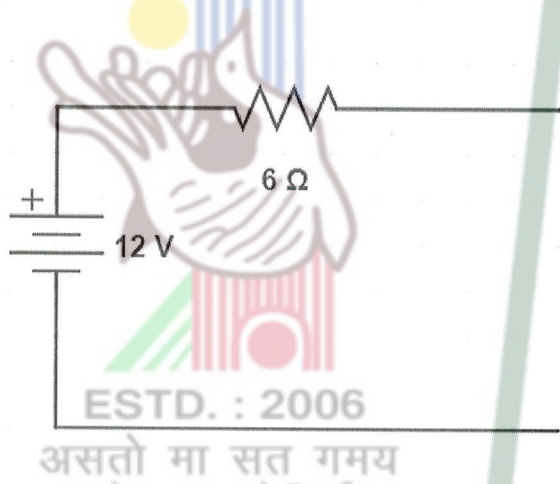
- d) State the Ohm's Law. 2
2. a) Using Node voltage method, find the current in the 4Ω resistance for the network shown in Question No. 1(c). 10
- b) Convert the voltage source of Fig below into an equivalent current source. 5



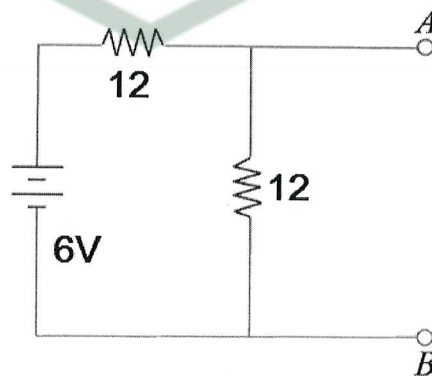- c) Determine the Norton equivalent circuits between terminals A and B for the circuit below. 5



3. a)

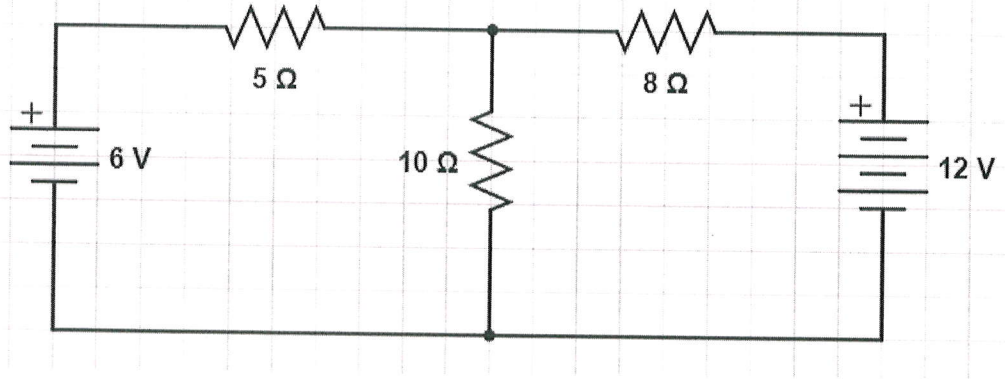

10


By using Superposition Theorem, find the current in resistance $10\ \Omega$ shown in Figure above.

b) Apply Thevenin's theorem to calculate the current through the $10\ \Omega$ resistor of the circuit given in Question No. 3(a)

10


4. a) Using star to delta conversion, compute the network resistance measured between terminals A and B.

10

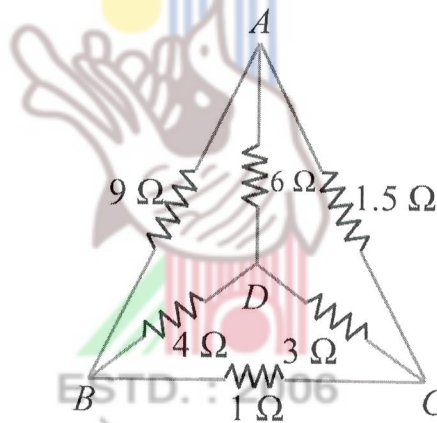

b) Use Millman's theorem, to find the current flowing through the $5\ \Omega$ load resistance R_L .

10

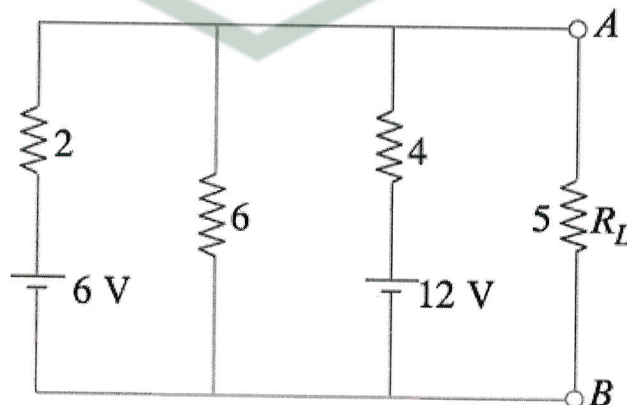

5. a) State and prove the Maximum Power Transfer Theorem as applicable to dc networks.

10

- b) An alternating current of frequency 50 Hz has a maximum value of 100 A. Write down the equation for its instantaneous value. 4
- c) A 50- μ F capacitor is connected across a 230-V, 50-Hz supply. Calculate (a) the reactance offered by the capacitor (b) the maximum current and (c) the r.m.s. value of the current drawn by the capacitor. 6
6. Write short notes on : 5x4
- Form Factor
 - Resonance
 - Power Factor
 - Power Triangle
7. a) In a series circuit containing pure resistance and a pure inductance, the current and the voltage are expressed as : 10
- $i(t) = 6 \sin(314t + 2\pi/3)$ and $v(t) = 18 \sin(314t + 5\pi/6)$
- What is the impedance of the circuit?
 - What is the value of the resistance?
 - What is the inductance in henry?
 - What is the power factor?
- b) A resistance of 20 Ω , an inductance of 0.2 H and a capacitance of 100 μ F are connected in series across 220-V, 50-Hz mains. Determine the followings (a) impedance (b) current (c) voltage across R, L and C (d) power in watts and VA (e) p.f. and angle of lag. 10