

Total number of printed pages: 6

D/3rd Semester/DIE301

2024

ELECTRICAL CIRCUITS AND NETWORKS


Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer *any five* questions.

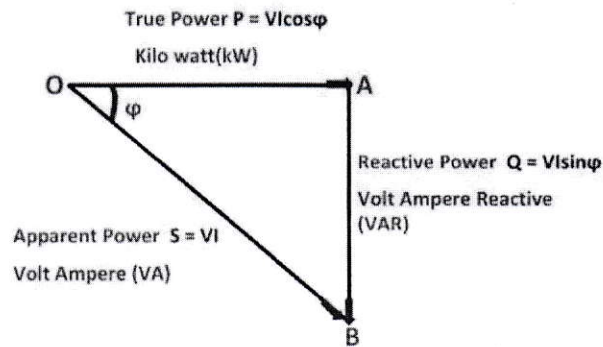
1. a) Choose the correct answer: 10
- i) A circuit contains two un-equal resistances in parallel
 - a) Current is same in both
 - b) Large current flows in larger resistor
 - c) Potential difference across each is same
 - d) Smaller resistance has smaller conductance.
 - ii) What is the total capacitance when two capacitors C1 and C2 are connected in series?
 - a) $(C1+C2)/C1C2$
 - b) $1/C1+1/C2$
 - c) $C1C2/(C1+C2)$
 - d) $C1+C2$
 - iii) The value of a given waveform at any instant time is termed as _____
 - a) Waveform
 - b) Instantaneous value
 - c) Cycle
 - d) Period
 - iv) An Inductor works as a _____ circuit for DC supply.
 - a) Open
 - b) Short
 - c) Polar
 - d) Non-polar
 - v) **Norton**'s equivalent circuit consists of a
 - a) Voltage source in series with a resistor
 - b) Current source in parallel with a resistor
 - c) Voltage source in parallel with a resistor
 - d) Current source in series with a resistor
 - vi) The relationship among True(P), Apparent(S) and Reactive Power(Q) can be expressed as



- a) $S = P + jQ$
 b) $S^2 = P^2 + Q^2$
 c) $S = \sqrt{P^2 + Q^2}$
 d) All of these
- vii) Power Factor is defined as
- The cosine of angle between the voltage and current phasor
 - The ratio of active power and apparent power
 - Both a) and b)
 - None of these
- viii) In superposition theorem, when we consider the effect of one voltage source, all the other voltage sources are
- Shorted
 - Opened
 - Removed
 - Undisturbed
- ix) What happens to the current in the series circuit if the resistance is halved ?
- It becomes half its original value
 - It becomes double its original value
 - It becomes zero
 - It becomes infinity
- x) Kilowatt-hour(kWh) is a unit of
- Current
 - Power
 - Energy
 - Resistance


- b) Find the total resistance across the points "a" and "c".

4

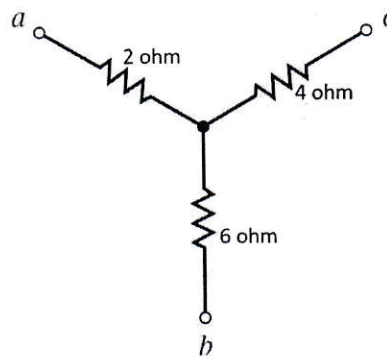

- c) Convert the following voltage source into its corresponding current

5

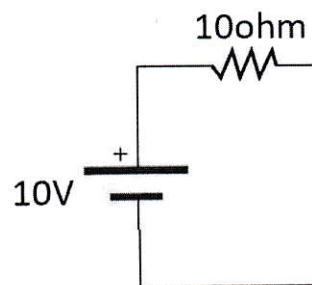


- d) State the Ohm's Law.

1

2. a) Using Thevenin's Theorem find the value of current flowing through 20 ohm resistance.


7

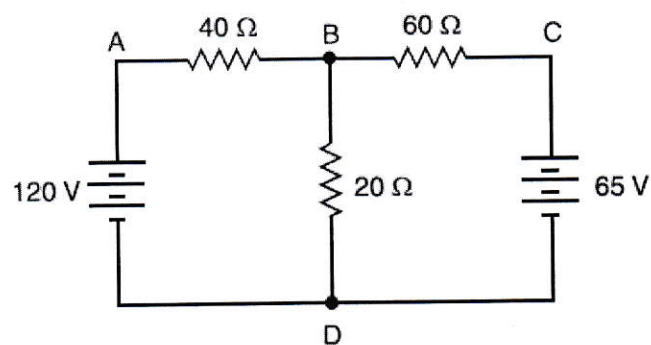

- b) By using Superposition Theorem, find the current in resistance 20 Ω shown in Figure above of question Q2(a).

8

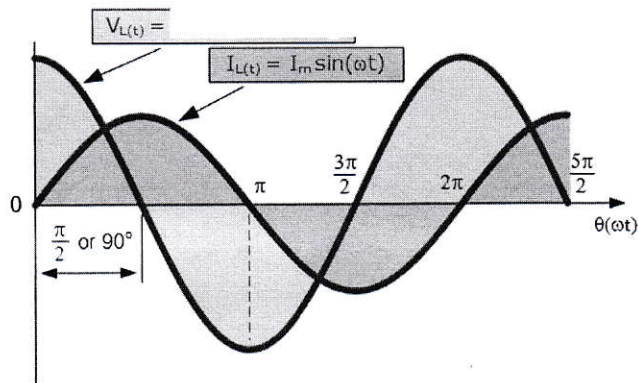c) Write the expression of voltage as displayed in the plot below: 5



3. a) State and prove the Maximum Power Transfer Theorem as applicable to dc networks. 10


b) State "TRUE" or "FALSE". 5

- i) When a short-circuit takes place, the fuse wire melts and breaks the circuit.
- ii) A resistor is a device that controls current in electric circuits.
- iii) Maximum power is transferred if load resistance is equal to internal resistance of the source.
- iv) An ideal voltage source has zero internal resistance.
- v) A real voltage source can be converted to an equivalent real current source and vice-versa.


c) Match the resistor values in column A with the correct colour coding from column B. 5

column A	column B
110 Ω	Red-red-red
5.5 M Ω	Brown-brown-brown
440 K Ω	Violet-violet-violet
2.2 K Ω	Yellow-yellow-yellow
770 M Ω	Green-green-green

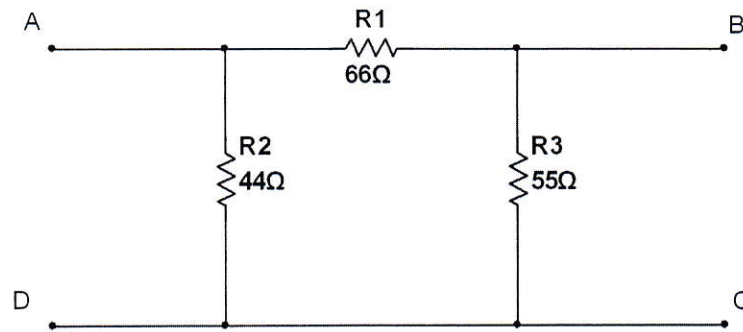4. a) Convert the following delta to its equivalent star connection. 10



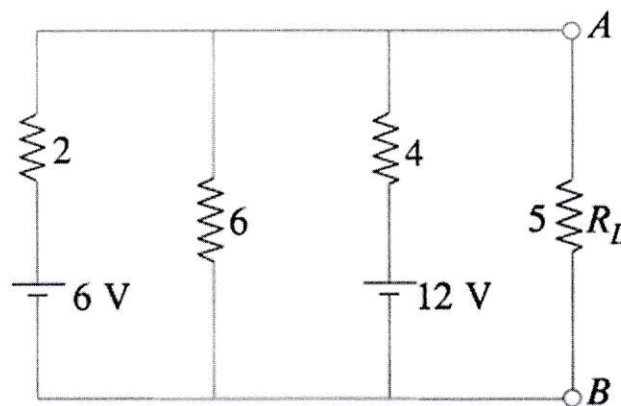- b) Use Millman's theorem, to find the current flowing through the 5 Ω load resistance R_L . 10



5. a) A 50- μ F capacitor is connected across a 230-V, 50-Hz supply. Calculate the reactance offered by the capacitor and the maximum current. 6
- b) An alternating current of frequency 60 Hz has a maximum value of 150 A. Write down the equation for its instantaneous value. 4
- c) A 60-Hz voltage of 115 V (r.m.s.) is impressed on a 100 Ω resistance: (i) Write the time equations for the voltage and the resulting current. Let the zero point of the voltage wave be at $t = 0$ (ii) Show the voltage and current on a time diagram. (iii) Show the voltage and current on a phasor diagram. 10
6. Write short notes on : 5x4
- Form Factor
 - Resonance
 - Power Factor
 - Power Triangle
7. a) In a series circuit containing pure resistance and a pure inductance, the current and the voltage are expressed as :

$$i(t) = 12 \sin(314t + \pi/6) \text{ and } v(t) = 12 \sin(314t + \pi/2)$$

- (a) What is the impedance of the circuit?
 - (b) What is the value of the resistance?
 - (c) What is the inductance in henry?
 - (d) What is the power factor?
- b) A resistance of $12\ \Omega$, an inductance of $0.5\ \text{H}$ and a capacitance of $50\ \mu\text{F}$ are connected in series across 220-V , 50-Hz mains. Determine the followings (a) impedance (b) current (c) voltage across R, L and C (d) power in watts and VA (e) p.f. and angle of lag. 10
