CENTRAL INSTITUTE OF TECHNOLOGY KOKRAJHAR (Deemed to be University) KOKRAJHAR :: BTR :: ASSAM :: 783370 **END – SEMESTER EXAMINATION DIPLOMA**

Semester: 3rd Session: July-December, 2024 Time: 3Hrs. Full Marks: 100 Course Code: DIE 301 Course Title: Electrical Circuits & Networks

QUESTION NO. 1 ISCOMPULSORY AND ANSWER ANY FOUR (4) FROM THE REST

01:

Match the following: *a*)

Column-A	Column-B
Effective value of an alternating quantity referred to as	90^{0}
In a pure capacitive circuit, the current leads the voltage	unknown resistance
by	
The phase difference between voltage and current in a	rotating vector
pure resistive circuit	
The Wheatstone bridge is used to measure	rms value
In phasor representation, a sinusoidal quantity is	0^0
represented as	

b) State **True** or **False**. If false, write the **correct statement**.

- In a parallel circuit, the total resistance is always higher than the resistance of the i) individual components.
- ii) According to Kirchhoff's Voltage Law (KVL), the total sum of the voltage around a closed circuit loop is equal to zero.
- The voltage divider circuit can be used to obtain a lower voltage from a higher voltage iii) source.
- The peak value of a sinusoidal waveform is always equal to its average value. iv)
- v) Phase shift refers to the horizontal shift of a waveform on a time axis, measured in degrees or radians.
- Fill in the blanks: **c**)
- the blanks: In the context of alternating quantities, what does the term 'frequency' refer to _____ i) [time taken to complete one full cycle/ number of cycles completed per second/ phase angle between current and voltage]
 - The 'effective' or 'RMS' value of an alternating current waveform is defined as____ ii) [square root of the mean of the squares of instantaneous values/ sum of instantaneous values/ peak value divided by 21
 - iii) In a pure resistive circuit [circuit does not consume power/ Voltage and current are in phase/ only inductive *reactance is present*]
 - _____ represents the total impedance. iv) In a series RLC circuit, ____

[sum of resistances only/ $Z = \sqrt{R^2 + (X_L - X_C)^2}$ / difference between peak and RMS values]

- v) In terms of power in AC circuits, the 'power triangle' represent_ [sum of powers in parallel circuits/ phase relationship between current and voltage/ relationship between real power, reactive power, and apparent power]
- Convert the voltage source of figure below into an equivalent current source d)

5

5





a) Use Millman's theorem, to find the voltage across 30Ω resistance:



b) Calculate the value of **R** which will absorb maximum power from the circuit below.



Q3:

a) The maximum values of the alternating voltage and current are 400 V and 20 A respectively in a circuit connected to 50 Hz supply and these quantities are sinusoidal. The instantaneous values of the voltage and current are 295 V and 12 A respectively at t = 0 both increasing positively.

Write down the expression for voltage and current at time t.

b) Through a coil of inductance 1 Henry, a current of the wave-form shown in the figure below is flowing. Sketch the wave form of the voltage across the inductance and calculate the r.m.s. value of the voltage.

2

10

8

8



c) State and explain the KCL & KVL.

Q4:

- a) A 50-Hz voltage of 115 V (r.m.s.) is impressed on a 100 ohm resistance :
 - (i) Write the time equations for the voltage and the resulting current. Let the zero point of the voltage wave be at t = 0
 - (ii) Show the voltage and current on a time diagram.
 - (iii) Show the voltage and current on a phasor diagram.
- b) A 50-Hz voltage of 230 volts effective value is impressed on a capacitance of 2 μF.
 (i) Write the time equations for the voltage and the resulting current. Let the zero axis of the voltage wave be at t = 0.
 (ii) Show the voltage and current on a phasor diagram.
- c) Calculate the total resistance between the terminals A & B in the figure below.



Q5:

- *a*) A vector is represented by 20 $e^{-j2\pi/3}$. Write the various equivalent forms of the vector and illustrate by means of a vector diagram, the magnitude and position of the above vector.
- b) In a series circuit containing pure resistance and a pure inductance, the current
 10 and the voltage are expressed as :
 - i (t) = 5 sin (314 t + 2 $\pi/3$) and
 - v (t) = 15 sin (314 t + 5 $\pi/6$)
 - (i) What is the impedance of the circuit?
 - (ii) What is the value of the resistance?
 - (iii) What is the inductance in henrys?
 - (iv) What is the average power drawn by the circuit?
 - (v) What is the power factor?
- *c)* Apply Thevenin's theorem to calculate the current through the 6 Ω resistor of the circuit of figure below:

4

9

5





a) An a.c. voltage (80 + j 60) volts is applied to a circuit and the current flowing is (-4 + j 10) 9 amperes.

Find

- (i) impedance of the circuit
- (ii) power consumed and all institute Of Technology
- (iii) Phase angle. Kokrajhar :: Bodoland
- **b**)
- A resistance of 20 Ω , an inductance of 0.2 H and a capacitance of 100 μ F are connected in series across 220-V, 50-Hz mains. **10**

Determine the following

- (i) impedance
- (ii) current
- (iii) voltage across R, L and C
- (iv) power in watts and VA
- (v) p.f. and angle of lag.

c) State the Ohm's Law.

Q7:

a) Apply KCL to find the value of I in the figure below.



- *b*) Write short notes on: (any four)
 - i) Power factor
 - ii) Resonance
 - iii) Form Factor
 - iv) Maximum Power Transfer Theorem
 - v) Norton's theorem

1