

Total No. of printed pages = 5

19/3rd Sem/DIE302

2021

**ELECTRONICS DEVICES  
AND CIRCUITS - I**

Full Marks - 100

Time - Three hours

The figures in the margin indicate full marks  
for the questions.

Answer any *five* questions.

1. (a) What is Diode? Explain how depletion region is formed in open circuited p-n junction. 6
- (b) Explain the behavior of p-n junction under forward biasing. 7
- (c) Plot the volt-ampere curve for a p-n diode and explain the nature of this curve. 6
- (d) The depletion region in an unbiased P-N junction contains \_\_\_\_\_. (Fill in the blank) 1

[Turn over

2. (a) Draw the symbol of a normal diode and a zener diode. 2
- (b) What do you mean by reverse breakdown of a diode ? Explain how reverse breakdown occurs in a diode. 2+6=8
- (c) Draw the circuit diagram of half-wave rectifier and explain the operation. 7
- (d) State the advantages of half-wave rectifier. 3
3. (a) Draw the full-wave rectifier circuit and explain its operation. 8
- (b) Derive expressions of average value of D.C. current and average D.C. load voltage of a full-wave rectifier. 7
- (c) A full-wave rectifier supplies a load of  $1\text{ K}\Omega$ . The A.C. voltage applied to the diodes is 220-0-220 volt rms. If diode resistance is neglected, calculate average D.C. voltage, average D.C. current, DC power output and RMS current. 5



4. (a) What is transistor? What are the types of BJT? State the two junctions in the transistor.

1+2+2=5

(b) Explain the working principles of NPN transistor.

7

(c) State the operating region of BJT.

3

(d) A transistor has  $I_B = 100\mu\text{A}$  and  $I_C = 2\text{mA}$ . Find

5

(i)  $\beta$  of the transistor,

(ii)  $\alpha$  of the transistor,

(iii) Emitter current,

(iv) If  $I_B$  changes by  $+25\mu\text{A}$  and  $I_C$  changes by  $+0.6\text{mA}$  find the new value of  $\beta$ .

5. (a) What is FET? Explain with neat sketch construction of n-channel and p-channel JFET.

1+6=7

(b) Explain the working of n-channel JFET.

8

(c) Explain the construction of E-MOSFET.

5

6. (a) Classify power amplifier based on mode of operation. 6
- (b) Give the differences between voltage amplifier and power amplifier. 4
- (c) Describe a transistor class A power amplifier with output transformer as load. 5
- (d) A class A power amplifier uses a transformer as a coupling device. The transformer has a turn ratio of 10 and the secondary load  $10\Omega$ . Zero signal current is 100mA. When signal is present at the base, the output voltage swings between 24V and 4V while the collector current swings between 0.9A and 0.5A. Determine :
- (i) collector impedance
  - (ii) signal power output
  - (iii) D.C power input and
  - (iv) overall efficiency



7. Write short notes on the following any *four* :

5×4=20

- (a) Clipping Circuits
- (b) Rectifier
- (c) Transistor CE configuration
- (d) MOSFET
- (e) Push-Pull power amplifier.
- (f) Power supply (Block diagram).

