

2022

ELECTRONICS DEVICES AND CIRCUITS-I

Full Marks: 100

Time: Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

1. a) What is p-n junction? Explain the theory of p-n junction. 2+5=7
- b) Explain the operation of forward biased diode. 7
- c) Draw and explain the V-I characteristics of a p-n junction diode. 6
2. a) What is rectifier? Draw the full wave rectifier circuit and explain its operation. 2+8=10
- b) Derive average D.C. current of full wave rectifier. 4
- c) Draw the load current and load voltage waveforms for half wave rectifier 4
- d) Draw the symbol of zener diode and p-n junction diode. 2
3. a) What are the types of BJT? Explain their construction. 2+2=4
- b) Explain the working principle of npn transistor. 8
- c) State the operating region of BJT. 3
- d) For a transistor has $I_E=1$ mA and $I_B=10$ μ A. Determine α and β . 5
4. a) Draw the neat circuit configuration of CB connection. 2
- b) Explain Q-point and DC load line. 3
- c) What is transistor biasing? Name different methods of transistor biasing. 4
- d) Explain fixed biased method. 5
- e) A fixed biased circuit with silicon transistor ($V_{BE}=0.7$ V) has $V_{CC}=15$ V, $V_{CE}=6$ V and collector current 7 mA. Find R_C , I_B , and R_B if $\beta=100$. 6

5. a) Explain the construction and operation of N channel JFET. 10
- b) Draw the following symbols 2
- (i) P channel E-MOSFET (iii) N Channel D-MOSFET
- c) Explain the operation of N-channel E-MOSFET. 8
6. a) What is power amplifier? Define Class A, Class B, and Class C power amplifier 7
- b) A sinusoidal signal $V_s=2\sin 350t$ is applied to a power amplifier. The resulting current is $i_0=15\sin 400t + 1.2\sin 800t + 0.8\sin 1250t$
- Calculate (i) the total harmonic distortion and (ii) increase in power (%) 5
- b) Derive the efficiency of a Class B power amplifier. 8
7. Write short notes on (any four): 5X4=20
- i) Regulated power supply
- ii) Diode reverse breakdown
- iii) Harmonic distortion
- iv) Adjustable voltage regulator
- v) Push Pull power amplifier
-