

Total No. of printed pages = 4

19/3rd Sem/DIE304

2021

DIGITAL ELECTRONICS

Full Marks – 100

Time – Three hours

The figures in the margin indicate full marks
for the questions.

Answer any *five* questions.

1. (a) Convert the following numbers : $2 \times 5 = 10$

(i) $(78)_{10}$ to Octal

(ii) $(45)_8$ to Binary

(iii) $(10010110)_2$ to Decimal

(iv) $(324)_{16}$ to Binary

(v) $(24.25)_{10}$ to BCD.

(b) Perform the following operations using 8-bit
2's complement technique : $2+2=4$

(i) $(+14)_{10} + (-12)_{10}$


(ii) $(-21)_{10} + (-35)_{10}$




(c) Convert the following binary codes into equivalent Gray codes : $2+2=4$

- (i) $(110110)_2$ (ii) $(111110)_2$.

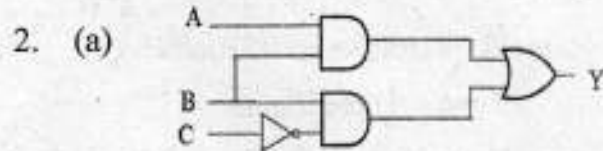(d) Implement a NOT gate using an EX-OR gate. 2



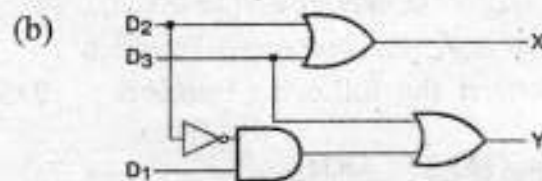For the diagram above, write its output expression and find out the truth table. 4



For the diagram above, write the output expressions for X and Y, and find out the truth tables for both X and Y. $3+3=6$

(c) What do you mean by the term "Universal gates" ? 2

(d) For the Boolean expressions given below, find out the truth table and draw the logic circuit using basic gates : $4+4=8$

(i) $Y = (\bar{A}.B + A.\bar{B}).C$

(ii) $Y = \bar{A}.B + \bar{B}.C$



3. (a) Minimize the following Boolean Expressions : 2+2=4

(i) $Y = \bar{A}BC + ABC + A\bar{B}C + ABC$

(ii) $Y = (A+B+\bar{C})(A+B+C)(\bar{A}+B+C)$

(b) Prove that : 2×3=6

(i) $X.(X+Y) = X$ (ii) $(\bar{X}+Y).Y = X.Y$

(iii) $(A+B).(A+\bar{B}) = A$

(c) State and prove De-Morgan's theorems. 6

(d) Write the dual and complement of the following Boolean expressions : 2+2=4

(i) $A+BC$ (ii) $(\bar{A}+B).(A+\bar{B})$

4. (a) Minimize using K-Map technique : 4+6=10

(i) $F(A,B,C) = m(0,1,2,6) + d(3,7)$

(ii) $F(A,B,C,D) = m(4,5,6,7,12,13,14,15) + d(0,1,11)$

(b) Explain the working of a half-adder circuit with the help of its truth table and logic diagram. 4

- (c) What is a full subtractor? Write its truth table, output expressions and draw the logic diagram. 6
5. (a) Explain the working of a 4-bit binary adder with proper block diagram. 6
- (b) What is a multiplexer? Explain the working of a 4:1 Mux. 6
- (c) Write the truth table of a 3-to-8 line Decoder and explain its working. 4
- (d) What is a parity generator circuit? Name the different types and briefly explain its use. 4
6. (a) Mention two differences between a Combinational circuits and Sequential circuits. 2
- (b) Draw the logic circuit of an Active HIGH S-R Latch and write its characteristic equation. 6
- (c) What are Programmable Logic devices? Name the different types. 4
- (d) Implement a Full-adder circuit with the help of a PLA. 8

