

2021

**ELECTRONICS DEVICES AND CIRCUITS-II**

*Full Marks: 60*

Time: 2 hours

*The figures in the margin indicate full marks for the questions.*

- A. Multiple Choice Questions 1 x 20=20
1. Op-amp can be used as
    - a. Voltage regulator
    - b. Comparator
    - c. Pulse generator
    - d. All of these
  2. Op-amp can amplify
    - a. D.C. signal
    - b. A.C. signal
    - c. Both (a) and (b)
    - d. None of the above
  3. An ideal Op-amp has
    - a. Infinite voltage gain
    - b. High output resistance
    - c. High slew rate
    - d. Very low CMRR
  4. For an inverting amplifier
    - a. Output voltage is out of phase with input
    - b. Output voltage is in phase with input
    - c. Output voltage is an impulse
    - d. None of the above

5. Op-amp can be effectively utilized in linear application by controlling
  - a. CMRR
  - b. Slew rate
  - c. Gain
  - d. Bandwidth
6. Which amplifier is used when we require an output which is equal to the input multiplied by positive constant?
  - a. Inverting amplifier
  - b. Non inverting amplifier
  - c. Subtractor
  - d. Differentiator
7. An integrator converts a D.C. signal into linearly increasing \_\_\_\_\_ signal.
  - a. Pulse wave
  - b. Ramp
  - c. Saw tooth
  - d. Impulse
8. A voltage follower
  - a. Is non inverting
  - b. Has no feedback
  - c. Has gain one
  - d. All of the above
9. Negative feedback
  - a. Reduces gain
  - b. Reduces distortion
  - c. Both (a) and (b)
  - d. Increases output impedance
10. In an LC transistor oscillator the active device is
  - a. LC tank circuit
  - b. Biasing circuit
  - c. Transistor
  - d. None of the above

11. In an LC oscillator the frequency of oscillator is \_\_\_\_\_ L or C.
  - a. Proportional to square of
  - b. Directly proportional to
  - c. Independent of the values of
  - d. Inversely proportional to square root of
12. A wien bridge oscillator uses \_\_\_\_\_ feedback.
  - a. Only positive
  - b. Only negative
  - c. Both positive and negative
  - d. None of the above
13. An oscillator differs from an amplifier because it
  - a. Has more gain
  - b. Requires no input signal
  - c. Always has the same input
  - d. Requires no D.C. supply
14. A tuned amplifier is used in
  - a. Radio frequency
  - b. Low frequency
  - c. Audio frequency
  - d. None of the above
15. Potential instability can be seen
  - a. Single tuned amplifier
  - b. Double tuned amplifier
  - c. Stagger tuned amplifier
  - d. None of the above
16. The resonance curve of the tuned amplifier for a high value of Q
  - a. Is flat
  - b. Is sharp
  - c. Has high bandwidth
  - d. None of the above

17. For faster switching action of a transistor
  - a. A capacitor may be connected across the base resistance
  - b. A capacitor may be connected in series with the base resistance
  - c. A capacitor may be connected across the emitter resistance
  - d. The value of coupling capacitor may be increased.
18. \_\_\_\_\_ multivibrator is a square wave oscillator
  - a. Monostable
  - b. Astable
  - c. Bistable
  - d. None of the above
19. When a transistor is used as a switch its operation is confined in
  - a. Cut off region
  - b. Saturation region
  - c. Active region
  - d. (a) and (b) both
20. The frequency of oscillation of an astable multivibrator depends on the
  - a. RC value of circuit
  - b. Value of transistor  $\beta$
  - c. Width of input impulse
  - d. Collector load resistors

B. Very Short Question

2\*6=12

1. What is virtual ground theory?
2. Why tuned amplifiers cannot be operated between 30 Hz to 10 Hz?
3. State the conditions under which a feedback amplifier works as an oscillator.
4. What is meant by CMRR? Explain whether this should be very high or very low for an Op-amp amplifier.
5. What are the advantages of negative feedback amplifier?
6. What is the importance of wien bridge oscillator?

C Short Question

4\*7=28

1. How bandwidth can be changed in the response curve by varying degree of

coupling in double tuned amplifier?

2. Describe inverting and non-inverting Op-amp.
3. Describe Hartley oscillator circuit and explain its action.
4. Find the operating frequency of a transistor Hartley oscillator if  $L_1=100 \mu\text{H}$ ,  $L_2=1 \text{ mH}$  and  $C=20\text{pF}$ .
5. What is a multivibrator? Explain the principle on which it works.
6. Draw thevenin's equivalent circuit of a voltage amplifier and derive its input voltage and output voltage.
7. Find  $V_o$  for the circuit shown in the following:

