

Total No. of printed pages = 5

19/5th Sem / DIE503

2021



**ELECTRICAL AND ELECTRONIC  
MEASUREMENTS**

Full Marks – 100

Time – Three hours


The figures in the margin indicate full marks  
for the questions.

Answer any *five* questions.

1. (a) From the point of view of measurement, how would you classify the resistances? 2
- (b) Describe the ammeter voltmeter method used for measurement of medium resistances. 7
- (c) A voltmeter of resistance  $500\Omega$  and a milliammeter of  $1\Omega$  resistance are used to measure a resistance by ammeter voltmeter method. If the voltmeter reads 20V and milliammeter reads 100mA, calculate the value of measured resistance:
  - (i) if the voltmeter is put across the resistance and milliammeter is connected in series with the unknown resistance;

[Turn over

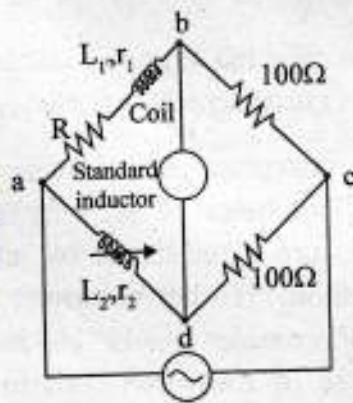- (ii) if the voltmeter is put across the unknown resistance with ammeter connected on the supply side. 6
- (d) Draw the circuit of Wheatstone bridge and derive the conditions of balance. 5
2. (a) Explain the principle of working a Kelvin's Double bridge and explain how the effect of contact resistance and resistance of leads is eliminated. 7
- (b) Mention the detectors commonly used for a.c. bridges. 3
- (c) Describe the working of a Hay's bridge for measurement of inductance. 5
- (d)




In the Maxwell's bridge above the arm "ab" Contains a coil with inductance "L1" and resistance "r1" in series with a non-inductive

resistance "R". Arm "bc" and "dc" are each a non-inductive resistance of  $100\Omega$ . Arm "ad" contains a standard variable inductor "L2" of resistance  $32.7\Omega$  ( $r_2$ ). Balance is obtained when  $L_2 = 47.8\text{mH}$  and  $R = 1.36\Omega$ . Find the value of resistance and inductance of the coil in the arm "ab". 5

3. (a) Describe the working of Heaviside Mutual Inductance Bridge for determination of mutual inductance of a coil. 6

(b)

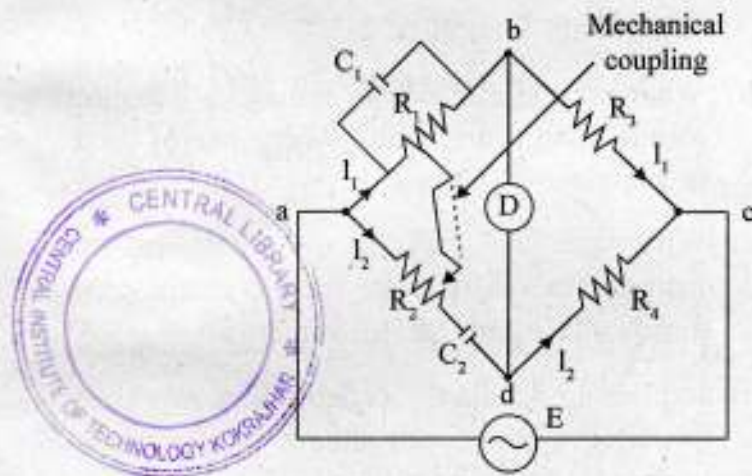

In the Wein's bridge above, calculate the value of the frequency for the given parameters:  $R_1 = 100\Omega$ ,  $R_2 = 150\Omega$ ,  $C_1 = 0.1\text{F}$  and  $C_2 = 0.05\text{F}$ . 4

- (c) State the different effects based on which the electrical measuring instruments are working. 6
- (d) Name the essential torques that can be found in an indicating instrument. 4
4. (a) The torque of an ammeter varies directly with the amount of current flowing through it. If a current of 10 A produces a deflection of 80 degree, what deflection will occur for a current of 4 A when the instrument is
- (i) spring controlled
- (ii) gravity controlled ? 4
- (b) What are the methods to introduce damping torque in an instrument ? Which one of these is popular and why ? 5
- (c) What are the sources of errors in MI Instruments ? Also, state the advantages and disadvantages of MI Instruments. 5
- (d) Explain in details the construction, working, advantages and disadvantages of Electrodynamicometer type instruments. 6
5. (a) Describe the constructional details and principles of operation of a d'Arsonval galvanometer. 7



- (b) Why does MI instrument have non-linear scales ? 2
- (c) List the advantages of electronic voltmeters. 3
- (d) With a suitable diagram, explain the main parts of a CRT. 8
6. Write short notes on any *four* : 5×4=20
- (a) Induction type energy meter
  - (b) Schering Bridge
  - (c) De Sauty's bridge
  - (d) Loss of charge method
  - (e) Megger.

