

2023

**ELECTRICAL AND ELECTRONIC MEASUREMENTS**

Full Marks : 100

Time : Three hours


*The figures in the margin indicate full marks for the questions.*

*Answer any five questions.*

1. a) What is the difference between an indicating and integrating instrument? 2+8=10  
What are the different principles of operation of measuring instruments?  
Describe each of them.
- b) Explain how d'Arsonval type galvanometer works? 6
- c) A moving coil instrument has a coil of dimensions 20 mm x 15 mm. 4  
The flux density in the air gap is  $1.8 \times 10^{-3}$  Wb/m<sup>2</sup> and the spring constant  
is  $0.1 \times 10^{-6}$  Nm/rad. Determine the number of turns required to produce an  
angular deflection of 60 degrees when a current of 5 mA is flowing through  
the coil.
2. a) Describe the constructional details and the working principle of single 7+2=9  
phase induction type energy meter.  
What are the advantages and disadvantages of single phase induction type  
energy meter?
- b) How does a galvanometer function as an ammeter and voltmeter? With the 4+3 = 7  
help of circuit diagram, derive the expression of multiplying factor of an  
ammeter.
- c) A moving-coil instrument whose resistance is 25  $\Omega$  gives a full-scale 4  
deflection with a voltage of 25 mV. This instrument is to be used with a  
series multiplier to extend its range to 10 V. Calculate the error caused by  
10°C rise in temperature. The temperature coefficient of copper is 0.004/°C  
and that of manganin is 0.00015/°C
3. a) Which bridge is suitable for medium resistance measurement and which 2+6=8  
one for low resistance measurement? With the help of circuit diagram,  
obtain the unknown value of resistance using Kelvin's double bridge.
- b) What do you mean by leakage resistance of a material? Explain how does a 1+5=6  
megger work in the measurement of high resistance?
- c) How ammeter-voltmeter method can give resistance measurement? What 4+2=6

kind of error is observed in ammeter-voltmeter method?

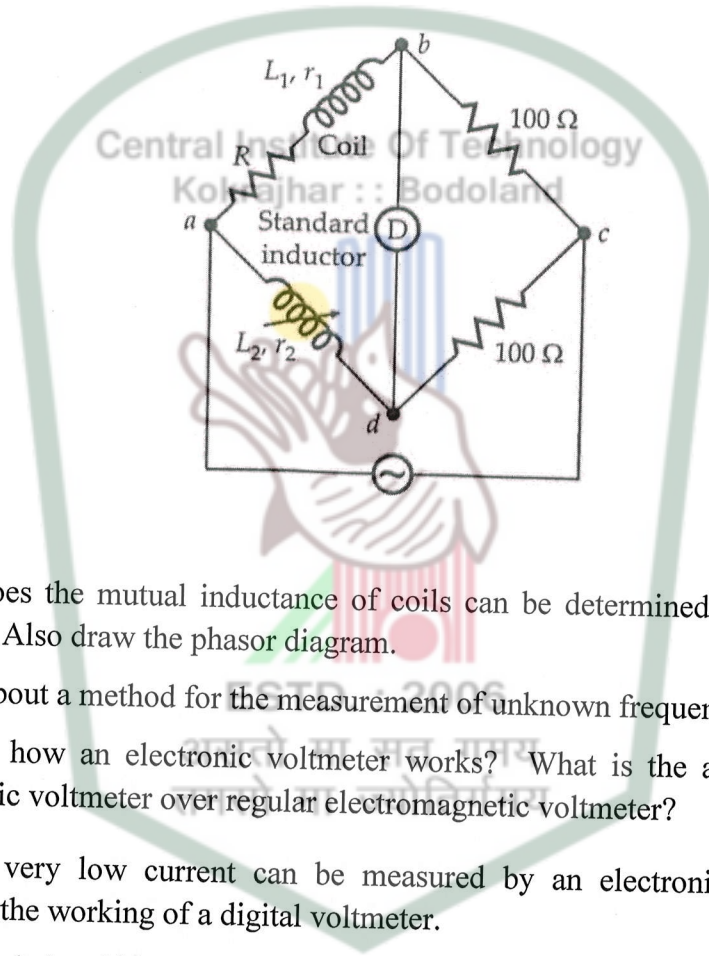4. a) Derive the expression of unknown inductance of Hay's bridge. Also draw the phasor diagram of the currents and voltages. 5+2=7
- b) Which parameter can be obtained using De Sauty's bridge? Derive the value of unknown capacitance using Schering bridge. 1+6=7
- c) A Maxwell's capacitance bridge as shown below is used to measure an unknown inductance in comparison with capacitance. The various values at balance,  $R_{bc} = 100 \Omega$ ;  $R_{cd} = 100 \Omega$ ;  $r_2 = 32.7 \Omega$ ;  $L_2 = 47.8 \text{ mH}$  and  $R = 1.36 \Omega$ . Calculate the values of  $r_1$  and  $L_1$ . 6



5. a) How does the mutual inductance of coils can be determined by a bridge circuit? Also draw the phasor diagram. 6+2=8
- b) Write about a method for the measurement of unknown frequency. 6
- c) Explain how an electronic voltmeter works? What is the advantage of electronic voltmeter over regular electromagnetic voltmeter? 5+1=6
6. a) How a very low current can be measured by an electronic ammeter? Explain the working of a digital voltmeter. 2+6=8
- b) With the help of block diagram, explain the function of the components of a cathode ray tube. 12

\*\*\*\*\*