

Total number of printed pages: 2

DIPLOMA (D) / V / DIE504

2024

POWER ELECTRONICS

Full Marks: 100

Time: Three hours

The figures in the margin indicate full marks for the questions.

Answer all five questions.

1. a) Answer the following questions in brief- 10 X 2 = 20
 - i) "The resistance of a semiconductor is dependent on temperature." Justify.
 - ii) Define the term "drift region" in power semiconductor devices.
 - iii) What is a semi-controllable semiconductor switch?
 - iv) Define Softness Factor of a diode.
 - v) Why is BJT called a bipolar device?
 - vi) What do you mean by Holding current of a thyristor?
 - vii) What is the relation between ∞ and β of a transistor?
 - viii) Define the term "Duty Cycle".
 - ix) What is the turn-on voltage of a PUT?
 - x) Name any two applications of a thyristor.

2. a) Briefly explain the reverse recovery characteristic of a diode with a suitable diagram. 4
b) Explain the different modes of operation of an SCR with the help of its static I-V characteristics. 6
c) Draw the diagram of a POWER MOSFET and briefly explain how it is turned ON. 5
d) State the different methods of turning ON a thyristor. 5

3. a) What is a firing circuit? Draw the circuit diagram of Resistance firing circuit of a thyristor and show the relation between the firing angle, 2 + 6 + 2 = 10

resistances and Gate turn-on voltage. Why is the firing angle of Resistance based circuit limited to 90° ?

- b) State the intrinsic stand-off ratio of a Unijunction transistor. 2
 - c) With the help of voltage and current waveforms, explain the working of a single-phase half-wave circuit with R-L-E load. 8
- 4.
- a) What is the main function of a DC chopper? Deduce the output voltage expression for an elementary chopper circuit. 6
 - b) Draw the circuit diagram and waveforms of a diode circuit with R-C load. 6
 - c) Define the terms i) Delay time (t_d), ii) Rise time (t_r), iii) Spread time (t_p) and iv) turn-off time (t_q) of a thyristor during switching. $4 \times 2 = 8$
- 5.
- a) Write short notes on any four. $5 \times 4 = 20$
 - i. GTO ii. Triac iii. IGBT iv. PUT
 - v. BJT as a switch vi. Two transistor model of thyristor

