

Total number of printed pages-7

53 (EC 201) BSEL

2014

BASIC ELECTRONICS

Paper : EC 201

Full Marks : 100

Time : Three hours


The figures in the margin indicate full marks for the questions.

Answer any five questions.

1. (a) Explain the $V-I$ characteristics with reference to the diode current equation. 3
- (b) Explain the physical mechanism of Avalanche and Zener breakdowns in a $p-n$ diode. 4
- (c) Draw and explain the working of a bridge type F.W.R. with necessary waveforms. 10
Derive the expression for average DC load current (I_{DC}) and efficiency (η).

Contd.

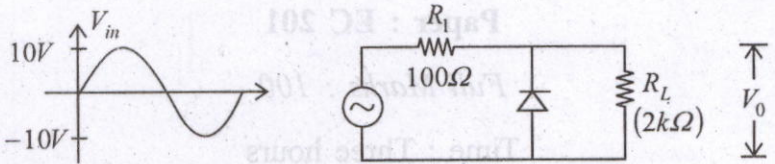
- (d) Sketch the output waveform for a clipper circuit shown in the figure below. Also obtain the peak magnitude of the output waveform. Assume silicon diode. 3



2. (a) Draw the input and output characteristics of a transistor in CE configuration. Show the different regions of operation. What are the biasing requirements for the transistor to operate in these regions? 10
- (b) Define alpha and beta of a transistor and obtain the relationship between them. 5

(c) For the transistor shown in figure below, the value of β is 100. Calculate the value of R_B that will just saturate the transistor.

Assume $V_{CE(sat)} = 0.3V$ 5

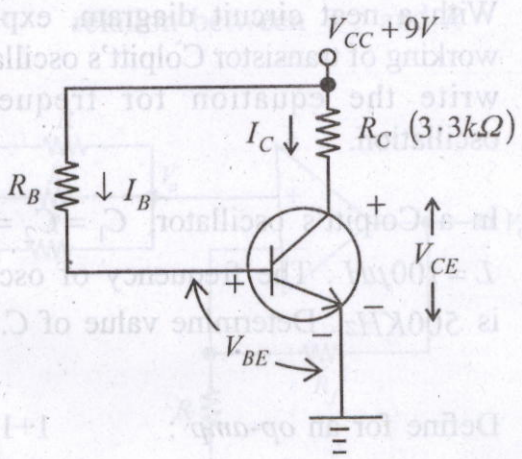


3. (a) Explain the working of N-channel FET and define the parameters of JFET. 10

(b) In what respect, a JFET differs from MOSFET? With the aid of neat sketch give the cross section of N-channel enhancement MOSFET and explain its construction, basic operation and characteristics. 10

4. (a) Draw the circuit of a two-stage $R-C$ coupled amplifier and explain the function of each component in the circuit. Also sketch the frequency response of the amplifier showing the different regions and bandwidth. 10
- (b) With a neat circuit diagram, explain the working of transistor Colpitt's oscillator, and write the equation for frequency of oscillation. 6
- (c) In a Colpitt's oscillator, $C_1 = C_2 = C$ and $L = 100\mu H$. The frequency of oscillations is 500KHz . Determine value of C . 4
5. (a) Define for an $op\text{-amp}$: 1+1+1+2=5
- (i) CMRR
- (ii) PSRR
- (iii) Slew Rate
- (iv) Virtual ground.
- (b) What are the ideal characteristics of $op\text{-amp}$? 5

(c) Show how *op-amps* can be used as a non-inverting amplifier and derive expression for its voltage gain. 5

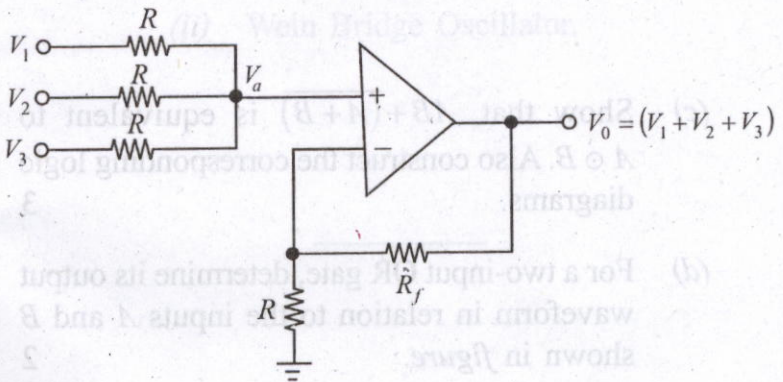(d) Given a non-inverting summing amplifier circuit and the output equation, find out the relation between R_f and R 5




6. (a) Perform the following : 5

(i) $(57 \cdot 6)_8 = (?)_2 = (?)_{16}$

(ii) $(44030)_{10} = (?)_2 = (?)_{16}$

(b) Write a boolean expression for the output Y in figure below and determine the truth table

5

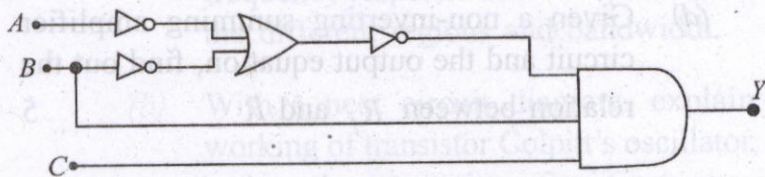


(c) Show that $AB + \overline{(A+B)}$ is equivalent to $A \odot B$. Also construct the corresponding logic diagrams.

3

(d) For a two-input OR gate, determine its output waveform in relation to the inputs A and B shown in figure.

2

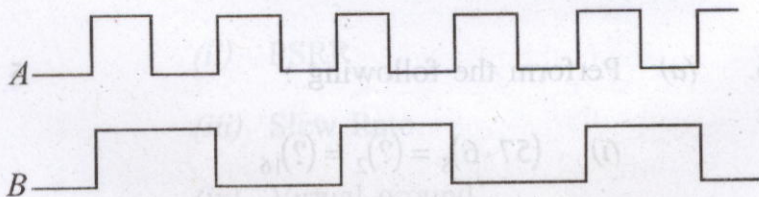

(e) What is a flip-flop? Draw the circuit diagram of S - R and J - K flip-flop and explain its operation with the help of truth table.

5

7. (a) Draw block diagram of a CRO and explain the function of each stage. 6
- (b) Describe the principle of working of LED. 6
- (c) Explain the following in brief : 4+4=8
- (i) SMPS
- (ii) Wein Bridge Oscillator.

The figures in the margin indicate full marks for the questions.

Answer any five questions.

- (a) Explain the $V-I$ characteristics with reference to the diode current equation. 3
- (b) Explain the physical mechanism of Avalanche and Zener breakdowns in a $p-n$ diode. 4
- (c) Draw and explain the working of a bridge type F.W.R. with necessary waveforms. 4
- (d) Derive the expression for average DC load current I_{dc} and efficiency (η) . 10