

Total number of printed pages-8

53 (EC 201) BSEL

2017

**BASIC ELECTRONICS**

Paper : EC 201

Full Marks : 100

Time : Three hours

***The figures in the margin indicate full marks for the questions.***

Answer **any five** questions out of **seven**.

1. (a) Differentiate between intrinsic and extrinsic semiconductors. Give *two* examples of each. 4
- (b) Derive the expression for conductivity of a semiconductor. 6

Contd.

(b) Draw the block diagram of a Cathode Ray Oscilloscope (CRO) and discuss the function of its various parts. 8

(c) Differentiate between the operation of LCD and LED displays. 4

(c) If  $n(x)$  is the concentration profile of electrons in the  $x$ -direction of a semiconductor material, evaluate the expression for electron diffusion current density in the  $+x$  direction. Assume  $\bar{l}_e$  and  $\bar{\tau}_e$  as the mean free path and mean free time of electrons between collision, respectively. 6

(d) Discuss how the current across a  $p$ - $n$  junction under open circuit condition remains zero although there exists an electric field at the junction. 4

2. (a) Derive the expression for minority carrier concentration profile when a  $p$ - $n$  diode is forward biased. Plot the concentration profile as a function of distance from the depletion region. Calculate the forward bias current in terms of the applied voltage.

4+2+4=10

(b) Explain the operation of Zener diode in the breakdown region of operation with the help of energy band diagram. 4

- (c) Explain the steps required in converting an AC voltage waveform to a DC waveform with the help of block diagram and necessary waveforms at the output of each stage. Discuss how ripple factor changes from stage to stage. 6

3. (a) Draw the output waveforms for the following diode circuits and identify its function. 4×2.5=10

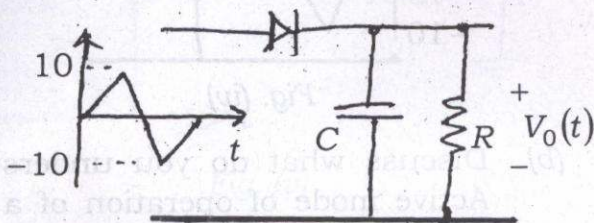


Fig. (i)

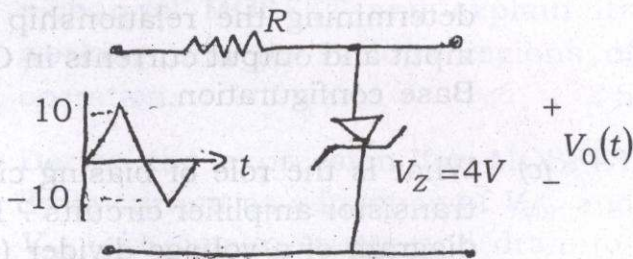


Fig. (ii)

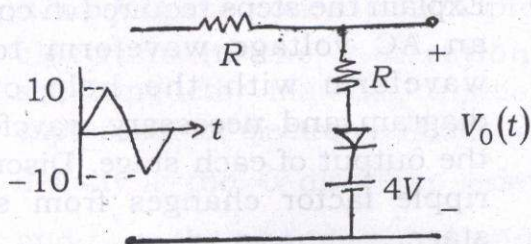


Fig. (iii)

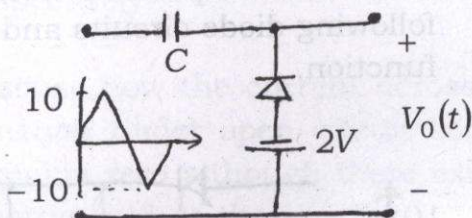


Fig. (iv)

- (b) Discuss what do you understand by Active mode of operation of a Bipolar Junction Transistor (BJT). Explain the significance of emitter injection ratio and base transport factor in determining the relationship between input and output currents in Common-Base configuration. 2+4=6
- (c) What is the role of biasing circuits in transistor amplifier circuits? Draw the diagram of a voltage divider (self-bias) circuit and comment on its merits. 2+2=4

4. (a) In the circuit shown below Fig. (v), a digital input with two levels,  $0V$  and  $5V$ , is given. Determine the operating point and mark it on the BJT output characteristics along with the load line.

5

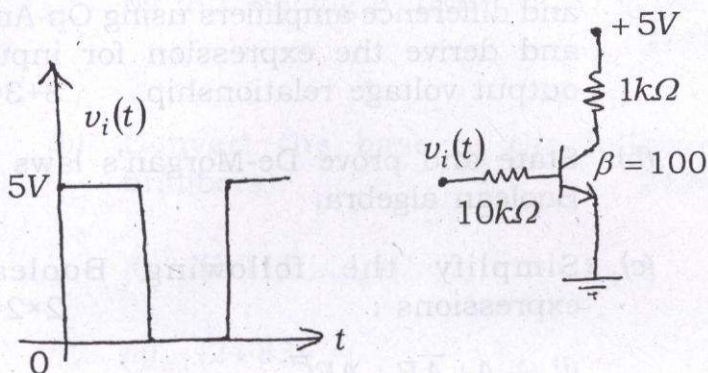


Fig. (v)

- (b) Draw the schematic diagram of an  $n$ -channel MOSFET and explain its working and its various regions of operation.

5

- (c) Derive the expression for MOSFET drain current as a function of  $V_{GS}$  and  $V_{DS}$ , the gate-to-source and drain-to-source potentials, respectively. Assume linear voltage drop along the channel.

6

(d) What do you understand by the transfer characteristics of an  $n$ -channel JFET? Derive the expression for transconductance of a JFET from its current voltage relationship. 4

5. (a) Draw the circuit diagrams of summing and difference amplifiers using Op-Amp and derive the expression for input-output voltage relationship. 3+3=6

(b) State and prove De-Morgan's laws in Boolean algebra. 5

(c) Simplify the following Boolean expressions : 2×2=4

(i)  $A + \overline{A}B + ABC\overline{C}$

(ii)  $\overline{A}\overline{B}C + AC + ABC + AB$

(d) Design a digital circuit which can Add <sup>if</sup> ( $M = 0$ ) or Subtract <sup>if</sup> ( $M = 1$ ) two 4-bit numbers in 2's complement representation. Here  $M$  is the mode-selection input to decide between Add and Subtract operation. 5

6. (a) Draw the 2-input NAND gate based circuit diagram of an SR flip-flop and explain how it can be used to store one bit of information. Discuss how one can improve the performance of S-R flip-flop by introducing 3-input NAND gates.

3+3=6

- (b) Convert the base of the following numbers :

2+2=4

(i)  $(1.111\dots)_2 = (\quad)_{10}$

(ii)  $(24.83)_{10} = (\quad)_{16}$

- (c) Draw a schematic diagram of a PMMC and discuss how it can be used to measure voltages and currents of various ranges using additional circuitry that contains a range selection switch.

10

7. (a) Discuss the operation of any digital voltmeter with necessary block diagram and waveforms.

8