

Total number of printed pages-7

53 (EC 201) BSEL

2018

BASIC ELECTRONICS

Paper : EC 201

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer **any five** questions out of **seven**.

1. (a) Using energy band diagram, briefly explain why conductivity differs for metals, semiconductors and insulators. 4
- (b) What do you understand by 'holes' in semiconductors? Explain how they give rise to drift current. 4
- (c) Discuss the cause of diffusion current and explain how to determine its direction for electrons and holes. 4

Contd.

- (d) Describe the mechanism of Avalanche breakdown in $p-n$ junction diode. 4
- (e) Draw the electron energy band diagram of a $p-n$ junction diode in open circuit condition and explain what happens to it when we apply forward and reverse bias to the diode. 4
2. (a) Draw the concentration profile of electrons and holes in open circuit condition and evaluate the expression for built-in voltage. 5
- (b) Write the equation for the rate of change of hole concentration in the n -side of a $p-n$ junction diode under forward bias condition and derive the concentration profile of holes in equilibrium condition. 5
- (c) From the concentration profile of minority carriers in a forward biased diode, derive the expression for diffusion current components. With the help of a neat diagram, explain how various current components change as a function of position along the length of the $p-n$ junction diode. 5

(d) Explain the law of junction and derive the diode current equation from the expression for diffusion currents due to minority carriers. Plot the V-I characteristics of diode under forward and reverse bias condition. 5

3. (a) Define the parameters : (i) rectification efficiency and (ii) ripple factor. Determine the expression for these in the case of a half-wave rectifier. 5

(b) Show that ripple factor of a half-wave rectifier can be considerably improved by introducing a capacitor of appropriate value across the load resistance. 5

(c) Draw the circuit of a Zener diode based voltage regulator. Explain how it can regulate an unregulated power supply. 5

- (d) For the diode circuits shown below, determine the output wave forms. Assume that the diodes have ideal characteristics. 5

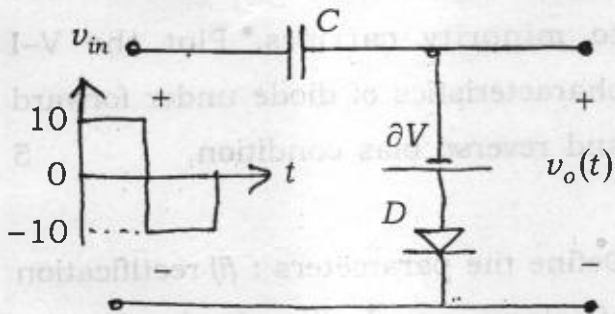


Fig. (1)

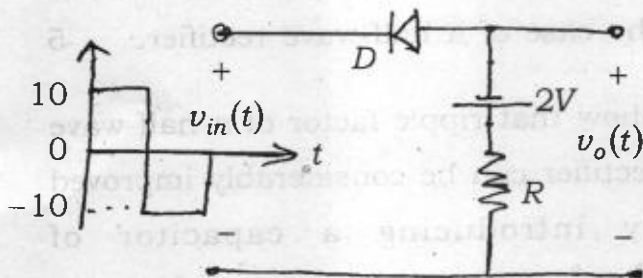


Fig. (2)

4. (a) Draw the input and output characteristics of an $n-p-n$ bipolar junction transistor (BJT) and explain the effect of changing the collector-base voltage when it is operating in the active mode. 5

(b) Why do we need biasing circuit to make the BJT function as an amplifier? Draw the voltage-divider (self-bias) biasing circuit and explain the steps in determining the resistance values. 5

(c) Explain the working of an n -channel MOSFET with the help of a neat schematic diagram. Derive the expression for drain current in both Ohmic and Saturation mode of operation. Draw the transfer characteristics and explain how to determine transconductance from it.

4+4+2

5. (a) Explain how a transistor can be used to amplify weak signals. Why the input and output resistance of a voltage amplifier is critical in determining its performance? 5

(b) Draw the circuit of a non-inverting Operational Amplifier Circuit and derive its expression for voltage gain. Discuss how the circuit could be modified to subtract one signal (say $v_2(t)$) from the other (say $v_1(t)$). 5

(c) Draw the circuit of a Wein Bridge Oscillator and evaluate — 10

(i) the condition for oscillation

(ii) the frequency of oscillation.

6. (a) Change the base of the following numbers : 4

$$(19\cdot23)_{16} = (\quad)_{10}$$

$$(11\cdot01)_{10} = (\quad)_2$$

(b) State and prove De Morgan's theorems. 4

(c) Simplify the following expressions : 4

(i) $(A + B)(\bar{A} + B)\bar{B}$

(ii) $A[A + AB]$

(d) Implement a full adder circuit using only NOR gates. 4

(e) What is the drawback of S-R flip-flop and explain how it can be overcome in J-K flip-flop ? 4

7. (a) With the help of a neat circuit diagram explain how currents in various ranges can be measured using a PMMC meter. 5
- (b) Draw the block diagram and explain the principle of operation of CRO. 5
- (c) Draw the functional block diagram of Function generator that can produce sine wave, square wave and triangular wave in the audio frequency range. 5
- (d) With the help of a neat schematic diagram, explain how liquid-crystal display work. 5
-