

Total number of printed pages-5

53 (EC 201) BSEL

2019

**BASIC ELECTRONICS**

Paper : EC 201

Full Marks : 100

Time : Three hours


**The figures in the margin indicate full marks for the questions.**

Answer **any five** questions.

1. (a) Describe the operation of an  $n-p-n$  (BJT) Transistor and write the expression for terminal currents. 8
- (b) Derive a relationship between  $I_{CEO}$  and  $I_{CBO}$ . 2
- (c) Describe the Barkhausen's criteria for oscillations, draw the circuit diagram of Hartley's oscillator and explain its operation. 2+8

Contd.

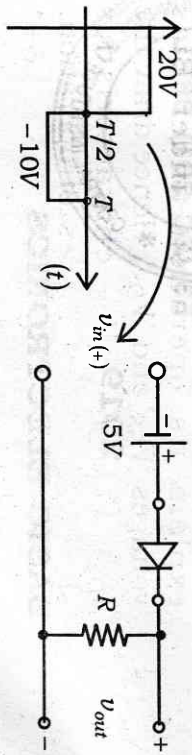2. (a) Find the output voltage for the following network and input signal. 5



- (b) Write a short note on n-type material of semiconductors and give examples. 5

- (c) Describe the common emitter configuration, draw the input and output characteristics with proper explanation of different operating modes. 10

3. (a) Describe the operation of a Center-tapped Bridge Rectifier, compare its performance parameters with a Bridge Rectifier. 7+3

- (b) Write a short note on Light-emitting Diode (LED). 5

- (c) Draw the input and output characteristics of an n-p-n transistor in Common-collector configuration and show various modes of operation. 5

4. (a) Draw the physical diagram of n-channel (Enhancement type) MOSFET and explain its operation under Bias voltages ' $V_{GS}$ ' and ' $V_{DS}$ '. Hence draw the  $I_{DS} \sim V_{GS}$ ,  $I_{DS} \sim V_{DS}$  characteristics showing different modes of operation. 6+4

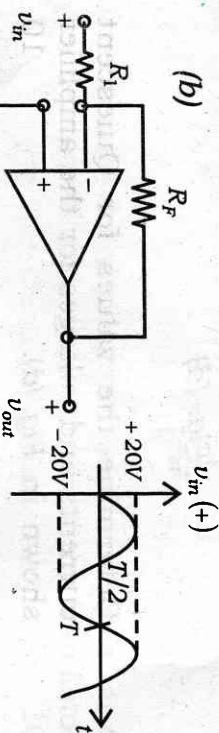


Fig. (a)

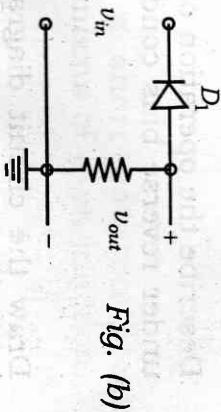


Fig. (b)

Derive the expression for voltage gain ( $v_{out}/v_{in}$ ) assuming ideal Op-amp (Fig. a). 6

- (c) Draw the output waveform for the circuit shown in Fig. (b) for input wave shown. 4

5. (a)

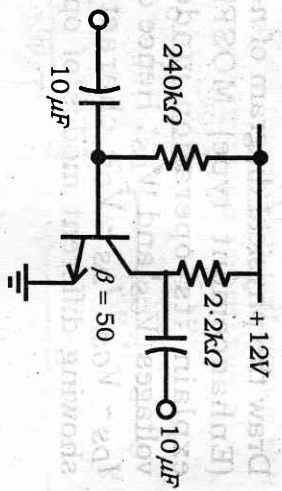


Fig. (d)

Determine the values for Quiescent currents and voltages for the amplifier shown in Fig. (d). 10


(b) Mention the features of an Op-amp. 5

(c) Describe the operation of a *pn* junction under reverse bias conditions. 5

6. (a) Draw the circuit diagram for a non-inverting amplifier and derive expression for voltage gain. 10

(b) Describe the operation of Half-wave Rectifier, derive expressions for Average value, rms value of output voltage and hence find out the rectification efficiency. 10

7. (a)

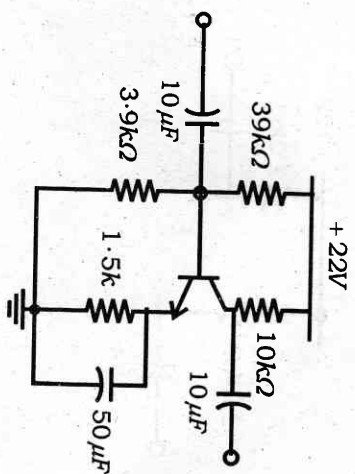

Determine quiescent voltages and currents at 3 terminals of the transistor for the above amplifier. 10

(b) Describe the construction and operation of LCD display with proper diagram. 10

8. Write a short note on breakdown mechanisms of a *pn* junction. 8

(b) Implement a 2-input OR gate using 2-input NAND and 2-input NOR gate. 8

(c) Define these terms : PIV, Pinch-off voltage. 4