

Total number of printed pages-12

53 (EC 301) ELDC

2019

**ELECTRONIC DEVICES &  
CIRCUITS**

Paper : EC 301

Full Marks : 100

Time : Three hours


**The figures in the margin indicate  
full marks for the questions.**

Answer **any five** questions.

1. (a) (i) Discuss the effect of Q-point location on ac operation. 3
- (ii) Write down the application of CC amplifier. 1
- (iii) Draw the small-signal model of the CB configuration. 2
- (b) (i) Compare voltage gain, current gain, input resistance, output resistance in between three different configurations (CC, CB, CE). 2

Contd.

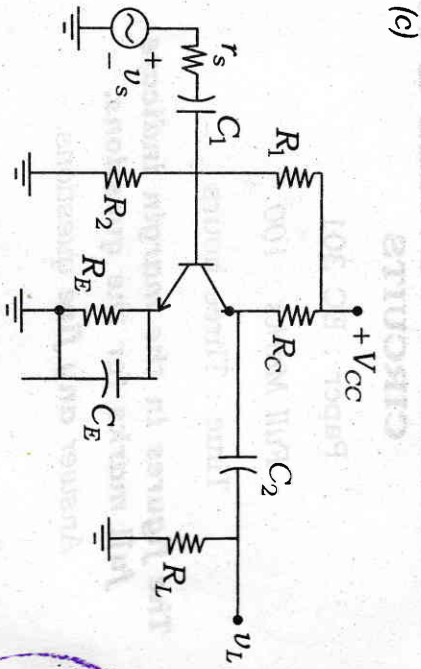
- (ii) What are the functions of coupling capacitor in a single stage amplifier? 2



For the above circuit :

- (i) Draw the equivalent ac circuit with small signal CE model. 4
- (ii) Calculate input resistance ( $r_i$ ), current gain ( $A_i$ ), voltage gain ( $A_v$ ), overall voltage gain, overall current gain  $\left(\frac{i_L}{i_s}\right)$ . 6


2. (a)

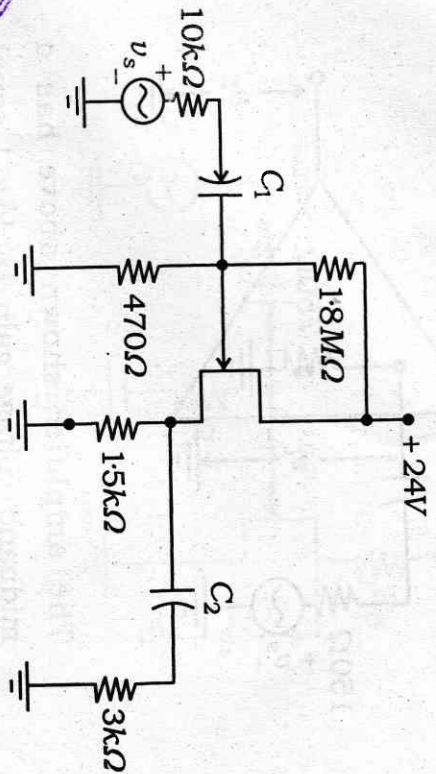

The JFET above has  $g_m = 5 \times 10^{-3} \text{ s}$  and  $r_d = 100k\Omega$ .

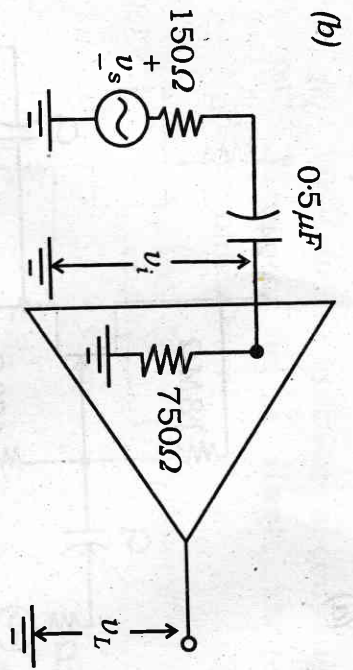
- Find (i) the input resistance
- (ii) the voltage gain
- (iii) the output resistance of the amplifier.






The amplifier shown above has a midband voltage gain  $|v_L/v_s|$  equal to 90. Find

- (i) the voltage gain  $|v_L/v_i|$
  - (ii) the lower cutoff frequency
  - (iii) the voltage gain  $|v_L/v_s|$  in dB, at the cutoff frequency.
- (c) (i) Explain how the shunt capacitance affects the high frequency response of an amplifier. 3
- (ii) What is the source of this shunt capacitance? 1

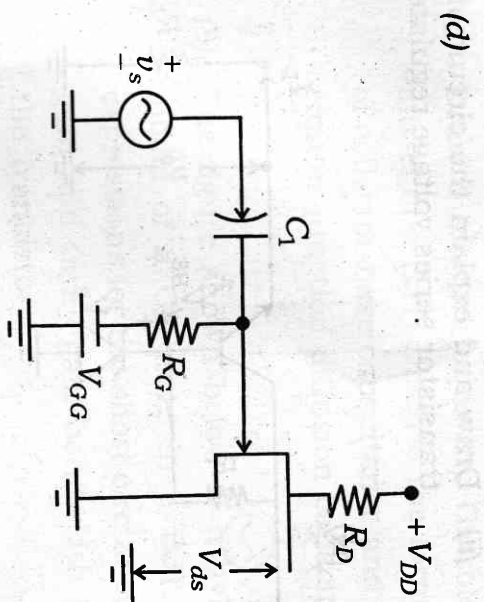


- (i) Draw the small signal equivalent circuit of the above amplifier and find out voltage gain equation. 4
  - (ii) Draw & discuss different types of Amplifier Models. 2
- (a) (i) What are different methods of Interstage Coupling. Discuss each type in brief. 4
- (ii) State and explain Miller's theorem. 2
- (b) (i) Draw & explain block diagram of a series voltage regulator. 5

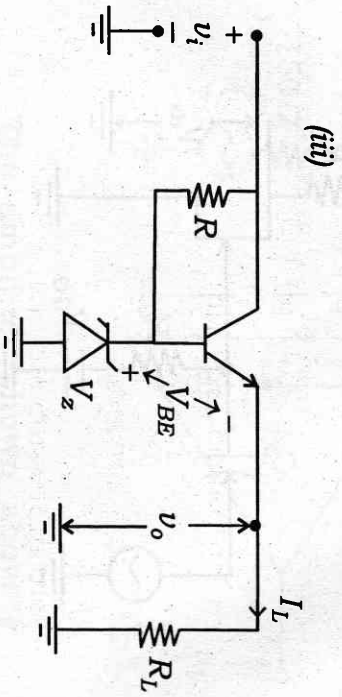- (ii) Draw and explain the circuit of a transistor series voltage regulator. 4




In the above Figure  
 $V_i = 20V$     $R = 200\ \Omega$     $V_z = 12V$   
 $V_{BE} = 0.65V$

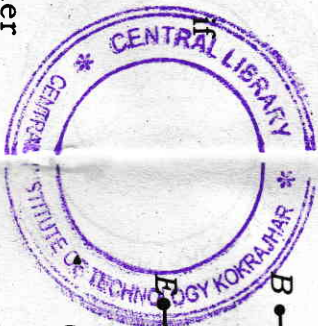- Find (a)  $V_o$   
 (b) The collector emitter voltage of the pass transistor and  
 (c) the current in the  $200\ \Omega$  resistor. 5




4. (a) Draw the hybrid- $\pi$  or the Giacoleto- $\pi$  model of a BJT. Discuss the formation of collector-base capacitance and base-emitter junction diffusion capacitance. 1+4

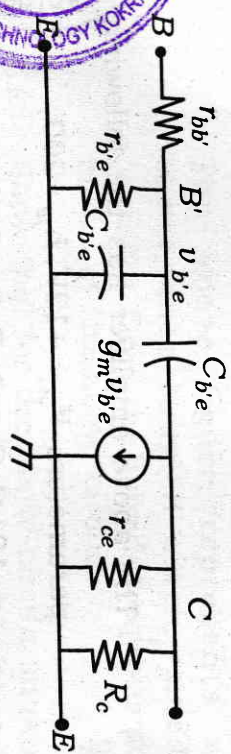
- (b) The figure shown below is a hybrid- $\pi$  model of a CE-stage in a BJT. Find expressions for the short circuit current gain and unity gain bandwidth ( $f_r$ ) of the transistor. 7



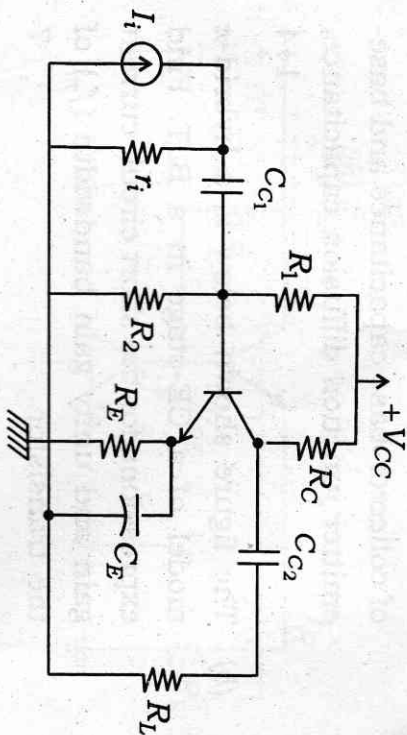- (c) The following low-frequency parameters are known for a given transistor at room temperature, and at  $I_c = 10mA$  and  $V_{CE} = 10V$ ,  $h_{ie} = 500\ \Omega$ ,  $h_{oe} = 4 \times 10^{-5} A/V$ ;  $h_{re} = 100$ ;  $h_{fe} = 10^{-4}$ . At the same operating point,  $f_T = 50 MHz$  and  $C_{b'e} = 3 pF$ . Calculate the values of all the hybrid- $\pi$  parameters. 8



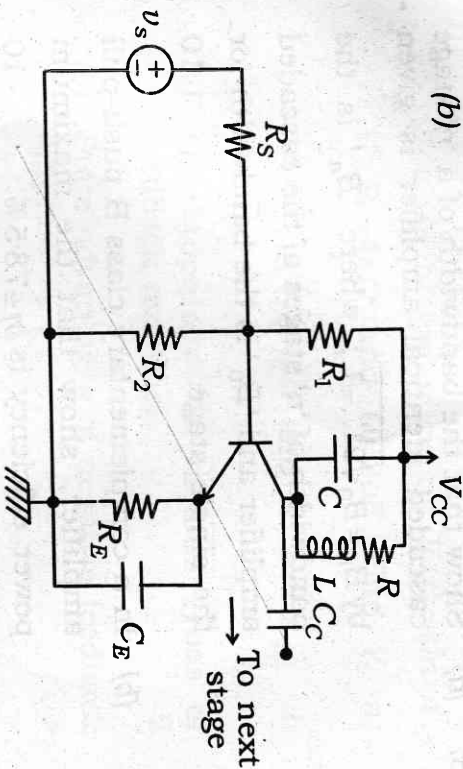The above amplifier has the following parameters  $V_{CC} = +12V$ ,  $h_{fe} = 200$ ;  $r_i = 10k\Omega$ ,  $C_{bc} = 2pF$ ,  $R_b = R_1 \parallel R_2 = 2k\Omega$ ;  $C_{be} = 200pF$ ,  $r_{bb'} = 20\Omega$ ,  $r_{b'e} = 150\Omega$ ,  $R_L = 200\Omega$  ( $R_C \gg R_L$ ). Draw the hybrid- $\pi$  model and hence find the mid-band gain, 3dB frequency  $f_H$ .



The above figure represents a capacitance coupled single tuned amplifier. Draw the hybrid- $\pi$  equivalent model of the above circuit. 2

(c)

Show that for the above circuit shown in (b), the voltage gain (without considering the source resistance  $R_s$ ) is given by

$$A_v = \frac{A_{res}}{1 + j2\delta Q_e}; \text{ where}$$

$\delta \rightarrow$  Fractional frequency variation,

$Q_e \rightarrow$  Effective quality factor of the o/p circuit.

$A_{res} \rightarrow$  Voltage gain at resonance ( $\delta = 0$ ).

6. (a) Show that the bandwidth of a 'n' stage cascaded identical amplifier is given by  $B_n = B_0 \sqrt{2^{1/n} - 1}$ ; where 'B<sub>n</sub>' is the bandwidth of 'n' stages of the cascaded amplifier and 'B<sub>0</sub>' is the bandwidth for the single stage. 10
- (b) In a complementary class B push-pull amplifier, show that the maximum power efficiency is  $\eta \approx 78.5\%$ . 10
7. (a) Define the following : 3
- (i) Offset voltage
- (ii) CMRR
- (iii) Slew Rate
- (b) Derive the expression of 3-input inverting summing amplifier. 5
- (c) Draw the circuit of an integrator and derive the expression for its output voltage. State application of an integrator. 6



- (d) For an integrator circuit  $V_i(t) = \sin \omega t$ .  
 If  $R_1 = 4k\Omega$  and  $C = 2\mu F$ , find  $V_o$  at  $\omega t = \frac{\pi}{2}$  if  $V_o(0) = 0$  and  $\omega = 1\text{MHz}$ . 6
8. (a) Give topology for various types of feedback amplifier. 2
- (b) State advantages of negative feedback amplifier. 3
- (c) Explain the effect of negative feedback on lower cutoff and upper cutoff frequency of the amplifier and prove that bandwidth with feedback is greater than bandwidth without feedback. 10
- An amplifier has midband voltage gain of 1000 with  $f_L = 50\text{Hz}$  and  $f_H = 50\text{kHz}$ . If 5% feedback is applied then calculate gain  $f_L$  and  $f_H$  with feedback. 5
9. (a) Differentiate between class A, B and C amplifier. 3
- (b) Explain the working of directly coupled class A amplifier with the help of neat diagram. 6

- (c) Maximum collector efficiency of class A amplifier is           . 1
- (d) Describe Hartley oscillator with its operation. 6
- (e) Find the operating frequency of a transistor Hartley oscillator, if  $L_1=100\mu H$ ,  $L_2=1mH$ , mutual inductance between the coils is  $20\mu H$  &  $C = 20pF$ . 4
10. (a) Differentiate between JFET and BJT. 4
- (b) Explain operation of *N*-channel FET. Also explain its static characteristic curves. 8
- (c) A JFET has a drain current of  $5mA$ . If  $I_{DSS}=10mA$  and  $V_{GS(off)} = -6V$ , find the value of  $V_{GS}$  and  $V_P$ . 3
- (d) Draw a neat circuit diagram of transistor monostable multivibrator and discuss its working. 5

