

Total number of printed pages-4

53 (EC 201) BSEL

2021

BASIC ELECTRONICS

Paper : EC 201

Full Marks : 100

Time : Three hours


The figures in the margin indicate full marks for the questions.

Answer **any five** questions out of **seven**.

1. (a) Describe the operation of Common base configuration, draw the input, output characteristics. 10
- (b) Derive the closed-loop gain for Inverting, Non-inverting amplifier. 10
2. (a) Classify the LC Oscillators, describe the operation of each oscillator with proper circuit diagram and derive the expression for frequency of oscillation. 10

Contd.

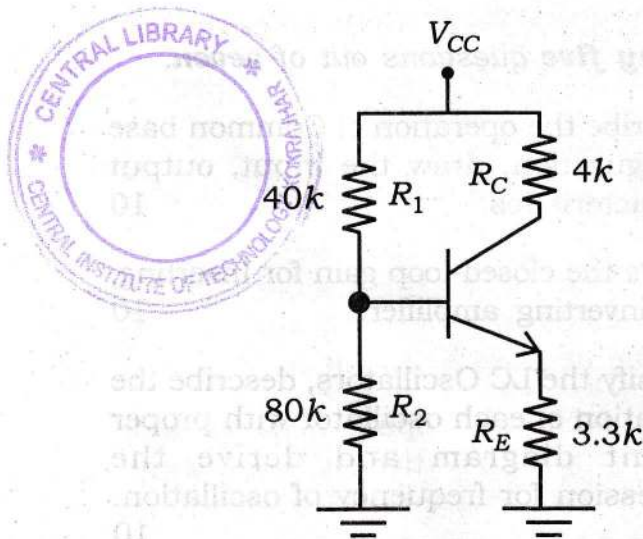- (b) Classify the various types of filters used after rectification, describe the operation of Diode-C filter and derive the expression for ripple voltage. 10
3. (a) Write short notes on: 10
- (i) Depletion region
 - (ii) Avalanche Breakdown.
- (b) Give a detailed comparison between negative and positive feedback. 10
4. (a) Calculate the DC terminal voltages and branch currents for the circuit below, for $\beta = 100$ and $V_{CC} = 15V$. 10



-
- (b) Describe the operation of n-channel enhancement type of MOSFET, draw the input and output characteristics. 10
5. (a) Derive the expression for average value of a half-wave rectifier. 5
- (b) Mention ideal features of an operational amplifier. 5
- (c) Compare the features of BJT and FET. 5
- (d) Draw the circuit diagrams, showing various types of biasing techniques used for a transistor in Common Emitter Configuration. 5
6. (a) Describe the operation of LCD display with proper diagram. 10
- (b) Draw the circuit diagram of biased clippers
- (i) capable of clipping positive half at a fixed positive DC level, while leaving the negative half as it is. 5
- (ii) capable of clipping negative half at a fixed negative DC level, while leaving the positive half as it is. 5

7. (a) Describe the operation of BJT in active mode for a p-n-p transistor. 10
- (b) Write a short note on Light Emitting Diode. 5
- (c) Write a short note on n-type semiconductor. 5

