

Total number of printed pages-6

53 (EC 301) ELDC

2013

(December)

ELECTRONIC DEVICES & CIRCUITS

Paper : EC 301

Full Marks : 100


Pass Marks : 30

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

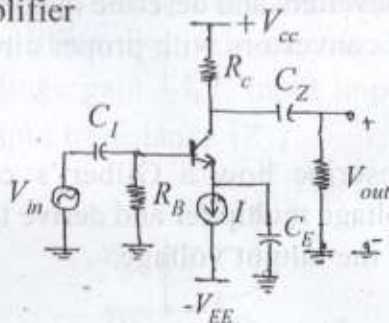
1. (a) Given the circuit diagram below is of an Amplifier



- (i) Find expression for voltage gain
(ii) Write the expression for terminal voltages at each of the terminal. 5+5

Contd.

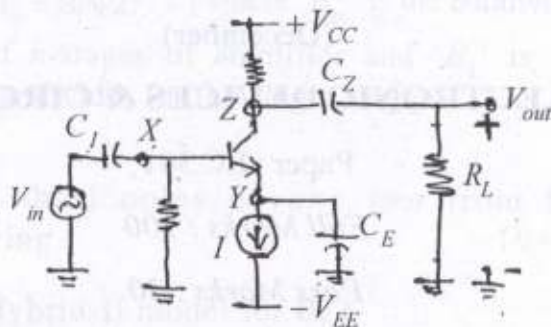- (b) The circuit shown below is assumed to be biased properly for amplification purpose.



Find the resistance looking into the terminals mentioned as node X, Y & Z.

3+4+3

2. (a) Mention various types of *DC-DC* converters and describe the buck boost-type of converters with proper circuit diagram.


10

- (b) Describe how a Gilbert's cell works as voltage multiplier and derive the expression of the output voltage.

10

3. (a) Shown below is a Common Source Amplifier.

10

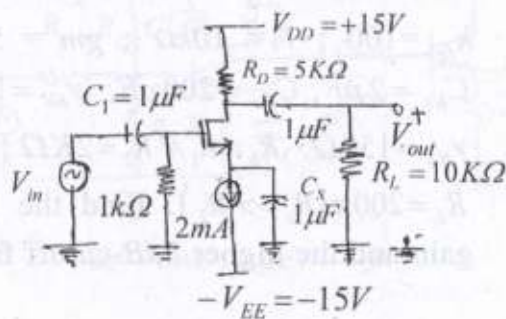

Find value of voltage gain, Input impedance and output impedance. Given


$$\mu\eta C_{ox} \frac{W}{L} = 1 \text{ mA/V}^2$$

$$\lambda = 0.1 \text{ V}^{-1} \text{ and } V_{TH} = 1 \text{ V}.$$

10


(b) The given circuit is a common collect (CC) amplifier. For this circuit calculate the voltage gain (A_v), input impedance (Z_i), output impedance (Z_o).


6+2+2

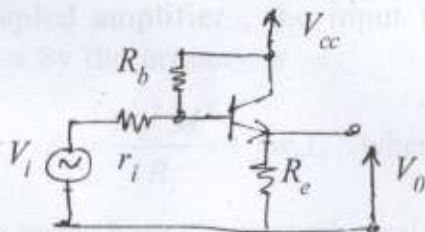

4. (a) The amplifier shown below has the following parameter : $V_{cc} = +12V$;
 $h_{fe} = 100$; $\gamma_i = 10k\Omega$; $g_m = 50mA/V$;
 $C_{b'c} = 2pF$; $C_{b'e} = 200pF$; $\gamma_{bb'} = 20\Omega$;
 $\gamma_{b'e} = 150\Omega$; $R_b = R_1 // R_2 = 2K\Omega$;
 $R_L = 200\Omega$ ($R_c \gg R_L$). Find the mid-band gain and the higher 3dB-cutoff frequency.

10

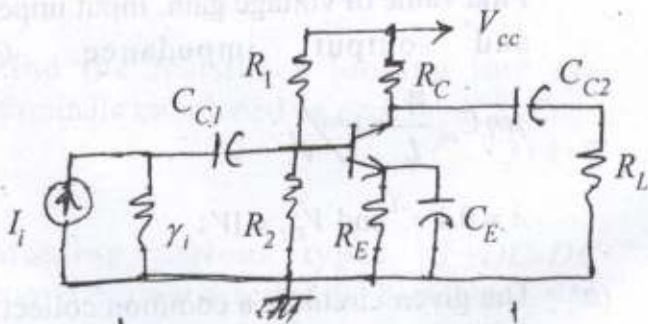

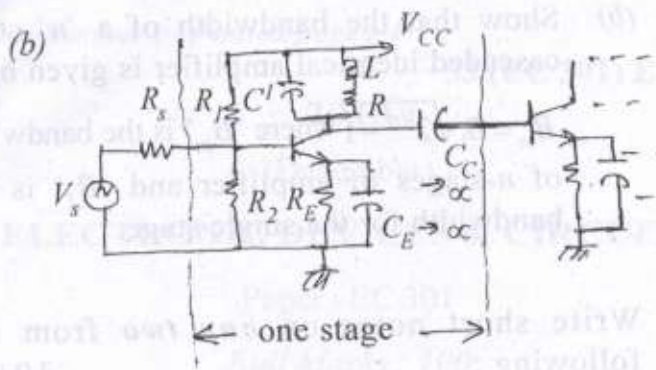

The above figure represents a capacitance coupled single-tuned amplifier. For this circuit, show that the voltage gain (without considering the source resistance R_s) is

$$\text{given by } A_v = \frac{A_{res}}{1 + j2\delta Q_e}$$

Where δ = fractional frequency deviation ;

Q_e = effective quality factor ;

A_{res} = Voltage gain at resonance. 10

5. (a) Show that for a double tuned inductively coupled amplifier ; the input impedance seen by the primary is 10

$$Z_m = \frac{W_0^2 M^2}{R_f} + j\omega_0 L_1 ; \text{ where}$$

the terms have their usual significance.

- (b) Show that the bandwidth of a 'n' stage cascaded identical amplifier is given by

$$B_{in} = B_1 \sqrt{2^{1/n} - 1}$$

where ' B_{in} ' is the bandwidth of n-stages of amplifier and ' B_1 ' is the bandwidth for the single stage. 10

6. Write short notes on **any two** from the following : 10+10

- (i) Hybrid-II model for BJT
- (ii) Miller's theorem and Miller Capacitors.
- (iii) Inductively coupled class-A power amplifier.