

Total number of printed pages-5

53 (EC 301) ELDC

2018

**ELECTRONIC DEVICES AND CIRCUITS**

Paper : EC 301

Full Marks : 100

Time : Three hours

***The figures in the margin indicate full marks for the questions.***


Answer **any five** questions out of **six**.

1. (a) Describe the operation of Common-Collector amplifier as an emitter follower. Briefly describe why it can be used as a voltage buffer. 8+2
- (b) Describe the operation of a Series Voltage regulator. 4
- (c) Derive the expression for transconductance of a BJT in Active mode. 6

Contd.

2. (a) An nMOSFET in saturation mode can be used as a voltage controlled current source. Justify with  $I_{DS} \sim V_{DS}$  characteristics. 5
- (b) Draw the circuit diagram for 2-stage cascaded CE-CE amplifier (DC coupled and RC coupled), mention the features of both types and draw small signal diagrams for each. 1+2+2
- (c) Describe the operation of Boost regulator and write the expression for its duty cycle. 10

3. (a)

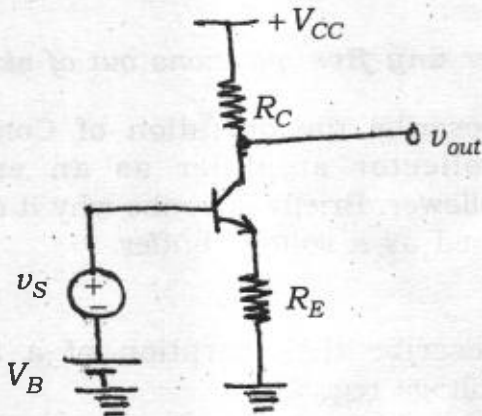


Derive the expressions for open circuit voltage gain, input resistance, output resistance for above circuit.

6+4+2


(b) Explain the operation and efficiency of a Class-AB amplifier, using proper circuit diagram and transfer characteristics. 8

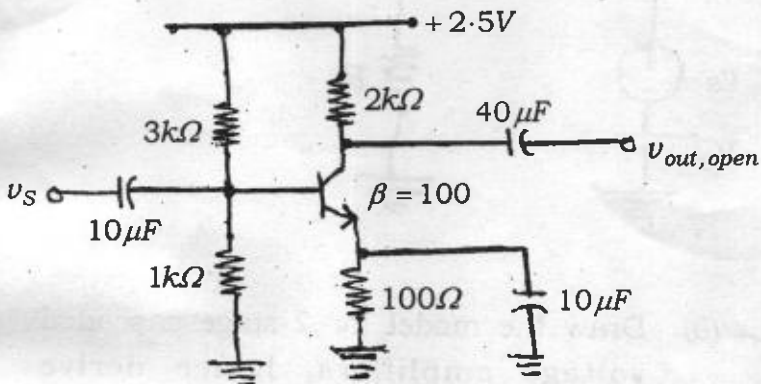4. (a) Calculate the values of open-circuit voltage gain, input resistance, output resistance for the circuit shown below. 6+2+2




(b) Describe the operation of emitter follower as a Class-A amplifier, hence derive the efficiency. 10

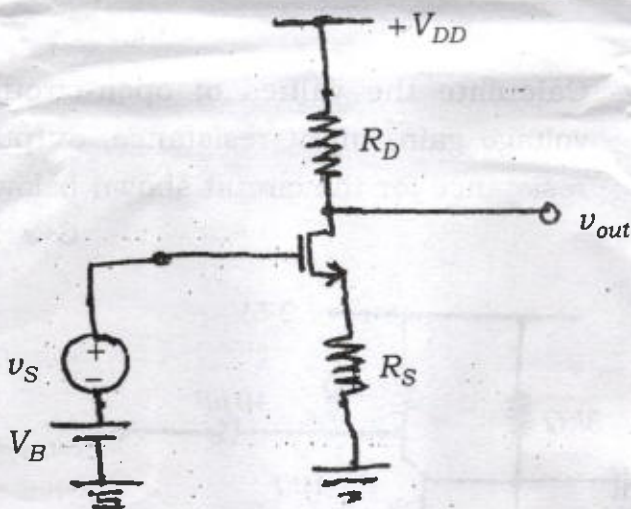5. (a) Derive the expression for open-circuit voltage gain,  $R_{in}$  and  $R_{out}$  for the circuit shown below. 6+2+2



- (b) Draw the model for 2-stage cascaded voltage amplifiers, hence derive the expressions for input loading, inter-stage loading and output loading parameters. 6
- (c) Describe the operation of series regulator using Zener diode with proper circuit diagram. 4

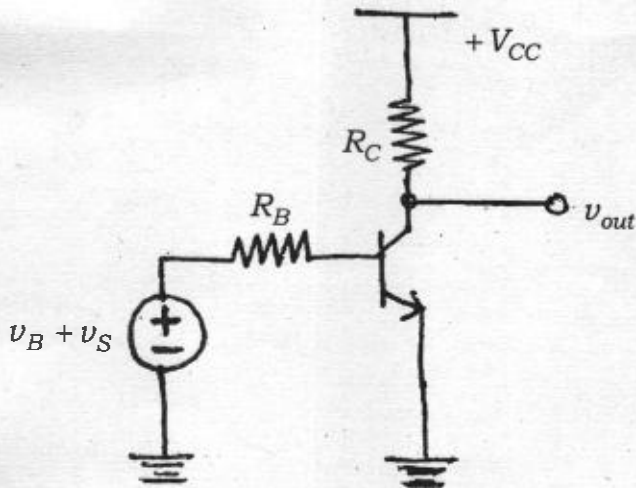6. (a) Derive the expression for  $-3\text{dB}$  frequency of the amplifier shown below in HF band. 6



- (b) Mention the features of CE-CE cascaded amplifiers with circuit diagram. 4
- (c) Mention the parasitic capacitances for a BJT in Active mode, hence draw the small-signal model in HF band. 4
- (d) Derive the small-signal voltage gain, input resistance, output resistance of a common-source amplifier. 6