

Total number of printed pages-5

53 (EC 301) ELDC

2019

## ELECTRONIC DEVICES AND CIRCUITS

Paper : EC 301

Full Marks : 100

Time : Three hours

**The figures in the margin indicate full marks for the questions.**



Answer **any five** questions out of 7.

1. (a) Why power amplifiers are necessary in electronic system? Mention the important parameters used for evaluating their performances. Explain the operation of class A power amplifier. 2+2+6
  
- (b) Describe the operation of Zener diode based series regulator and derive the expression for its duty cycle. 8+2

Contd.

2. (a) Determine the node voltages and branch currents in the circuit given below. (Fig.1) 4

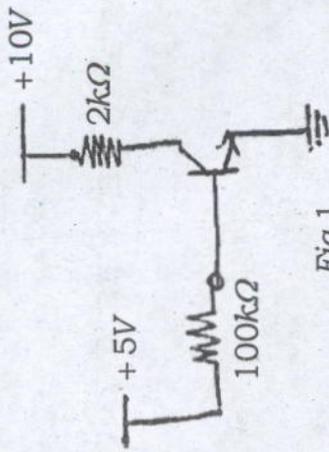


Fig.1

- (b) Derive the expression for small-signal voltage gain, input resistance and output resistance for the amplifier shown in Fig 2. 10

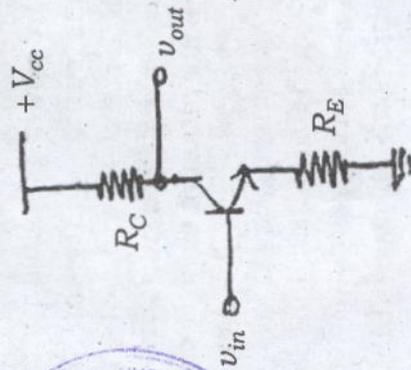


Fig.2

- (c) Write a short note on shunt voltage regulator. 6

3. (a) Describe the operation of Class-B power amplifier and hence derive its efficiency. 8+2

- (b) Common-Collector amplifier can work as a voltage buffer. Justify with proper expressions. 10

4. (a) Describe the need of tuned amplifiers in electronic communication systems. Classify them. Derive the expression for small-signal voltage gain, hence plot the frequency response. 2+2+6

- (b) Explain the operation of Buck-Boost regulator and derive its efficiency. 8+2

5. (a) Give a detail comparison (table format) about the small-signal operation of BJT-amplifiers, and hence discuss which amplifier is suitable for voltage amplification. 6+2

(b) Calculate the value of voltage gain, input resistance and output resistance for the following amplifier (Fig 3)

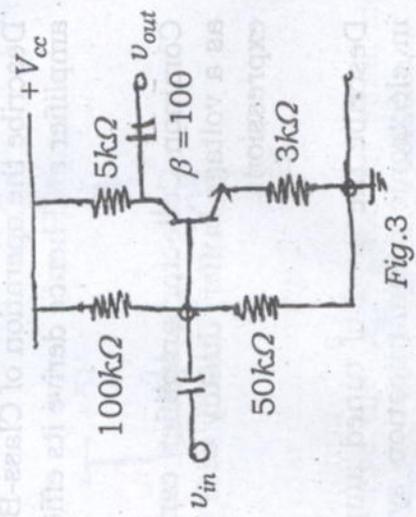


Fig.3

6. (a) Derive the expression for the small-signal voltage gain, input resistance and output resistance for the amplifier shown in Fig 4. 6+4+2

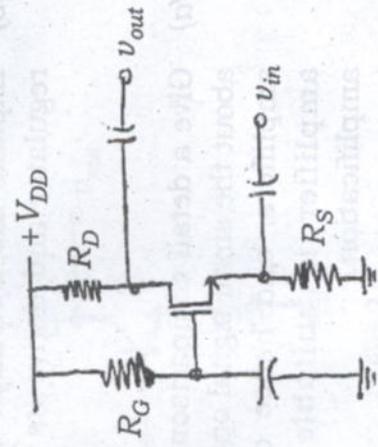


Fig.4

(b) Describe various types of coupling techniques used in designing multi-stage amplifiers and derive the expression for voltage gain of a CE-CC cascade. 4+4

7. (a) Why input impedance and output impedance of an amplifier are important? Prove that a common-source amplifier has more input impedance than a common emitter amplifier. 2+8

(b) Describe the operation of a Buck regulator and derive the expression for its duty cycle. 8+2

