

Total number of printed pages-4

53 (EC 401) DGEL

2012 C

2013

(May)

## DIGITAL ELECTRONICS

Paper : EC 401

Full Marks : 100

Pass Marks : 30

Time : Three hours

*The figures in the margin indicate full marks for the questions.*

*Answer any five questions.*

1. (a) Express the following decimal numbers in the XS-3 code. 3

(i) 2515      (ii) 653

- (b) Minimize the following expression using K-map

$$Y(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 5, 6, 7, 11, 13, 14)$$

5

Contd.

- (c) Design a 5-bit odd parity generator. Draw and explain the carry look-ahead adder.

5+7=12

2. (a) Design a 2-bit comparator using logic gates.

5

- (b) What is multiplexer? Implement the following function using 8 : 1 MUX.


$$f(A, B, C, D) = \sum m(2, 4, 5, 7, 10, 14)$$

3+8=11

- (c) Distinguish between combinational and sequential circuits.

4

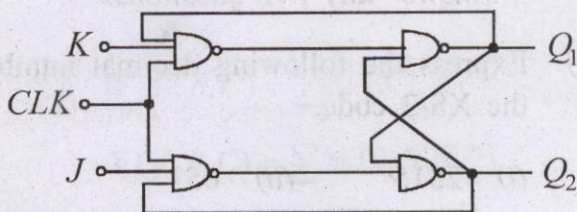3. (a) Identify  $Q$  and  $\bar{Q}$  outputs of the clocked J-K flip-flop shown in figure below :



- (b) Draw the logic circuit of J-K flip-flop using T-flip-flop.

6

- (c) Design a MOD-5 synchronous counter using T-flip-flop.

10



4. (a) What is register ? Describe the working of a 4-bit SISO shift register and draw the waveforms of shift register for serial input. 3+7=10
- (b) Design a sequential generator using J-K flip-flop to generate the sequence. 10
- $0 \rightarrow 2 \rightarrow 4 \rightarrow 5 \rightarrow 1 \rightarrow 7 \rightarrow 6$
5. (a) For a memory with M words storage, find the number of pins required for addressing and range in binary format for each of the following cases.
- (i)  $M = 64$       (ii)  $M = 16$  5
- (b) State the relative merits of static and dynamic RAMs. 5
- (c) State the full name of the following memory devices and describe very briefly the function of *each one*. 10
- (i) ROM      (ii) EPROM
6. (a) Explain CMOS inverter gate with a circuit diagram. 5

(b) Explain the basic ECL OR / NOR gate with a neat circuit diagram. Why does the ECL family have the lowest propagation delay of all logic families? 10

(c) When does a TTL circuit act as a current source? As a current sink? 5

7. (a) Draw the block diagram of PLA and write the applications of PLA. 5

(b) Realize the following equations with a suitable PLA and draw the logic diagram using PLA.

(i)  $f_1(A, B, C, D) = A\bar{B}D + \bar{A}B\bar{D}$   
 $f_2(A, B, C, D) = A + B\bar{D}$  6

(ii)  $W(A, B, C) = \sum m(0, 1, 4)$  9

$$X(A, B, C) = \sum m(0, 3, 4, 7)$$

$$Y(A, B, C) = \sum m(1, 2, 6)$$

$$Z(A, B, C) = \sum m(2, 3, 6, 7)$$