

Total number of printed pages-5

53 (EC 401) DGEL

2014

DIGITAL ELECTRONICS

Paper : EC 401

Full Marks : 100

Pass Marks : 30

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

1. (a) Convert the following decimal numbers to Gray Code and excess-3 code.

(i) $(126)_{10}$

(ii) $(379)_{10}$

4

Contd.

(b) State and prove De Morgan's theorem. Write the Boolean equations for the circuits of fig. 1(a) & fig. 1(b). Simplify the equations and draw the simplified logic circuit.

3+5=8

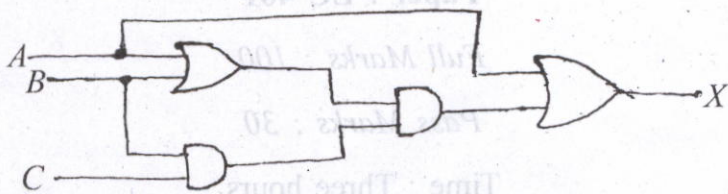


fig. 1(a)

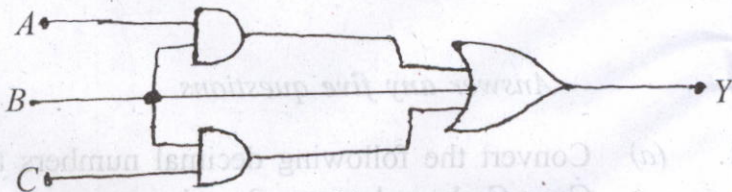


fig. 1(b)

(c) Describe the operation of Full adder and Full subtractor.

8

2. (a) Obtain the simplified expression in product of sums by using K-maps and implement it using basic gates only.

$$(i) F(A, B, C, D) = \sum m(2, 3, 5, 13, 14) + d(8, 9, 10, 11)$$

$$(ii) F(P, Q, R, S) = \sum m(2, 3, 6, 7, 8, 9, 12, 13) + d(4, 10, 14) \quad 10$$

- (b) How does look ahead carry adder speed up operation of addition? Explain 5

- (c) Describe the operation of 3 line to 8 line decoder. 5

3. (a) Design the following code converters : 2×5=10
(any two)

(i) BCD to XS-3

(ii) Gray to binary

(iii) BCD to sevensegment common anode.

- (b) An *S-R* flip flop is connected as shown in fig. (2). Determine the Q output in relation to the clock. What specific function does this device perform? 4

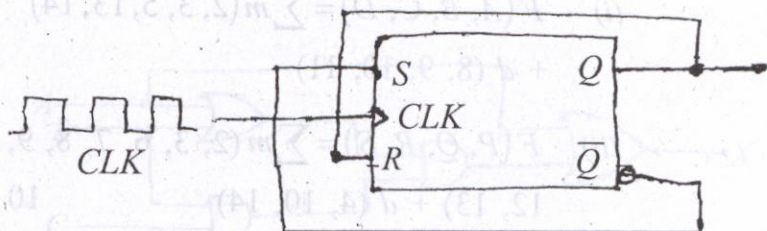


fig. (2)

- (c) Describe the working of a *J-K* flip flop. How does it differ from *T* flip flop. 6
4. (a) Explain what you understand by a register. Describe the working of a serial in serial out shift register. 2+5=7
- (b) Design a Mod-9 ripple counter using *J-K* flip flop and draw the output waveform. 7
- (c) Design a circuit to generate the sequence $0 \rightarrow 1 \rightarrow 5 \rightarrow 4 \rightarrow 7 \rightarrow 3$ using *T*-flip flop. 6
5. (a) What is the difference between truth table and excitation table. Design and implement a Mod-6 synchronous counter using *J-K* flip flop. 3+7=10

- (b) Convert the following flip flop 10
 (i) S-R to D flip flop
 (ii) J-K to S-R flip flop

6. (a) State the relative merits of static and dynamic RAMs. With suitable example, explain expanding the word size and word capacity of the memory. 5+10=15

- (b) Design a $2K \times 8$ bit memory chip using $2K \times 4$ chips. 5

7. (a) Draw the Block diagram of PLA and explain the functions. 10

- (b) What is the difference between PLA and PAL. Realize the following equations with suitable PLA. Draw the logic diagram using PLA. 2+8=10

$$W(A, B, C) = \sum m(0, 1, 4)$$

$$X(A, B, C) = \sum m(0, 3, 4, 7)$$

$$Y(A, B, C) = \sum m(1, 2, 6)$$

$$Z(A, B, C) = \sum m(2, 3, 6, 7)$$