

Total number of printed pages-7

53 (EC 401) DGEL

2017

DIGITAL ELECTRONICS

Paper : EC 401

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer **any five** questions.

1. (a) Perform the following operations using 2's complement arithmetic. $2+2=4$

(i) $(+37)+(-18)$

(ii) $(+24)-(+14)$

- (b) For the logic circuit shown below, answer the following: $2+2+4=8$

 


Figure 1

Contd.

- (i) Draw the truth table
- (ii) Find out the expression for Y and simplify
- (iii) Implement the same using only 2-input NAND gates.

(c) Simplify the following Boolean expressions — 2+2=4

(i) $[A\bar{B}(C+BD) + \bar{A}\cdot\bar{B}]C$

(ii) $\overline{AB+AC} + \bar{A}\bar{B}C$

(d) Minimize using K-map.

$$Y(A, B, C, D) = \sum m(0, 2, 3, 8, 10, 12) + \phi(6, 9, 15)$$

4

2. (a) Design a full-adder using two half-adders and explain its working. 4

(b) Using full-adders, design a circuit that is capable of performing both 4-bit binary addition as well as subtraction.

5


(c) Implement the Boolean function

$$F(A, B, C) = \bar{A}C + A\bar{B}C + AB\bar{C} \text{ using a 4:1 MUX.}$$

3

- (d) Determine the function performed by the following circuit. Also, what will be the output (Y) if $S_1 = 1$ and $S_0 = 0$?

3

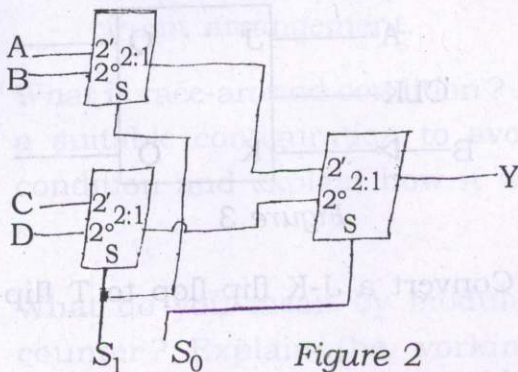

- (e) Implement a Full-subtractor using 2×4 decoders and some basic gates if required.
3. (a) Differentiate between —
- (i) Synchronous and Asynchronous inputs
 - (ii) Level and Edge triggered flip-flops
 - (iii) D-latch and D-flip-flop.
- (b) Explain the working of an active HIGH J-K flip-flop.

- (c) Consider a J-K flip-flop shown below. Find out its characteristic table and write the characteristic equation for Q_{n+1} in terms of A and B. 4

 


Figure 3

- (d) Convert a J-K flip-flop to T flip-flop. 6
4. (a) A new clocked flip-flop has two inputs X and Y in addition to the clock input. The flip-flop functions as follows —
 $2+2+6=10$
- If $XY=00$, the flip-flop changes state with each clock pulse
- If $XY = 01$, the output Q becomes '1' with the next clock pulse
- If $XY = 10$, the output Q becomes '0' with next clock pulse
- If $XY = 11$, the output Q retains its state.
- (i) Write the characteristic table for the XY flip-flop

- (ii) Write the excitation table for the flip-flop
- (iii) Show the necessary steps required to implement this XY flip-flop using a J-K flip-flop and draw the circuit arrangement.

(b) What is race-around condition? Provide a suitable configuration to avoid this condition and explain how it works.

B	A	Next State (Q _{next})	5
1	1	0	
x	1	0	

(c) What do you mean by modulus of a counter? Explain the working of a 4-bit binary ripple counter. 5

5. (a) Differentiate between asynchronous and synchronous counters. 2

(b) Determine the number of flip-flops required to design a counter that is capable of counting upto 4000 items. 2

(c) Design a 3-bit counter which counts in the following sequence — 8

0 → 3 → 6 → 1 → 4 → 7 → 2 → 5 → 0 → 3... etc.

- (d) The following table gives an excitation table of a certain flip-flop having A and B as inputs. Use this flip-flop to design a MOD-5 synchronous counter that follows the sequence $0 \rightarrow 1 \rightarrow 3 \rightarrow 5 \rightarrow 7$ and resets to 0 at the end of sequence. Also, the counter should reset itself to 0 whenever its goes to unwanted state.

Present State (Q_n)	Next State (Q_{n+1})	A	B
0	0	0	0
0	1	0	1
1	0	1	x
1	1	x	1

Table 1 8

6. (a) Design an Excess-3 to BCD code converter using suitable PLA or PAL. 8

- (b) Implement the following Boolean functions using suitable PAL —

$$W(A, B, C) = \sum m(0, 1, 2, 4, 6)$$

$$X(A, B, C) = \sum m(0, 2, 6, 7)$$

$$Y(A, B, C) = \sum m(3, 6)$$

$$Z(A, B, C) = \sum m(1, 5, 7) \quad 8$$

(c) Differentiate between — 4

(i) ROM and RAM

(ii) Static RAM and Dynamic RAM.