

2017

**DIGITAL ELECTRONICS**

Paper : EC 401 (Back)

Full Marks : 100

Time : Three hours

**The figures in the margin indicate full marks for the questions.**


Answer **any five** questions.

1. (a) Convert the following decimal numbers to Gray code and excess-3code.

(i)  $(102)_{10}$       (ii)  $(145)_{10}$       4

- (b) State and prove De Morgan's theorem.      4

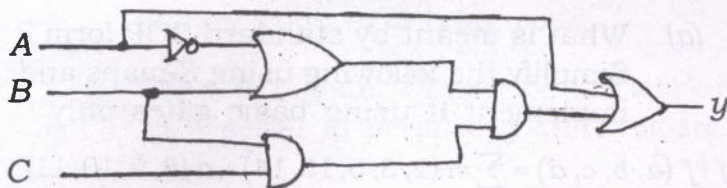- (c) For the logic circuit shown below, answer the following :



- (i) Find out the expression for y and simplify.

Contd.

- (ii) Draw the truth table.  
 (iii) Implement the simplified logic circuit using NAND gates only.

6

(d) Simplify the following Boolean expressions : 3+3=6

(i)  $Y = ABCD + ABC\bar{D} + \bar{A}BCD + \bar{A}BC\bar{D}$

(ii)  $[A\bar{B}(C + BD) + \bar{A}\bar{B}]C$

2. (a) What is parity generator? Design a combinational logic circuit with four input variables that will produce logic 1 output when the number of '1' in input is even. 2+4=6

(b) Design a 2-bit comparator using gates. 6

(c) Design a full subtractor and explain its operation. 6

(d) What is binary decoder? 2

3. (a) What is meant by standard SOP form? Simplify the following using K-maps and implement it using basic gates only

(i)  $f(a, b, c, d) = \sum m(2, 3, 5, 13, 14) + d(8, 9, 10, 11)$


(ii)  $f(P, Q, R, S) = \prod M(1, 2, 3, 8, 10, 12, 13, 14, 15)$   
 2+5+5=12

(b) What is Multiplex? Implement a full adder using two 4:1 MUX. 2+6=8

4. (a) Differentiate between sequential and combinational circuits. 4

(b) Draw a neat logic diagram of clocked J-K flip-flop using NAND gates and explain its operation. 6

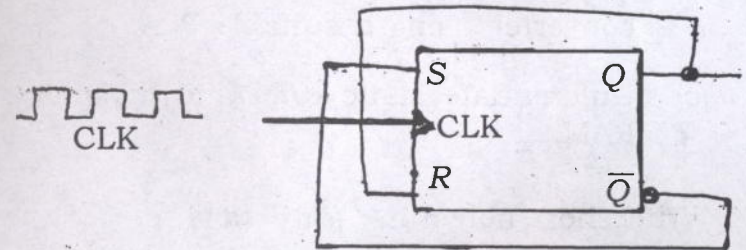(c) An S-R flip-flop is connected as shown in fig. below. Determine the Q output in relation to the clock. What specific function does this device perform? 6



(d) Design a logic circuit converts a 3 bit binary code to a Gray code. 4

5. (a) What is register? Describe the working of a serial in serial out shift register. 2+4=6

(b) Design and implement a Mod-5 synchronous counter using J-K flip-flop. 7

(c) Design a circuit to generate the sequence  $0 \rightarrow 2 \rightarrow 4 \rightarrow 6 \rightarrow 3$ . 7

6. (a) What is the difference between PLA and PAL? Realize the following equations with a suitable PLA.  $2+8=10$

$$W(A, B, C) = \sum m(0, 1, 4)$$

$$X(A, B, C) = \sum m(0, 3, 4, 7)$$

$$Y(A, B, C) = \sum m(1, 2, 6)$$

$$Z(A, B, C) = \sum m(2, 3, 6, 7)$$

(b) Design a 3 bit Gray to binary code converter using a suitable PLA. 7

(c) Differentiate static RAM and dynamic RAM. 3

7. Write short notes on : **(any two)**  $2 \times 10 = 20$

(i) Multiplexer and Demultiplexer

(ii) Programmable Logic Devices

(iii) Seven Segment Decoder.