

Total number of printed pages-7

53 (EC 401) DGEL

2018

**DIGITAL ELECTRONICS**

Paper : EC 401

Full Marks : 100

Time : Three hours

**The figures in the margin indicate full marks for the questions.**

Answer **any five** questions.

1. (a) Convert the following —  $4 \times 0.5 = 2$
- (i)  $(23.15)_{16}$  to Binary
  - (ii)  $(84.25)_{10}$  to Octal
  - (iii)  $(101011)_2$  to Gray
  - (iv)  $(11000.011)_2$  to Octal
- (b) Perform the following operations using 2's complement arithmetic — 4
- (i)  $(+45) + (-19)$
  - (ii)  $(+32) - (+18)$

Contd.

(c) Implement EX-OR and EX-NOR gates using only NOR gates. 4

(d) For the circuit given below, answer the following — 2+2+2=6

 


Fig : (1)

- (i) Expression for Y and simplify
- (ii) Truth table
- (iii) Implement the simplified expression using only NAND gates.

(e) Simplify the following Boolean expressions — 2+2=4

(i)  $[A\bar{B}(C+BD)+\bar{A}\bar{B}]C$

(ii)  $\overline{AB+AC}+\bar{A}\bar{B}C$

2. (a) Find the simplified expression for the following using K-map technique and implement the same using basic gates.

4+6=10

(i)  $Y(A, B, C, D) = \pi M(1, 2, 5, 6, 7, 13, 14)$   
 $+ \phi(0, 3, 15)$

$$(ii) \quad F(A, B, C, D, E)$$

$$= \sum m(0, 1, 2, 4, 5, 6, 13, 16, 17, 18, 20, 21, 22, 31)$$

$$+ \phi(8, 9, 10, 11, 30)$$

- (b) Explain the working of a Carry Propagation Lookahead Carry Generator for a 4-bit parallel binary adder. 6
- (c) A digital circuit has two *i/p* lines and four *o/p* lines such that, the *o/p* lines are used to turn ON/OFF four LEDs. Design the logic circuit so that at least one LED is turned ON depending on the status of *i/p* lines but no two LEDs should be turned on simultaneously. 4
3. (a) Implement the given Boolean Expression using a 4:1 MUX — 5

$$Y = ABC + A\bar{B} + \bar{B}C$$

- (b) Implement a Full-Adder using a 3-to-8 decoder and external NOR gates. 5

- (c) Find out the Boolean Expression for the following — 2+3=5

(i)

 


Fig. (2.1)

(ii)

 


Fig. (2.2)

- (d) Explain the construction and working of an Active HIGH J-K flip-flop.

5

4. (a) Consider an Active HIGH J-K flip-flop shown Below, and answer the questions that follow — 5+5=10

 


Fig.(3)

- (i) Find out the characteristic table and characteristic equation for  $Q_{n+1}$  in terms of A.
- (ii) Show the o/p wave form for 'Q' if the q/p 'A' changes its state to low (assuming it was HIGH permanently)
- (b) The excitation table of a flip-flop 'AB' is given as — 10

$Q_n$	$Q_{n+1}$	A	B
0	0	X	1
0	1	X	0
1	0	0	X
1	1	1	X

Use this 'AB' flip-flop to construct a D-flip-flop.

5. (a) Explain the working of a 4-bit ripple counter with necessary diagram and also show how it can be used to count UP or count DOWN by adding external logic hardware. 10

(b) Design a counter that follows the given count sequence — 8

000 → 010 → 011 → 101 → 111 → 000

(c) Differentiate between Asynchronous and Synchronous Counters. 2

6. (a) Realize the following equations with a suitable PLA. 12

$$W(A,B,C,D) = \sum m(0,1,5,9,12)$$

$$X(A,B,C,D) = \sum m(1,2,3,9,10)$$

$$Y(A,B,C,D) = \sum m(4,5,12)$$

$$Z(A,B,C,D) = \sum m(2,3,6,9)$$

(b) Explain how D-flip-flops are used to construct an  $n$ -bit register with an example and necessary diagram. 8

7. Write short notes on : **(any four)**  $4 \times 5 = 20$

(i) TTL

(ii) ECL

- (iii) BCD to Seven Segment Decoder
  - (iv) Magnitude Comparator
  - (v) Binary Codes
  - (vi) Memory Devices.
-

