

Total number of printed pages-6

53 (EC 401) DGEL

2021

DIGITAL ELECTRONICS

Paper : EC 401

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer **any five** questions.

1. (a) Explain the working of a standard TTL NAND with the help of circuit diagram. 6
- (b) For any logic family, describe the following terms briefly — Propagation delay, Fan-out and Noise margin. 6
- (c) Mention some advantages of a TTL circuit with open-collector. 3
- (d) Implement a two-input EX-OR in CMOS. 5

Contd.



2. (a) Implement the following Boolean expressions using NAND gates only — 4

(i) $Y = A \cdot B + \bar{A} \cdot \bar{B}$

(ii) $Y = \bar{A}(\bar{A} + B)$

(b) Minimize the following — 3+5=8

(i) $Y(A, B, C) = \Pi M(0, 1, 3, 7) \cdot \phi(5)$


(ii) $Y(A, B, C, D, E) = \sum m(1, 2, 3, 6, 8, 10, 21, 24, 31) + \phi(5, 15)$

(c) Perform the following operations using 2's complement arithmetic — 4

(i) $(+40) - (+25)$

(ii) $(+15) - (-18)$

 (d) Determine the O/P expression and truth table for the logic circuit shown below — 4





3. (a) What is a full-adder? Determine its truth table and logic circuit. 4



(b) Explain the working of a Four-Bit parallel adder-subtractor. 6

(c) What are parity generator and parity checker circuits? Briefly explain *any one* type with the help of its truth table and logic circuit. 6

 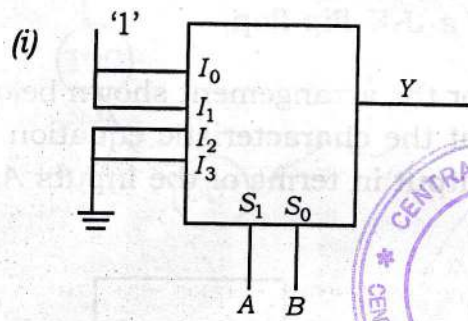(d) Find out the O/P expression for the following — 4




  4. (a) Explain the working of a 3-to-8 line Decoder with the help of its truth table and logic circuit. 5
- (b) Differentiate between Level-triggered and Edge-triggered flip-flops. 2
- (c) Explain the working of an active HIGH S-R latch. 5
- (d) Implement a D-flip-flop with the help of a J-K flip-flop. 5
- (e) For the arrangement shown below, find out the characteristic equation for the output in terms of the inputs A , B and C . 3



5. (a) Design a modulo-6 ripple counter that skips the states 110 and 111. 6

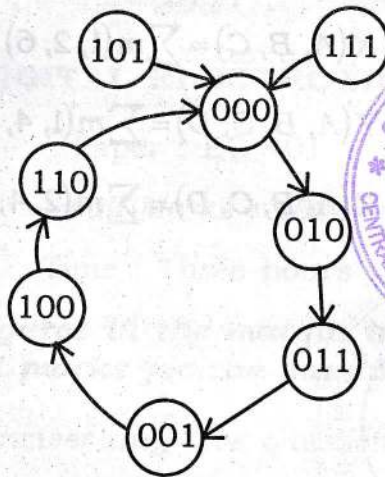- (b) Design a counter using J-K flip-flops based on the state transition diagram shown below — 8



- (c) Draw the timing waveforms for a Four-bit Serial-in-Serial-out shift register if the input data is (1010). 6
6. (a) Briefly explain the different types of memory devices. 4
- (b) Explain how a binary '1' is written into a dynamic RAM cell with the help of its circuit diagram. 6

(c) Implement the following with a suitable PLA : 10

(i) $W(A, B, C) = \sum m(0, 1, 5)$

(ii) $X(A, B, C) = \sum m(1, 2, 6)$

(iii) $Y(A, B, C, D) = \sum m(1, 4, 6, 9)$

(iv) $Z(A, B, C, D) = \sum m(2, 4, 8, 12)$

