

Total number of printed pages-6

53 (EC 403) LICR

2016

LINEAR INTEGRATED CIRCUIT

Paper : EC 403

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.


Answer **any five** questions.

- (a) Draw the circuit diagram for mono-stable multivibrator using 555-timer and describe the fuel-operation with timing diagrams. Derive the expression for the time period of the output waveform. 2+6+2


(b) How a precision rectifier is different from a normal rectifier? Explain the fuel-operation of a precision rectifier with circuit diagram and o/p waveforms. 2+6+2

Contd.

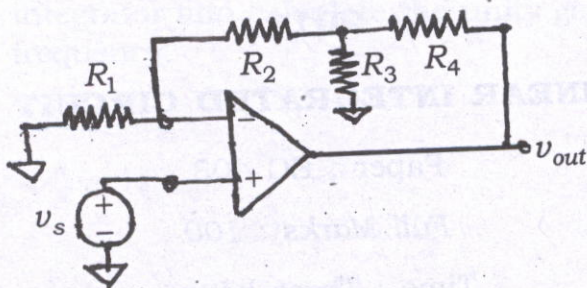2. (a) Assuming an ideal op-amp, derive the expression for the output voltage for the following circuit 8



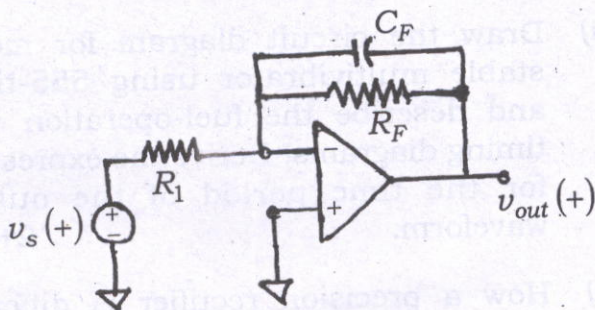
- (b) Calculate the DC gain, -3dB frequency and unity gain frequency of the following circuit. What is the high frequency gain of the circuit? 2+4+4+2



3. (a) Derive the expression for differential gain in a dual input unbalanced output (Active load). 12

(b) An Astable multivibrator can produce square waves. Justify with circuit diagram and full explanation of the operation for the same circuit. 8

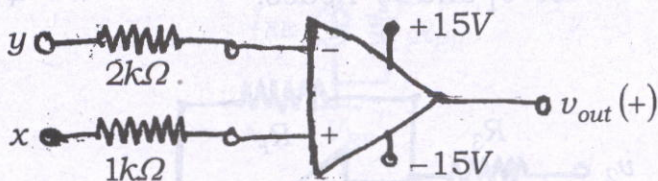
4. (a) A sinusoidal input of $10V_{p-p}$, $1kHz$ is applied to the following circuit at 'x' node and a reference voltage of $+5V$ at 'y' node. Draw the output and input waveforms. 5



(b) Design an Active-Butterworth 1st order low-pass filter which has a DC gain of $60dB$ in the pass band and edge of stop-band frequency $10kHz$. 5


(c) How can you make a wide-band pass filter with the help of low pass and high pass filter? Explain. 5

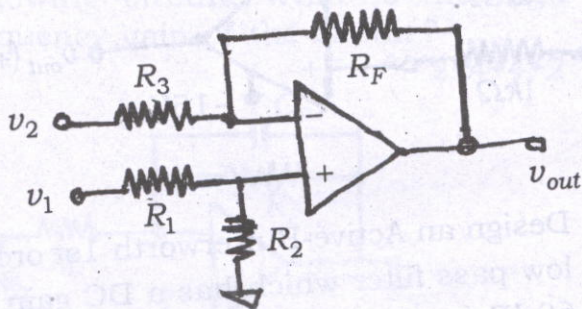- (d) Design a logarithmic amplifier using op-amp. 5
5. (a) Describe how an op-amp can be used for current amplification with proper circuit diagram. 5
- (b) Derive the expression for the output voltage in the circuit shown below and mention the input resistance expression for v_1 and v_2 nodes. 4+2




3. (c) Calculate the expression for common-mode gain for the above circuit shown and mention what will be output resistance of the same circuit. 7+2

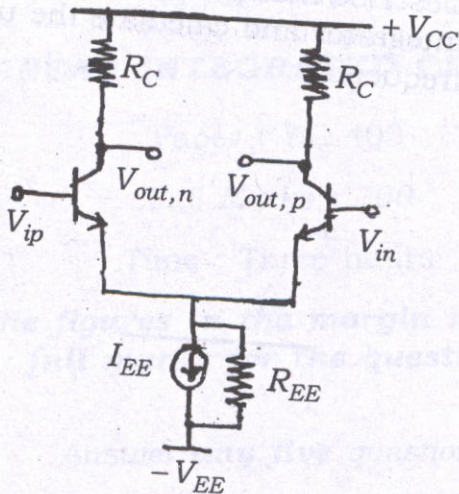6. (a) Derive the expression for differential gain and common-mode gain for the following circuit. 5+5



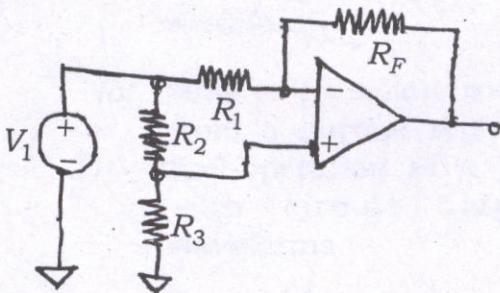- (b) Derive the expression for output voltage for the following circuit (Assuming ideal op-amp). 10



7. (a) Describe the operation of PLL with the help of block diagram. 10
- (b) Describe the operation of non-inverting integrator and calculate the unity gain frequency. 10

