

Total number of printed pages-4

53 (EC 403) LINC

2014

## LINEAR INTEGRATED CIRCUIT

Paper : EC 403

Full Marks : 100

Pass Marks : 30

Time : Three hours


**The figures in the margin indicate full marks for the questions.**

*Answer any five questions.*

1. (a) Describe the individual blocks of a phase Locked Loop with its functionality and write the Applications of PLL. 10
- (b) Mention different types of ADCs. 10  
Write the operation of SAR ADC.
2. (a) How an Instrumentation Amplifier is superior in performance as compared to operational Amplifier ? Derive the expression for the output voltage of an *B-op-Amp*-Instrumentation Amplifier. 10

*Contd.*

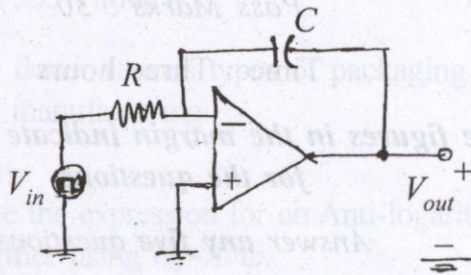
- (b) Design a band pass filter having  $f_L = 200\text{Hz}$  &  $f_\pi = 10\text{kHz}$ . Find the Quality factor and plot the frequency response. 5+5
3. (a) Describe how DC-non idealities effect the performance of the following circuit and how the effect can be nullified 10



- (b) Describe the operation of a Square-wave generator with proper timing waveforms and expressions. 10
4. (a) Write the measurement techniques required for measuring input offset voltage, input bias currents. 5

(b) Why frequency compensation is important in *Op-Amp* circuits? Explain. Mention types of compensation techniques. 10


(c) 5

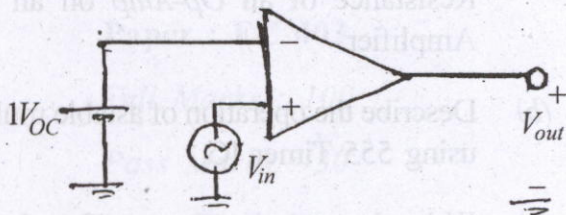

Describe the operation of the above circuit ; plot the input and *O/P* waveforms ; given

$$V_{in(+)} = 3 \sin 2\pi (1 \times 10^3) t.$$

5. (a) 12

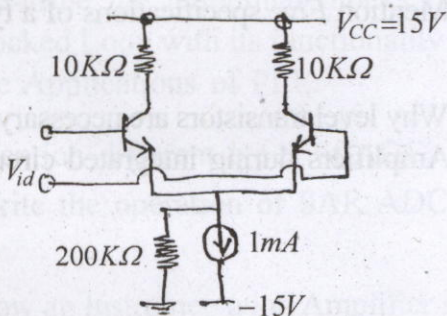

Shown above is a circuit of differential Amplifier ; Find differential input resistance, Small-signal voltage gain, common-mode gain, common-mode input resistance and CMRR in *dB*.



- (b) Describe the operation of a precision Half-wave Rectifier using *Op-Amp*. 8
6. (a) Describe the effect of non-zero output-Resistance of an *Op-Amp* on an inverting-Amplifier. 5
- (b) Describe the operation of astable multi-vibrator using 555 Timer IC. 10
- (c) Write down various types of packaging used in IC manufacturing. 5
7. (a) Derive the expression for on Anti-logarithmic Amplifier using *Op-Amp*. 10
- (b) Mention *Five* specifications of a typical ADC. 5
- (c) Why level transistors are necessary in cascaded Amplifiers during integrated circuit design ? 5