

Total number of printed pages-3

53 (EC 602) DLDG

2014

VLSI

Paper : EC 602

Full Marks : 100

Time : Three hours

*The figures in the margin indicate full marks for the questions.*

*Answer any five questions.*


1. (a) Describe the fabrication steps for an n-well CMOS technology with neat sketch. 10
- (b) Describe the operation of a CMOS inverter and find the expression for inverter threshold. 5+5
2. (a) Implement the following logic function in CMOS. 5
$$y = \overline{(A \cdot B) + (C \cdot D)}$$
- (b) Draw the layout for the above logic circuit. 10
- (c) Explain in brief the use of P-MOS  $\phi$ n-MOS transistors as a pass gate. 5

Contd.

3. (a) What is Bi-CMOS technology? Draw the cross-sectional view of a typical Bi-CMOS technology. Write the advantages and disadvantages of Bi-CMOS technology in comparison to CMOS technology. 2+5+3
- (b) What do you mean by Channel Length Modulation in a MOSFET transistor? Describe. 5
- (c) In a layout, the n-well layer used is of  $1\mu\text{m}$  long,  $500\text{nm}$  wide and  $20\text{nm}$  thick, given the resistivity is  $0.008\Omega\text{-cm}$ , find Sheet Resistance and Total Resistance. 5
4. (a) Describe the operation of an SRAM cell with proper circuit diagram. 10
- (b) Probe Testing is necessary in manufacturing integrated circuits. Explain why? 5
- (c) What you mean by Scaling? Explain how  $I_{\text{DS}}$ ,  $V_{\text{TH}}$ ,  $C_{\text{OX}}$ ,  $V_{\text{DD}}$  gets affected due to constant-field scaling. 5
5. (a) Describe the operation of a Bi-CMOS inverter and explain its problems. Why are improvements needed in the basic circuit to avoid these problems? 8+2

(b) Given a circuit below :

10

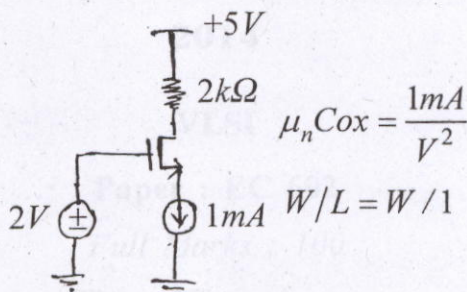

Find the value of  $V_{GS}$ ,  $V_{DS}$ ,  $g_m$  and  $r_o$

6. (a) Write VHDL code for implementing a 4:1 MUX using 2:1 MUXes in structural model. 10
- (b) Describe the Built-in-Self-Test technique used in Testing integrated circuits. 10
7. (a) Design a full-Adder having inputs as A, B, C and output as sum and carry in CMOS logic and draw the schematic diagram. 10
- (b) Write short note on oxidation. 5
- (c) Write the lithographic steps required for patterning a poly in a nMOS technology. 5