

Total number of printed pages—4

53 (EC 602) VLSI

2017

VLSI

Paper : EC-602

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer **any five** questions out of **seven**.

1. (a) Describe the fabrication steps for Bipolar Technology of draw the layout of $n-p-n$ Transistor by labelling each layer. 8+2
- (b) Describe the operation of 6T-SRAM cell and draw the layout of the cell. 8+2
2. (a) Draw the CMOS implementation of a Full-Adder. 6

Contd.


(b) Draw the layout of XOR and XNOR gate (2-input). 4

(c) List out the parasitic capacitance available in a MOS transistor and explain these capacitances with relevant expressions. Hence draw the small signal model of high frequencies.

2+6+2


3. (a) Describe the operation of CMOS inverters and hence derive the expression for threshold voltage. 6+4

 (b) Describe the lithographic sequences required to get pattern shown below. (With proper diagram) 6



(c) Write a short note on VLSI Design flow for digital circuit design. 4

 
4. (a) Draw the CMOS implementation of its corresponding layout of the circuit shown below : 2+4



- (b) Draw the diagram of an memory array. Explain the operation of 4bit \times 4bit NOR based ROM array and draw the corresponding layout. 2+8+4

5. (a) Calculate the expressions for rise and fall time for a CMOS inverter. 10

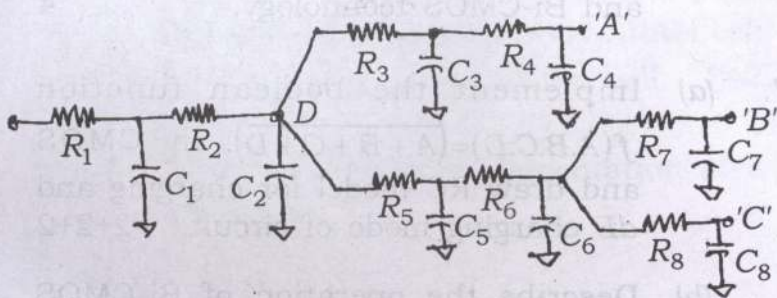- (b) Calculate the Elmore's delay for the RC-tree shown below of the node : 'A', 'B', 'C', 'D'. 10



6. (a) Explain the rotation operation for 4 bit binary number $B = b_3b_2b_1b_0$ with cross-bar switch diagram. (both left rotation and right rotation). 5+5

(b) A CMOS inverter designed in a CMOS process has $(W/L)_n = 6$ and $(W/L)_p = 8$ and the process parameters are as follows :

$$K'_n = 150 \mu A/V^2 \quad K'_p = 62 \mu A/V^2$$

$$V_{Tn} = 0.7V \quad V_{TP} = -0.85V$$

If the supply voltage used is 3.3V and total output capacitance is 150 fF, then calculate the rise time and fall time and maximum signal frequency.

2+2+2

(c) Compare the performances of CMOS and Bi-CMOS technology. 4

7. (a) Implement the boolean function $f(A,B,C,D) = \overline{(A+B+C+D)}$ in CMOS and draw RC model for charging and dB charging mode of circuit. 2+2+2

(b) Describe the operation of Bi-CMOS inverter and discuss its problems.

10+4