

Total number of printed pages-5

53 (EC 602) VLSI

2018

VLSI

Paper : EC 602


Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer **any five** questions out of **seven**.

 1. (a) Describe the lithographic sequences required for the following diagram (pattern). 6



- (b) Write a short note on oxidation process. 4
- (c) Derive the expression for Drain-to-Source current of an n -MOSFET biased in Triode mode and plot the $I_{DS} \sim V_{DS}$ characteristics. 10

Contd.

2. (a) Draw the cross-bar switch matrix for 4-bit left and right rotation. 5+5
- (b) Draw the cross-sectional view of Bi-CMOS technology. 4
- (c) Implement the boolean function in CMOS logic $f(A, B, C) = \overline{A + (B.C)}$ and draw the lumped RC model for charging and discharging path. 2+2+2
3. (a) Describe the operation of 1 bit DRAM cell and compare its performance with 1 bit SRAM cell. 8+2
- (b) Draw the CMOS schematics for a 2:1 MUX and corresponding layout. 2+4
- (c) Describe the operation of n-MOS as a pass transistor. 4
4. (a) Consider the CMOS inverter with following parameters.

$$nMOS : V_{TH.N} = 0.6V, \mu_n C_{ox} = 60 \mu A / v^2, \left(\frac{w}{L}\right)_N = 8$$


$$pMOS : V_{TH.P} = 0.7V, \mu_p C_{ox} = 25 \mu A / v^2, \left(\frac{w}{L}\right)_P = 12$$

Calculate the value of switching threshold, if the supply used is 3.3V.

4

 - (b) Calculate the on-resistance of the MOS circuit shown below :

$$\left[\text{given } \mu_n C_{ox} = 100 \mu \frac{A}{V^2}, \left(\frac{W}{L} \right) = 10 \right]$$




2

- (c) Write short note on constant voltage scaling. 4

- (d) Explain the operation of 2-4 bit binary numbers and draw the array base of multiplier architecture. 2+8

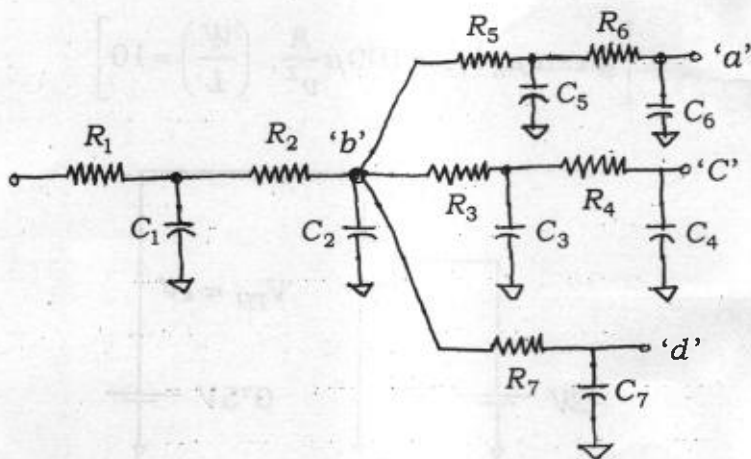5. (a) Calculate Elmore's Delay for the following RC-tree shown as 'a', 'b', 'c', 'd'. 10



- (b) Explain the logical implementation of 4 bit magnitude comparator with proper explanation. 10
6. (a) Describe the operation of 4 bit \times 4 bit NOR based ROM array with circuit diagram. 10
- (b) Draw the layout and schematic for the function $f(A, B, C) = \overline{(A + B)}.C$ 6
- (c) Describe the operation of a CMOS inverter. 4

7. (a) Draw and explain the fabrication steps for n-well CMOS process. 10
- (b) Explain the logical implementation of Zero/one detector and its operation. 6
- (c) Describe the inversion process of an n-MOS transistor biased properly. 4
-