

Total number of printed pages—6

53 (EC 301) ELDC

2014

ELECTRONICS DEVICES & CIRCUITS

Paper : EC 301

Full Marks : 100

Time : Three hours

*The figures in the margin indicate full marks
for the questions.*

Answer any Five questions out of Eight questions.

1. (a) Describe the graphical method and calculate the gain of the transistor amplifier by using both DC and AC load line. 7
- (b) Explain the characteristic comparison between CE, CB and CC amplifiers. 6
- (c) Compare the analysis of a transistor amplifier using H-parameters between common emitter amplifier and common-base amplifier. 7

Contd.

2. (a) With the help of diagram calculate and explain the voltage gain, input impedance and output impedance of Common Drain (CD) amplifier. 10
- (b) Point out the difference between voltage amplifier and power amplifier. Also give the characteristic comparison between the same. 10
3. (a) Explain Class A push-pull power amplifier and point out the difference of two collector currents. 10
- (b) For a source follower JFET amplifier, $R_g = 230M\Omega$, $R_s = 12.5K\Omega$ and $g_m = 800\mu sec$. Assuming infinite input resistance and neglecting FET output resistance, calculate voltage gain, input resistance and output resistance of the amplifier. 5
- (c) A Class B push-pull amplifier must deliver 20watt of audio-power to the output load
- (i) if the output transformer is 80% efficiency, what is the minimum power drain on the power supply under optimum conditions and
- (ii) what is the minimum average dissipation rating required for each transistor? 5

4. (a) Describe the necessity of a tuned amplifier over a certain frequency amplifiers. 5

(b) Explain the frequency response curve of Double tuned amplifier. Also point out the use of double tuned over single tuned amplifier. 9

(c) Explain the efficiency of Class B amplifier and point out that why Class B operation is more efficient than Class A operation. 6


5. (a) A voltage amplifier has a gain of $-10 \frac{V}{mv}$; express in dB .

(b) CE-CC cascade is advantageous than CE-CE cascade in terms of which parameter ?

(c) DC Coupled amplifiers are better than RC Coupled amplifier for integrated circuits application ; why ?

- (d) If Quiescent collector current increased by a factor of 2 then what happens to the transconductance of a BJT.
- (e) Write the expression for collector current that includes Early effect and draw the corresponding small signal model for BJT.
- (f) Draw the high frequency model of a BJT.
- (g) Gain of an amplifier falls at high frequencies. Why?
- (h) Out of CE, CB and CC configuration of amplifier topologies, which configuration is suitable for current amplification purpose and why?
- (i) Mention *four* specifications of a voltage regulator IC.
- (j) What is the interactive UPS ? $10 \times 2 = 20$
6. (a) Describe the operation of a Buck boost regulator with proper circuit diagram and find the expression for Duty cycle. 10

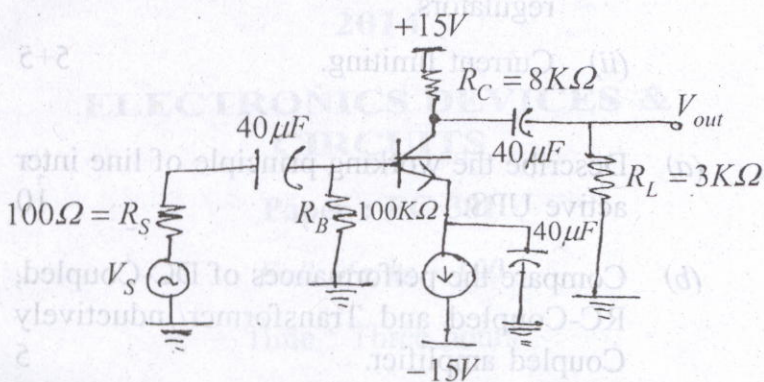- (b) Find (i) the gain of the amplifier circuit shown below.



- (ii) Find the input resistance
 (iii) Find the output resistance. 4+4+2

7. (a) Two non-ideal voltage amplifiers having ; input resistance R_{in1} , R_{in2} , output resistances R_{out1} , R_{out2} , gains AV_1 , AV_2 ; are cascaded and is driven by a non-ideal voltage source having source resistance R_S . The cascaded amplifier drives load R_L ;

- (i) Find the expression for over all voltage gain.
 (ii) How interstage coupling effect can be eliminated ? 6+4

- (b) Write short notes on :
- (i) Short circuit protection for voltage regulators.
 - (ii) Current limiting. 5+5
8. (a) Describe the working principle of line interactive UPS. 10
- (b) Compare the performances of DC-Coupled, RC-Coupled and Transformer/Inductively Coupled amplifier. 5
- (c) Find the expression for short circuit current gain of an $n-p-n$ transistor in saturation. 5