

Total No. of printed pages = 6

ECE-3101/EDC-II/5th Sem/2013/N

**ELECTRONIC CIRCUIT  
AND DEVICES - II**

Full Marks - 100

Pass Marks - 30

Time - Three hours

The figures in the margin indicate full marks  
for the questions.


Answer any *five* questions.

1. (i) Explain in steps how the load line and Q point can be determined in the output characteristics of a common emitter BJT configuration. Take the example of fixed bias common emitter configuration. 8
- (ii) In the given common emitter voltage divider bias configuration, determine the relations for the following : 6
  - (a) Input impedance

[Turn over

(b) Output impedance

(c) Voltage gain

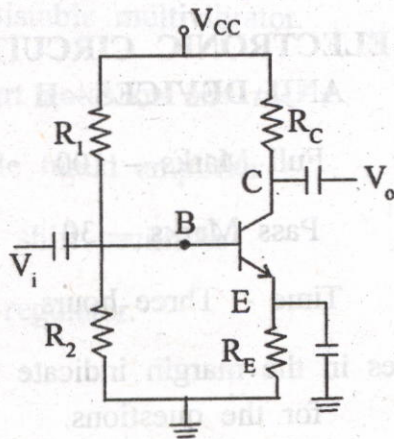


(iii) For the emitter bias network, determine :

6


(a)  $I_b$

(b)  $I_c$

(c)  $V_{CE}$

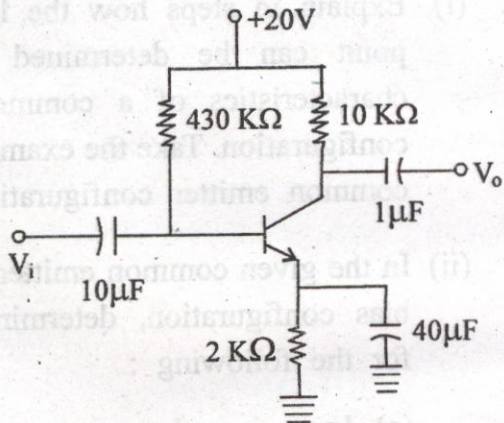


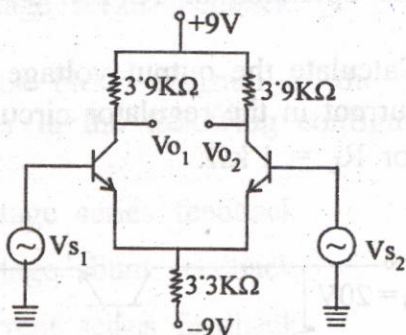2. (i) Calculate the d.c voltages and current in the circuit. 5



- (ii) Perform a.c analysis over a single input differential amplifier configuration and determine the relation for voltage gain. 7
- (iii) With the help of block diagram and relevant voltage waveforms, explain the operation of switching regulator or SMPS. 8
3. (i) What are the characteristics of an ideal operational amplifier? Explain briefly. 5
- (ii) Design a non-inverting amplifier using opamp having a voltage gain of 11. 5
- (iii) How opamp can be used to design an active filter? Explain with an example. 5
- (iv) Draw the circuit diagram of Wein bridge oscillator and describe its working. 5

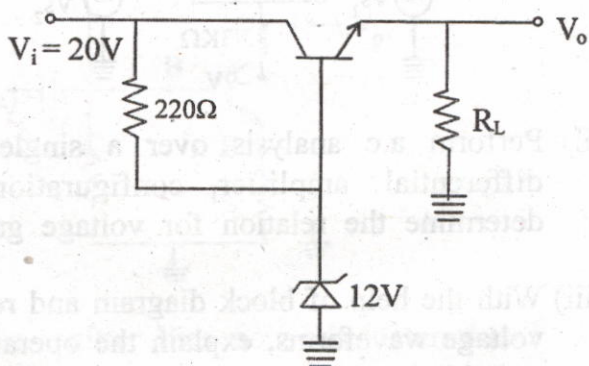4. (i) Describe with the help of a circuit diagram the operation of IC LM 317. 5
- (ii) Calculate the output voltage and the Zener current in the regulator circuit of the figure for  $R_L = 1\text{ k}\Omega$ . 5



- (iii) What is the difference between a regulated power supply and an unregulated power supply. 2
- (iv) Draw a voltage supply using a full-wave bridge rectifier, capacitor filter and IC regulator to provide an output of +12V. 4
- (v) What are the advantages of negative feedback? Explain. 4

5. (i) Deduce the expression for input impedance for voltage series feedback. 5
- (ii) Draw the block diagram of the feedback amplifier in the following configurations : 8
- (a) Voltage series feedback
  - (b) Voltage shunt feedback
  - (c) Current series feedback
  - (d) Current shunt feedback <sup>1i</sup>
- (iii) Determine the voltage gain and input impedance with feedback for voltage series feedback having  $A = -20$ ,  $R_i = 100 \text{ k}\Omega$  and  $R_o = 50 \text{ k}\Omega$  while  $\beta = -0.1$ . 5
- (iv) What are the Barkhausen criteria for oscillation ? 2
6. (i) With the help of a circuit diagram, explain the operation of a single tuned amplifier. Also, discuss the frequency response characteristics. 7
- (ii) Mention the reasons of oscillation in a tuned amplifier. Briefly explain the methods used to stabilize the tuned amplifier generated oscillations. 3

(iii) With the help of circuit diagrams, describe how a 555 timer can be used as :

(a) Astable multivibrator

(b) Bistable multivibrator.  $5+5=10$

7. Write short notes on any two :  $10 \times 2 = 20$

(i) Double tuned amplifier

(ii) Phase shift oscillator

(iii) Bulk regulator.